

BLACK+DECKER

The Best DIY Series from
the Brand You Trust

ADVANCED HOME WIRING

Updated 4th Edition



DC Circuits • Transfer Switches
Panel Upgrades • Circuit Maps • More



ADVANCED HOME WIRING

Updated 4th Edition

DC Circuits • Transfer Switches
Panel Upgrades • Circuit Maps • More



MINNEAPOLIS, MINNESOTA



First published in 2015 by Cool Springs Press,
an imprint of Quarto Publishing Group USA Inc.,
400 First Avenue North, Suite 400, Minneapolis, MN 55401

© 2015 Quarto Publishing Group USA Inc.

All rights reserved. With the exception of quoting brief passages for the purposes of review, no part of this publication may be reproduced without prior written permission from the Publisher.

The information in this book is true and complete to the best of our knowledge. All recommendations are made without any guarantee on the part of the author or Publisher, who also disclaims any liability incurred in connection with the use of this data or specific details.

Cool Springs Press titles are also available at discounts in bulk quantity for industrial or sales-promotional use. For details write to Special Sales Manager at Quarto Publishing Group USA Inc., 400 First Avenue North, Suite 400, Minneapolis, MN 55401 USA. To find out more about our books, visit us online at www.coolspringspress.com.

Library of Congress Cataloging-in-Publication Data

ISBN: 978-1-58923-906-1

Digital edition published in 2015
Digital ISBN: 978-1-62788-563-8

Acquisitions Editor: Mark Johanson
Design Manager: Brad Springer
Layout: Danielle Smith-Boldt
Edition Editor: Bruce Barker
Photography: Rau + Barber
Photo Assistance: Adam Esco

Printed in China
10 9 8 7 6 5 4 3 2 1

Advanced Home Wiring

Created by: The Editors of Creative Publishing international, Inc., in cooperation with BLACK+DECKER.

BLACK+DECKER and the BLACK+DECKER logo are trademarks of The Black & Decker Corporation and are used under license. All rights reserved.

NOTICE TO READERS

For safety, use caution, care, and good judgment when following the procedures described in this book. The publisher and BLACK+DECKER cannot assume responsibility for any damage to property or injury to persons as a result of misuse of the information provided.

The techniques shown in this book are general techniques for various applications. In some instances, additional techniques not shown in this book may be required. Always follow manufacturers' instructions included with products, since deviating from the directions may void warranties. The projects in this book vary widely as to skill levels required: some may not be appropriate for all do-it-yourselfers, and some may require professional help.

Consult your local building department for information on building permits, codes, and other laws as they apply to your project.

Contents

Advanced Home Wiring

| | |
|---|------------|
| Introduction | 5 |
| Wiring Safety | 6 |
| Planning Your Project | 8 |
| Highlights of the National Electrical Code | 12 |
| Wiring a Room Addition | 22 |
| Wiring a Kitchen | 26 |
| Circuit Maps | 31 |
| Common Household Circuits | 32 |
| GFCI & AFCI Breakers | 48 |
| Replacing a Service Panel | 50 |
| Grounding & Bonding a Wiring System | 58 |
| Installing a Subpanel | 64 |
| Baseboard Heaters | 68 |
| Wall Heaters | 72 |
| Backup Power Supply | 74 |
| Installing a Transfer Switch | 80 |
| Outbuildings | 86 |
| Standalone Solar Lighting System | 94 |
| Troubleshooting & Repairs | 101 |
| Types of Wall Switches | 110 |
| Specialty Switches | 118 |
| Ground-fault (GFCI) & Arc-fault (AFCI) Protection | 120 |
| Junction Boxes, Device Boxes & Enclosures | 122 |
| Index | 125 |



6



30




68



86




94

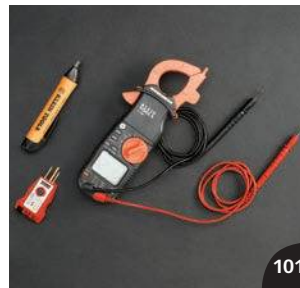


101



105

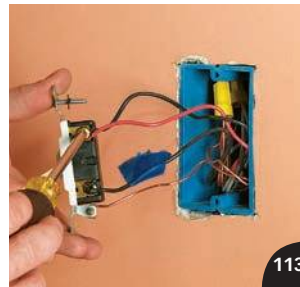

113

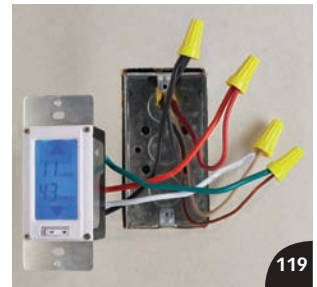

119



Q/REF

20
10 MA
AFCI TEST
HOM

15
10 MA
AFCI TEST
HOM

15
10 MA
AFCI TEST
HOM

20
10 MA
AFCI TEST
HOM

15
10 MA
AFCI TEST
HOM

20
10 MA
AFCI TEST
HOM

15
10 MA
AFCI TEST
HOM

20
10 MA
AFCI TEST
HOM

51
10 MA
AFCI TEST
HOM

20
10 MA
AFCI TEST
HOM

51
10 MA
AFCI TEST
HOM

0E
10 MA
AFCI TEST
HOM

0E
10 MA
AFCI TEST
HOM

51
10 MA
AFCI TEST
HOM

51
10 MA
AFCI TEST
HOM

H0405100053

N0902161501

H0407022179

Introduction

Experienced home electricians understand the need to keep up with changes in the world of wiring. Wiring projects, and more advanced projects in particular, almost always require a permit from your municipality and typically an on-site inspection or two as well. If you aren't up-to-date with wiring codes, there is a likelihood that your project will not pass inspection. But beyond the practicality of passing inspections, the codes that govern wiring practices are updated for good reason: they improve safety. And when you're talking about your own home and family, that's worth paying attention to.

This newest edition of BLACK+DECKER *Advanced Home Wiring* has been reviewed and revised to reflect the many changes to wiring code published in the 2014 edition of the National Electrical Code (NEC), which is updated every three years. And this time around there were an unusually high number of changes. They include the requirement that an available neutral wire be present in every switch box, expansion of the types of circuits that require AFCI protection, a new prohibition on tying into a garage receptacle, and more. Several of these changes are reflected in the updated information you'll find here.

Almost all of the advanced wiring projects featured in this book involve new circuitry, panel upgrades, or troubleshooting with diagnostic equipment. Among the high-level projects: making a direct-current, solar-electric circuit; upgrading the grounding and bonding on your new 200-amp or larger home circuit; installing an automatic transfer switch for your backup power supply; wiring a room addition; and using a multimeter to precisely locate an open neutral in a home circuit.

Because the projects found in this book are advanced in nature, do not attempt any of them unless you are confident in your abilities. Consult a professional electrician if you have any concerns—in many cases your best solution might be to do some of the work yourself, such as pulling new sheathed cable through walls, and to have the electrical contractor do the other work, such as making the connections. But do keep in mind that home wiring can be a fun and fascinating pursuit, and successfully accomplishing a major project is personally gratifying and can also save you substantial amounts of money.

Wiring Safety

Safety should be the primary concern of anyone working with electricity. Although most household electrical repairs are simple and straightforward, always use caution and good judgment when working with electrical wiring or devices. Common sense can prevent accidents.

The basic rule of electrical safety is: Always turn off power to the area or device you are working on. At the main service panel, remove the fuse or shut off

the circuit breaker that controls the circuit you are servicing. Then check to make sure the power is off by testing for power with a voltage tester. *Tip: Test a live circuit with the voltage tester to verify that it is working before you rely on it.* Restore power only when the repair or replacement project is complete.


Follow the safety tips shown on these pages. Never attempt an electrical project beyond your skill or confidence level.



Shut power OFF at the main service panel or the main fuse box before beginning any work.



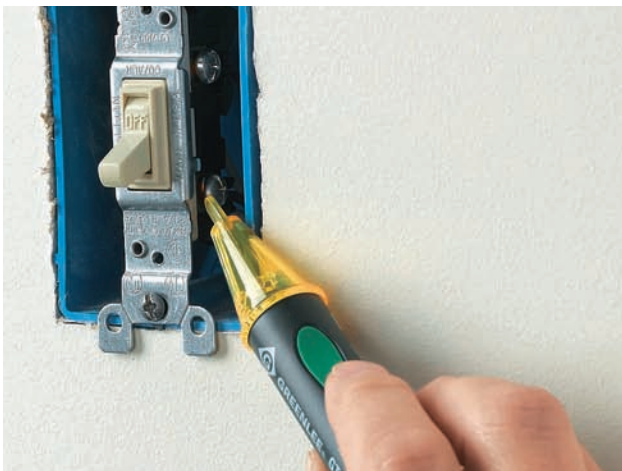Create a circuit index and affix it to the inside of the door to your main service panel. Update it as needed.



Confirm power is OFF by testing at the outlet, switch, or fixture with a voltage tester.



Use only UL-approved electrical parts or devices. These devices have been tested for safety by Underwriters Laboratories.



Wear rubber-soled shoes while working on electrical projects. On damp floors, stand on a rubber mat or dry wooden boards.



Use fiberglass or wood ladders when making routine household repairs near the service mast.



Extension cords are for temporary use only. Cords must be rated for the intended usage.



Breakers and fuses must be compatible with the panel manufacturer and match the circuit capacity.



Never alter the prongs of a plug to fit a receptacle. If possible, install a new grounded receptacle.



Do not penetrate walls or ceilings without first shutting off electrical power to the circuits that may be hidden.

Planning Your Project

Careful planning of a wiring project ensures you will have plenty of power for present and future needs. Whether you are adding circuits in a room addition, wiring a remodeled kitchen, or adding an outdoor circuit, consider all possible ways the space might be used, and plan for enough electrical service to meet peak needs.

For example, when wiring a room addition, remember that the way a room is used can change. In a room used as a spare bedroom, a single 15-amp circuit provides plenty of power, but if you ever choose to convert the same room to a family recreation space, you will need additional circuits.

When wiring a remodeled kitchen, it is a good idea to install circuits for an electric oven and countertop range, even if you do not have these electric appliances. Installing these circuits now makes it easy to convert from gas to electric appliances at a later date.

A large wiring project adds a considerable load to your main electrical service. In about 25 percent of all homes, some type of service upgrade is needed before new wiring can be installed. For example, many homeowners will need to replace an older 60-amp electrical service with a new service rated for 100 amps or more. This is a job for a licensed electrician but is well worth the investment. In other cases, the existing main service provides adequate power, but the main circuit breaker panel is too full to hold any new circuit breakers. In this case it is necessary to install a circuit breaker subpanel to provide room for hooking up added circuits. Installing a subpanel is a job most homeowners can do themselves (see pages 65 to 67).


This chapter gives an easy five-step method for determining your electrical needs and planning new circuits.

Five Steps for Planning a Wiring Project




1 **Examine your main service panel** (see page 10). The amp rating of the electrical service and the size of the circuit breaker panel will help you determine if a service upgrade is needed.


2

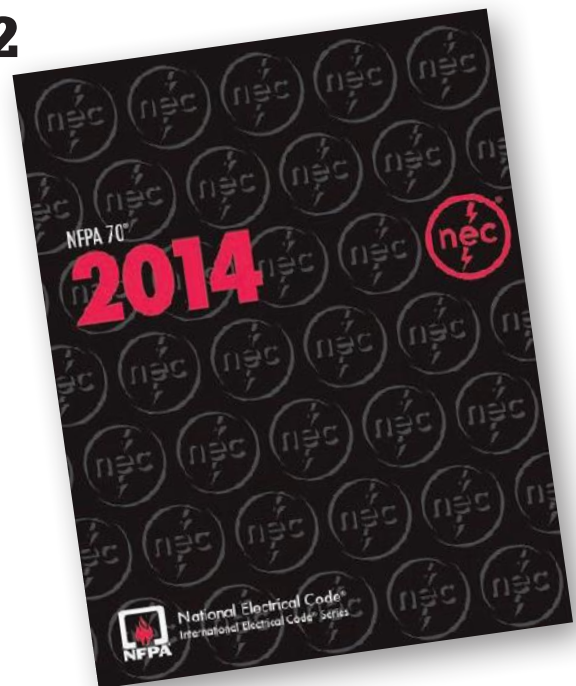

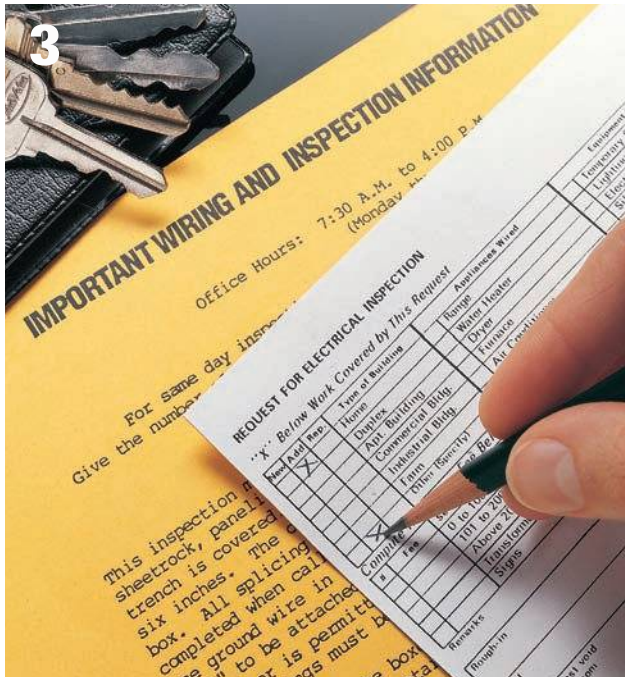
Learn about codes (see pages 11 to 13). The National Electrical Code (NEC), and local electrical codes and building codes, provide guidelines for determining how much power and how many circuits your home needs. Your local electrical inspector can tell you which regulations apply to your job.



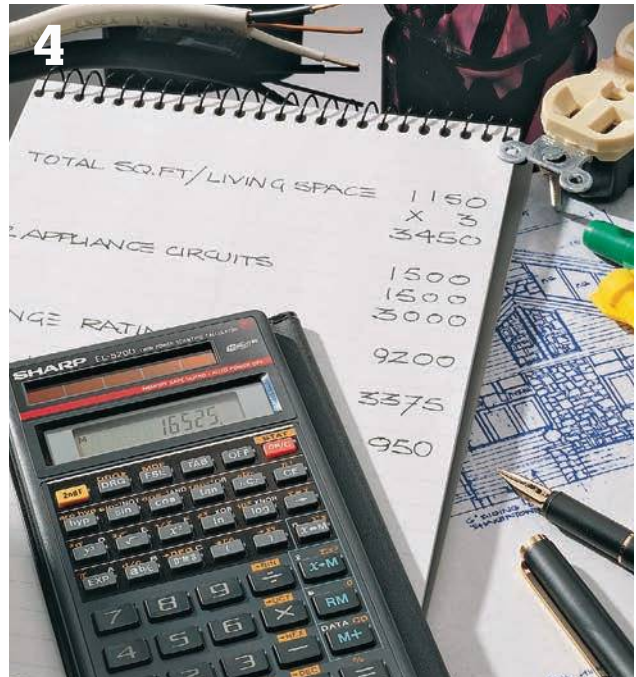Prepare for inspections (see pages 14 to 15). Remember that your work must be reviewed by your local electrical inspector. When planning your wiring project, always follow the inspector's guidelines for quality workmanship.



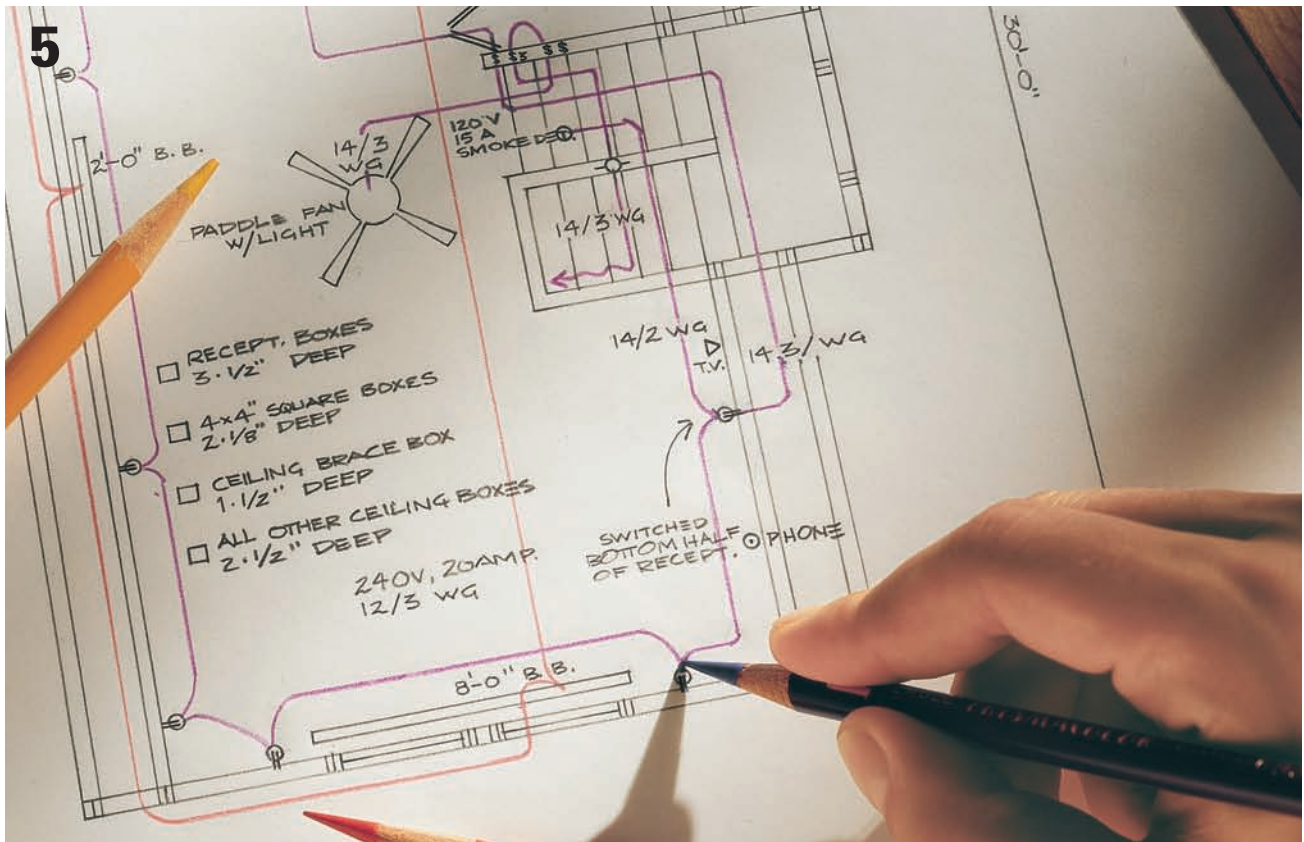Evaluate electrical loads (see pages 16 to 19). New circuits put an added load on your electrical service. Make sure that the total load of the existing wiring and the planned new circuits does not exceed the service capacity or the capacity of the panel.



Draw a wiring diagram and get a permit (see pages 20 to 21). This wiring plan will help you organize your work.

Examine Your Main Service Panel

The first step in planning a new wiring project is to look in your main circuit breaker panel and find the size of the service by reading the amperage rating on the main circuit breaker. As you plan new circuits and evaluate electrical loads, knowing the size of

the main service helps you determine if you need a service upgrade.


Also look for open circuit breaker slots in the panel. The number of open slots will determine if you need to add a circuit breaker subpanel.



Find the service size by opening the main service panel and reading the amp rating printed on the main circuit breaker. In most cases, 100-amp service provides enough power to handle the added loads of projects such as the ones shown in this book. A service rated for 60 amps or less should be upgraded. Note: In some homes the main circuit breaker is located in a separate box.



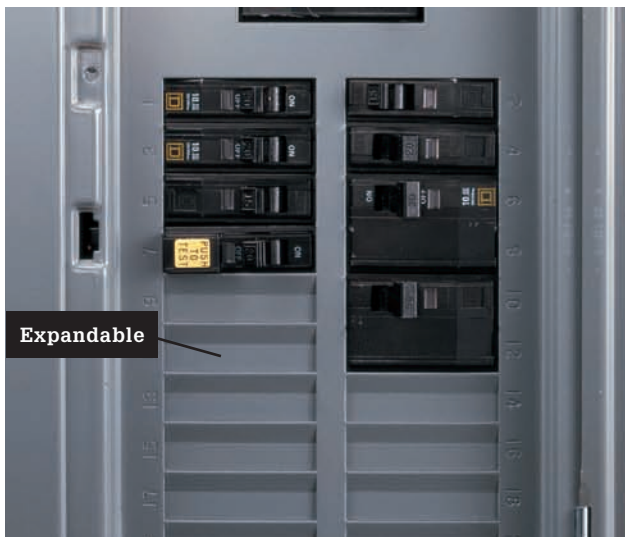Older service panels use fuses instead of circuit breakers. Have an electrician replace this type of panel with a circuit breaker panel that provides enough power and enough open breaker slots for the new circuits you are planning.



Look for open circuit breaker slots in the main circuit breaker panel or in a circuit breaker subpanel, if your home already has one. You will need one open slot for each 120-volt circuit you plan to install and two slots for each 240-volt circuit. If your main circuit breaker panel has no open breaker slots, install a subpanel (see pages 65 to 67) to provide room for connecting new circuits.

Learn About Codes

To ensure public safety, your community requires that you get a permit to install new wiring and have the work reviewed by an inspector. Electrical inspectors use the National Electrical Code (NEC) as the primary authority for evaluating wiring, but they also follow the local building code and electrical code standards.

Most communities use a version of the NEC that is not the most current version. Also, many communities make amendments to the NEC, and these amendments may affect your work.

As you begin planning new circuits, call or visit your local electrical inspector and discuss the project with him or her. The inspector can tell you which of the national and local code requirements apply to your job and may give you a packet of information summarizing these regulations. Later, when you apply to the inspector for a work permit, he or she

will expect you to understand the local guidelines as well as a few basic NEC requirements.

The NEC is a set of standards that provides minimum safety requirements for wiring installations. It is revised every three years. The national code requirements for the projects shown in this book are thoroughly explained on the following pages. For more information, you can find copies of the current NEC, as well as a number of excellent handbooks based on the NEC, at libraries and bookstores.

In addition to being the final authority of code requirements, inspectors are electrical professionals with years of experience. Although they have busy schedules, most inspectors are happy to answer questions and help you design well-planned circuits.

Basic Electrical Code Requirements



Electrical code requirements for living areas: Living areas need at least one 15-amp or 20-amp basic lighting/receptacle circuit for each 600 sq. ft. of living space and should have a dedicated circuit for each type of permanent appliance, such as an air conditioner, or a group of baseboard heaters. Receptacles on basic lighting/receptacle circuits should be spaced no more than 12 ft. apart. Many electricians and electrical inspectors recommend even closer spacing. Any wall more than 24" wide also needs a receptacle. Every room should have a wall switch at the point of entry to control either a ceiling or wall-mounted light or plug-in lamp. Kitchens and bathrooms must have a ceiling or wall-mounted light fixture.

Highlights of the National Electrical Code ▶

BY MATERIAL

Panels

- Maintain a minimum 30" wide by 36" deep of clearance in front of the panel.
- Match the amperage rating of the circuit when replacing fuses.
- Use handle ties on all 240-volt breakers and on 120-volt breakers protecting multi-wire branch circuits.
- Close all unused panel openings.
- Label each fuse and breaker clearly on the panel.

Electrical Boxes

- Use boxes that are large enough to accommodate the number of wires and devices in the box.
- Install all junction boxes so they remain accessible.
- Leave no gaps greater than 1/8" between wallboard and the front of electrical boxes.
- Place receptacle boxes flush with combustible surfaces.
- Leave a minimum of 3" of usable cable or wire extending past the front of the electrical box.

Wires & Cables

- Use wires that are large enough for the amperage rating of the circuit.
- Drill holes at least 2" from the edges of joists. Do not attach cables to the bottom edge of joists.
- Do not run cables diagonally between framing members.
- Use nail plates to protect cable that is run through holes drilled or cut into studs less than 1 1/4" from the front edge of a stud.
- Do not crimp cables sharply.
- Contain spliced wires or connections entirely in a plastic or metal electrical box.
- Use wire connectors to join wires.
- Use staples to fasten cables within 8" of an electrical box and every 54" along its run.
- Leave a minimum 1/4" (maximum 1") of sheathing where cables enter an electrical box.
- Clamp cables and wires to electrical boxes with approved clamps. No clamp is necessary for one-gang plastic boxes if cables are stapled within 8".
- Connect only a single wire to a single screw terminal. Use pigtails to join more than one wire to a screw terminal.

Switches

- Use a switch-controlled receptacle in rooms without a built-in light fixture operated by a wall switch.
- Use three-way switches at the top and bottom on stairways with six risers or more.
- Use switches with grounding screws with plastic electrical boxes.
- Locate all wall switches within easy reach of the room entrance and not behind the door.
- Install a neutral wire in switch boxes.
- Use black or red wires to supply power to switched devices.

Receptacles

- Install receptacles on all walls 24" wide or greater.
- Install receptacles so a 6-ft. cord can be plugged in from any point along a wall or every 12 ft. along a wall.
- Include receptacles in any hallway that is 10 ft. long or longer.
- Use three-slot, grounded receptacles for all 15- or 20-amp, 120-volt branch circuits.
- Include a switch-controlled receptacle in rooms without a built-in light fixture operated by a wall switch.
- Install GFCI-protected circuits in bathrooms, kitchens, garages, crawl spaces, unfinished basements, and outdoor receptacle locations.

Light Fixtures

- Use mounting straps that are anchored to the electrical boxes to mount ceiling fixtures.
- Keep non-IC-rated recessed light fixtures 3" from insulation and 1/2" from combustibles.
- Include at least one switch-operated lighting outlet in every room.

Grounding

- Ground receptacles by connecting receptacle grounding screws to the circuit grounding wires.
- Use switches with grounding screws whenever possible. Always ground switches installed in plastic electrical boxes and all switches in kitchens, bathrooms, and basements.

BY ROOM

Kitchens/Dining Rooms

- Install at least two 20-amp small appliance receptacle circuits.
- Install dedicated 15-amp, 120-volt circuits for dishwashers and food disposals (required by many local codes).
- Install GFCI protection for all countertop receptacles; receptacles behind fixed appliances do not need to be GFCI protected.
- Position receptacles for appliances that will be installed within cabinets, such as microwaves or food disposals, according to the manufacturer's instructions.
- Include receptacles on all counters wider than 12".
- Space receptacles a maximum of 48" apart above countertops and closer together in areas where many appliances will be used.
- Locate receptacles on the wall above the countertop not more than 20" above the countertop.
- Install at least one receptacle not more than 12" below the countertop on islands and peninsulas that are 12" x 24" or greater.
- Do not connect lights to the small appliance receptacle circuits.
- Install at least one wall or ceiling-mounted light fixture.

Bathrooms

- Install a separate 20-amp GFCI-protected circuit only for bathroom receptacles.
- Ground switches in bathrooms.
- Install at least one receptacle not more than 36" from each sink.
- Install at least one ceiling- or wall-mounted light fixture.

Utility/Laundry Rooms

- Install a separate 20-amp circuit for a washing machine.
- Install approved conduit for wiring in unfinished rooms.
- Use GFCI-protected circuits for 120-volt receptacles within 6 feet from a sink (including the washing machine receptacle).

Living, Entertainment, Bedrooms

- Install at least one 15- or 20-amp lighting/receptacle circuit for each 600 sq. ft. of living space.
- Install a dedicated circuit for each permanent appliance, such as an air conditioner or group of electric baseboard heaters.
- Use electrical boxes listed and labeled to support ceiling fans.
- Include receptacles on walls 24" wide or more.
- Space receptacles on walls in living and sleeping rooms a maximum of 12 ft. apart.
- Check with your local electrical inspector about requirements for installing smoke and carbon monoxide alarms during remodeling.

Outdoors

- Check for underground utilities before digging.
- Use UF cable or other wiring approved for wet locations for outdoor wiring.
- Run cable and wires in schedule 80 PVC plastic and other approved conduit, as required by local code.
- Install in-use rated weatherproof receptacle covers.
- Bury cables and wires run in conduit at least 18" deep; cable not in conduit must be buried at least 24" deep.
- Use weatherproof electrical boxes with watertight covers.
- Install GFCI-protected circuits for receptacles.
- Support boxes that are not attached to a building and that contain switches or receptacles using at least two pieces of conduit. Secure the conduit not more than 18 feet from the box. Locate the box at least 12" above the ground.

Stairs/Hallways

- Use three-way switches at the top and bottom on stairways with six risers or more.
- Include receptacles in any hallway that is 10 ft. long or longer.
- Position stairway lights so each step and landing is illuminated.

Prepare for Inspections

Electrical inspectors who issue the work permit for your wiring project will also visit your home to review the work. Make sure to allow time for these inspections as you plan the project. For most projects, inspectors make two visits.


The first inspection, called the rough-in, is done after the cables are run between the boxes but before the insulation, wallboard, switches, and fixtures are installed. The second inspection, called the final, is done after the walls and ceilings are finished and all electrical connections are made.

When preparing for the rough-in inspection, make sure the area is neat. Sweep up sawdust and clean up any pieces of scrap wire or cable insulation. Before inspecting the boxes and cables, inspectors will check to make sure all plumbing and other mechanical work is completed. Some electrical inspectors will ask to see your building and plumbing permits.

At the final inspection, inspectors check random boxes to make sure the wire connections are correct. If they see good workmanship at the selected boxes, the inspection will be over quickly. However, if they spot a problem, inspectors may choose to inspect every connection.

Inspectors have busy schedules, so it is a good idea to arrange for an inspection several days in advance. In addition to basic compliance with code, inspectors expect your work to meet their own standards for quality. When you apply for a work permit, make sure you understand what the inspectors will look for during inspections.

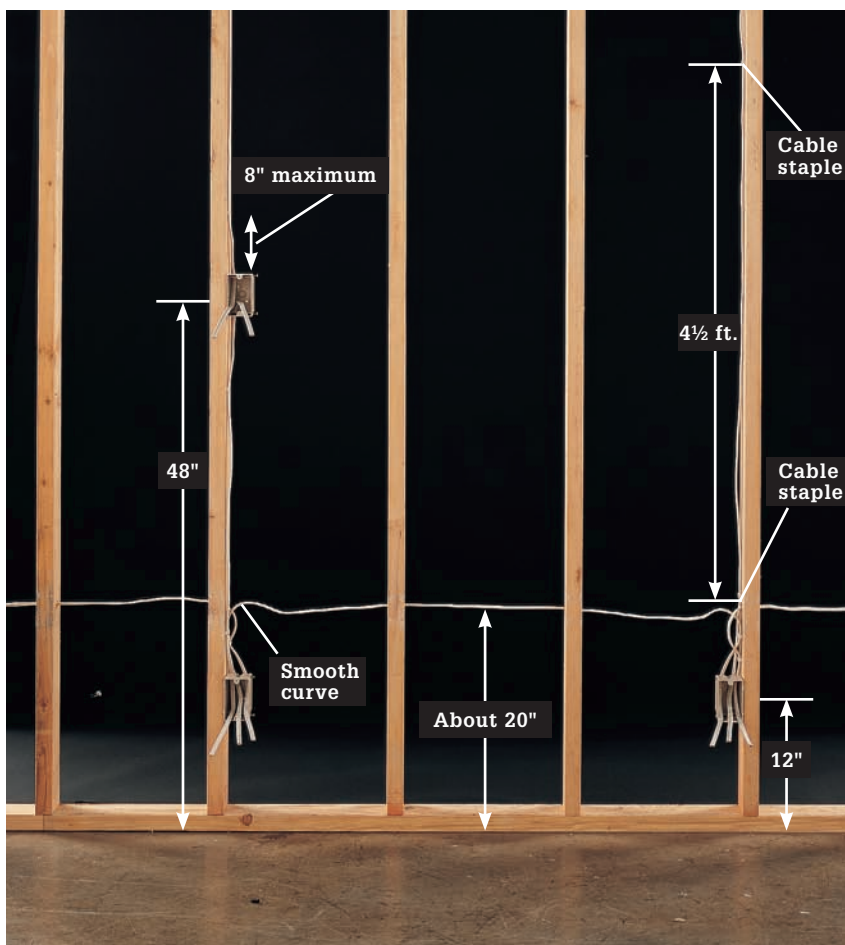
You cannot put new circuits into use legally until an inspector approves them at the final inspection. If you have planned carefully and done your work well, electrical inspections are routine visits that give you confidence in your own skills.



Inspectors may measure to see that electrical boxes are mounted at consistent heights. Height may not be dictated by code, but consistency is a sign of good workmanship. Measured from the center of the boxes, receptacles in living areas typically are located 12" above the finished floor and switches at 48". For special circumstances, inspectors allow you to alter these measurements. For example, you can install switches at 36" above the floor in a child's bedroom, or set receptacles at 24" to make them more convenient for someone using a wheelchair.


Inspectors will check cables to see that they are anchored by cable staples driven within 8" of each box and every 4½ ft. thereafter when they run along studs. When bending cables, form the wire in a smooth curve. Do not crimp cables sharply or install them diagonally between framing members. Some inspectors specify that cables running between receptacle boxes should be about 20" above the floor.

What Inspectors Look for

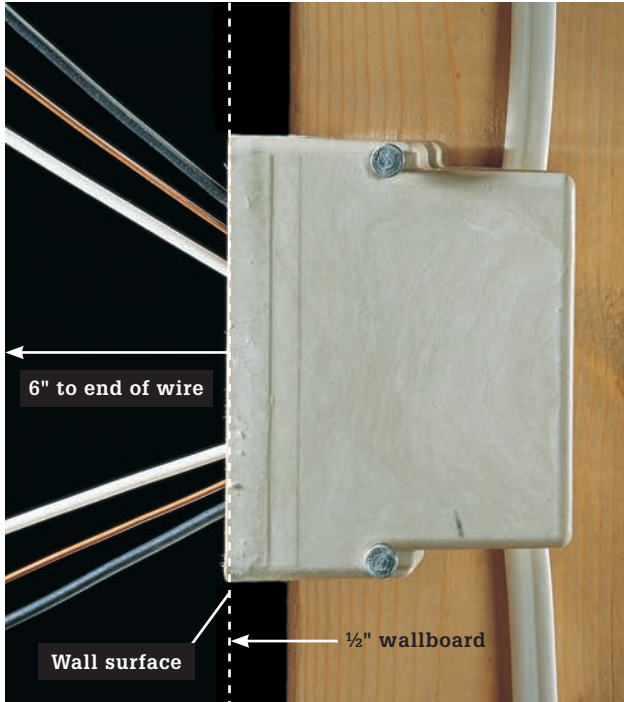


Electrical box faces should extend past the front of framing members so the boxes will be flush with finished walls (left). Inspectors will check to see that all boxes are large enough for the wires they contain. Cables should be cut and stripped back so that at least 3" of usable length extends past the front of the box and so that at least 1/4" of sheathing reaches into the box (right). Label all cables to show which circuits they serve: inspectors recognize this as a mark of careful work. The labels also simplify the final hookups after the wallboard is installed.

Is your Receptacle Spacing Correct? ▶

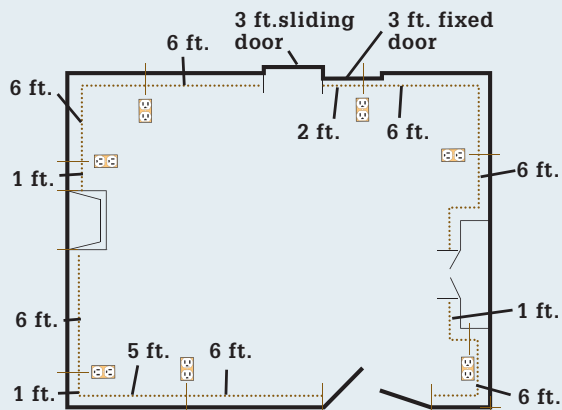

Example of receptacle spacing requirements in a typical room. Measure receptacle spacing distance along the wall line. Install receptacles along partial height walls and along balcony guards in lofts and similar areas.

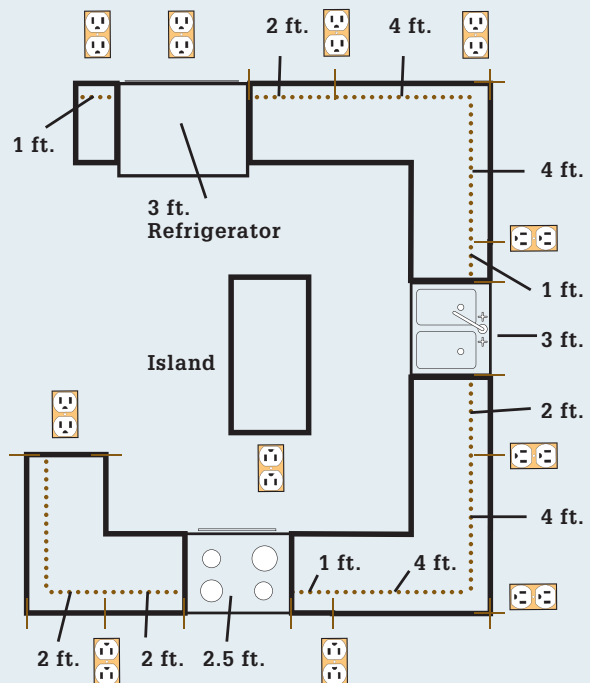Example of countertop receptacle spacing in a typical kitchen (right).



Evaluate Electrical Loads

Before drawing a plan and applying for a work permit, make sure your home's electrical service provides enough power to handle the added load of the new circuits. In a safe wiring system, the current drawn by fixtures and appliances never exceeds the main service capacity.

To evaluate electrical loads, use whatever evaluation method is recommended by your electrical inspector. Include the load for all existing wiring as well as that for proposed new wiring when making your evaluation.

Most of the light fixtures and plug-in appliances in your home are evaluated as part of general allowances for basic lighting/receptacle circuits and small-appliance circuits. However, appliances that are permanently installed require their own dedicated circuits. The electrical loads for these appliances are added in separately when evaluating wiring.

If your evaluation shows that the load exceeds the main service capacity, you must have an electrician upgrade the main service before you can install new wiring. An electrical service upgrade is a worthwhile investment that improves the value of your home and provides plenty of power for present and future wiring projects.



Amperage ▶



Amperage rating can be used to find the wattage of an appliance. Multiply the amperage by the voltage of the circuit. For example, a 13-amp, 120-volt circular saw is rated for 1,560 watts.

| AMPS × VOLTS | TOTAL CAPACITY | SAFE CAPACITY |
|----------------|----------------|---------------|
| 15 A × 120 V = | 1,800 watts | 1,440 watts |
| 20 A × 120 V = | 2,400 watts | 1,920 watts |
| 25 A × 120 V = | 3,000 watts | 2,400 watts |
| 30 A × 120 V = | 3,600 watts | 2,880 watts |
| 20 A × 240 V = | 4,800 watts | 3,840 watts |
| 30 A × 240 V = | 7,200 watts | 5,760 watts |


Calculating Loads



Add 1,500 watts for each small appliance circuit required by the local electrical code. In most communities, three such circuits are required—two in the kitchen and one for the laundry—for a total of 4,500 watts. No further calculations are needed for appliances that plug into small-appliance or basic lighting/receptacle circuits.



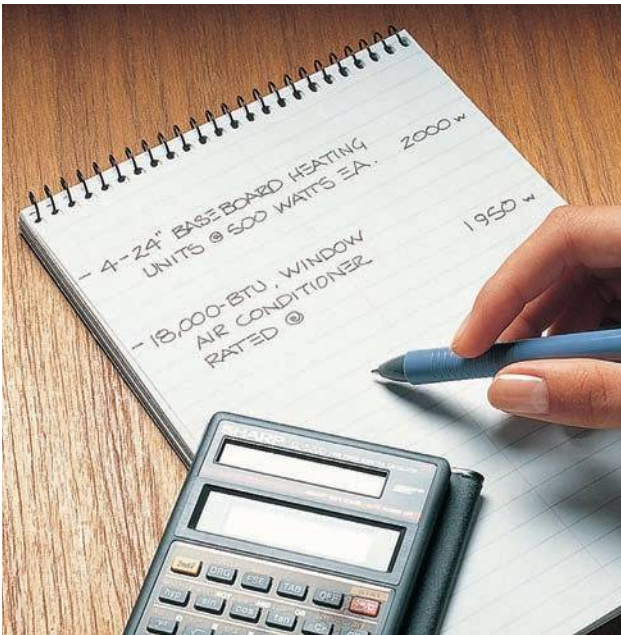If the nameplate gives the rating in kilowatts, find the watts by multiplying kilowatts times 1,000. If an appliance lists only amps, find watts by multiplying the amps times the voltage—either 120 or 240 volts.



Air-conditioning and heating appliances are not used at the same time, so figure in only the larger of these two numbers when evaluating your home's electrical load.

Fixed Devices ▶

Do not connect one or more fixed devices that in total exceed 50 percent of a multiple outlet branch circuit's amperage rating. Fixed devices do not include light fixtures. This means that all fixed devices (such as a permanently wired disposal or hot water circulating pump) on a multiple outlet branch circuit may not exceed 7.5 amps (about 900 watts) on a 15-amp multiple outlet branch circuit and may not exceed 10 amps (about 1,200 watts) on a 20-amp multiple outlet branch circuit.

Locating Wattage



Light bulb wattage ratings are printed on the top of the bulb. If a light fixture has more than one bulb, remember to add the wattages of all the bulbs to find the total wattage of the fixture.



Electric water heaters are permanent appliances that require their own dedicated 30-amp, 240-volt circuits. Most water heaters are rated between 3,500 and 4,500 watts. If the nameplate lists several wattage ratings, use the one labeled "Total Connected Wattage" when figuring electrical loads.



Food disposers are considered permanent appliances and may require their own dedicated 15-amp, 120-volt circuits. Most disposers are rated between 500 and 900 watts.



Dishwashers installed permanently under a countertop may need a dedicated 15-amp, 120-volt circuits. Dishwasher ratings are usually between 1,000 and 1,500 watts. Portable dishwashers are regarded as part of small appliance circuits and are not added in when figuring loads.



Electric ranges can be rated for as little as 3,000 watts or as much as 12,000 watts. They require dedicated 120/240-volt circuits. Find the exact wattage rating by reading the nameplate found inside the oven door or on the back of the unit.




Microwave ovens are regarded as permanent appliances. Add in its wattage rating when calculating loads. The nameplate is found on the back of the cabinet or inside the front door. Most microwave ovens are rated between 500 and 1,200 watts.



Freezers are permanent appliances that may need a dedicated 15- or 20-amp, 120-volt circuits. Freezer ratings are usually between 240 and 480 watts. But combination refrigerator-freezers rated for 1,000 watts or less are plugged into small appliance circuits and do not need their own dedicated circuits. The nameplate for a freezer is found inside the door or on the back of the unit, just below the door seal.



Electric clothes dryers are permanent appliances that need dedicated 30-amp, 120/240-volt circuits. The wattage rating is printed on the nameplate inside the dryer door. Use 5,000 watts as a minimum, regardless of the printed rating. Washing machines and gas-heat clothes dryers with electric tumbler motors do not need dedicated circuits. They plug into the 20-amp small-appliance circuit in the laundry room.

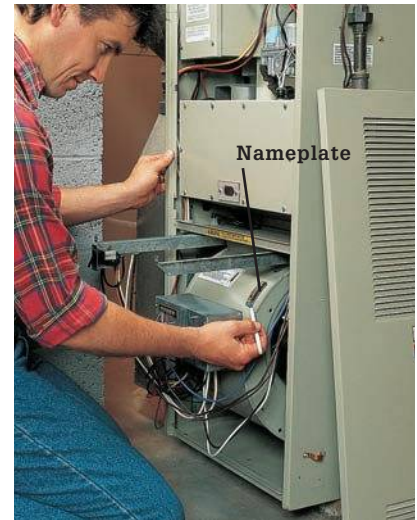

Forced-air furnaces and heat pump air handlers have electric fans and are considered permanent appliances. They require dedicated 15-amp, 120-volt circuits. Include the fan wattage rating, printed on a nameplate inside the control panel, when figuring wattage loads for heating. You should also include the wattage rating for heat pump backup heating coils.



A central air conditioner requires a dedicated 240-volt circuit. Estimate its wattage rating by adding the numbers labeled RLA and FLA on the air conditioner's metal plate. Multiply the $RLA+FLA$ by 240.



Window air conditioners, both 120-volt and 240-volt types, are permanent appliances that require dedicated circuits. The wattage rating, which can range from 500 to 2,000 watts, is found on the nameplate located inside the front grill. Make sure to include all window air conditioners in your evaluation.



Electric room heaters that are permanently installed require a dedicated circuit and must be figured into the load calculations. Use the maximum wattage rating printed inside the cover. In general, 240-volt baseboard-type heaters are rated for 180 to 250 watts for each linear foot.

Draw a Diagram & Obtain a Permit

Drawing a wiring diagram is the last step in planning a circuit installation. A detailed wiring diagram helps you get a work permit, makes it easy to create a list of materials, and serves as a guide for laying out circuits and installing cables and fixtures. Use the circuit maps on pages 30 to 47 as a guide for planning wiring configurations and cable runs. Bring the diagram and materials list when you visit electrical inspectors to apply for a work permit.


Never install new wiring without following your community's permit and inspection procedure. A work permit is not expensive, and it ensures that your work will be reviewed by a qualified inspector. If you install new wiring without the proper permit, an accident or fire traced to faulty wiring could cause your insurance company to discontinue your policy and can hurt the resale value of your home.

When electrical inspectors look over your wiring diagram, they will ask questions to see if you have

a basic understanding of the electrical code and fundamental wiring skills. Some inspectors ask these questions informally, while others give a short written test. Inspectors may allow you to do some, but not all, of the work. For example, they may ask that all final circuit connections at the circuit breaker panel be made by a licensed electrician, while allowing you to do all other work.

A few communities allow you to install wiring only when supervised by an electrician. This means you can still install your own wiring but must hire an electrician to apply for the work permit and to check your work before inspectors review it. The electrician is held responsible for the quality of the job.

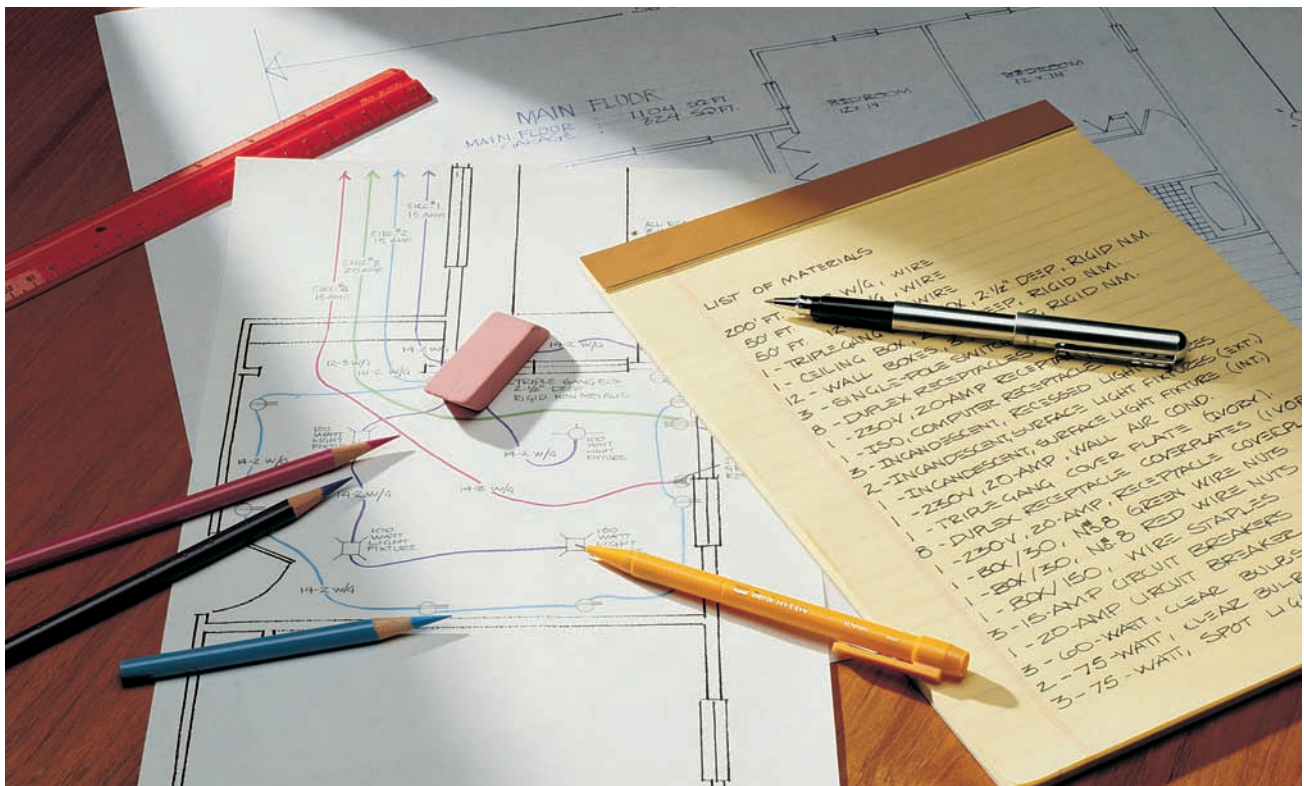Remember that it is the inspectors' responsibility to help you do a safe and professional job. Feel free to call them with questions about wiring techniques or materials.




A detailed wiring diagram and a list of materials is required before electrical inspectors will issue a work permit. If blueprints exist for the space you are remodeling, start your electrical diagram by tracing the wall outlines from the blueprint. Use standard electrical symbols (next page) to clearly show all the receptacles, switches, light fixtures, and permanent appliances. Make a copy of the symbol key and attach it to the wiring diagram for the inspectors' convenience. Show each cable run, and label its wire size and circuit amperage.

How to Draw a Wiring Plan



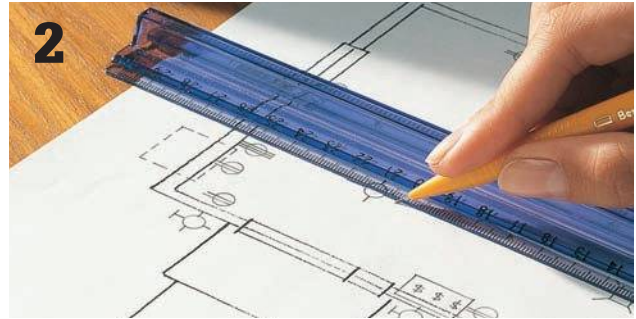
1 Draw a scaled diagram of the space you will be wiring, showing walls, doors, windows, plumbing pipes and fixtures, and heating and cooling ducts. Find the floor space by multiplying room length by width, and indicate this on the diagram.



2 Mark the location of all switches, receptacles, light fixtures, and permanent appliances, using the electrical symbols shown below. Where you locate these devices along the cable run determines how they are wired. Use the circuit maps on pages 30 to 47 as a guide for drawing wiring diagrams.



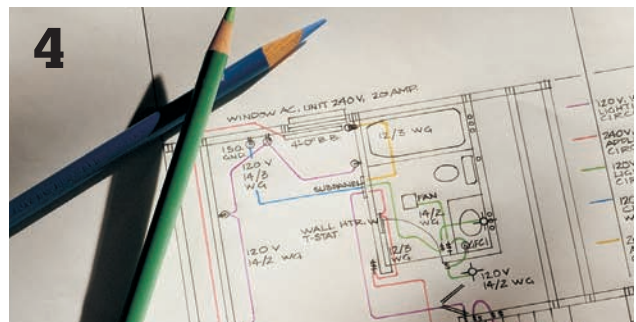3 Draw in cable runs between devices. Indicate cable size and type and the amperage of the circuits. Use a different-colored pencil for each circuit.



4 Identify the wattages for light fixtures and permanent appliances and the type and size of each electrical box. On another sheet of paper, make a detailed list of all materials you will use.

Electrical Symbol Key ▶

(copy this key and attach it to your wiring plan)

| | | | | | | | |
|--|----------------------------|--|-------------------------|--|-------------------------------|--|-------------------------|
| | 240-volt receptacle | | Switched receptacle | | Junction box | | Ceiling fan |
| | Isolated ground receptacle | | Weatherproof receptacle | | Ceiling pull switch | | Electric door opener |
| | Duplex receptacle | | Thermostat | | Surface-mounted light fixture | | Low-voltage transformer |
| | 240-volt dryer receptacle | | Pilot-light switch | | Recessed light fixture | | Television jack |
| | Singleplex receptacle | | Single-pole switch | | Fluorescent light fixture | | Telephone outlet |
| | Fourplex receptacle | | Timer switch | | Wall-mounted light fixture | | Smoke detector |
| | GFCI duplex receptacle | | Three-way switch | | Weatherproof light fixture | | Vent fan |

Wiring a Room Addition

The photo below shows the circuits you would likely want to install in a large room addition. This example shows the framing and wiring of an unfinished attic converted to an office or entertainment room with a bathroom. This room includes a subpanel and five new circuits plus telephone and cable-TV lines.


A wiring project of this sort is a potentially complicated undertaking that can be made simpler by breaking the project into convenient steps, and finishing one step before moving on to the next. Turn to pages 24 to 25 to see this project represented as a wiring diagram.

Individual Circuits

■ **#1: Bathroom circuit.** This 20-amp dedicated circuit supplies power to bathroom lights and fans, as well as receptacles that must be GFCI-protected at the box or at the receptacle. As with small appliance circuits in the kitchen, you may not tap into this circuit to feed any additional loads.

■ **#2: Computer circuit.** A 15-amp dedicated circuit with isolated ground is recommended, but an individual branch circuit is all that is required by most codes.

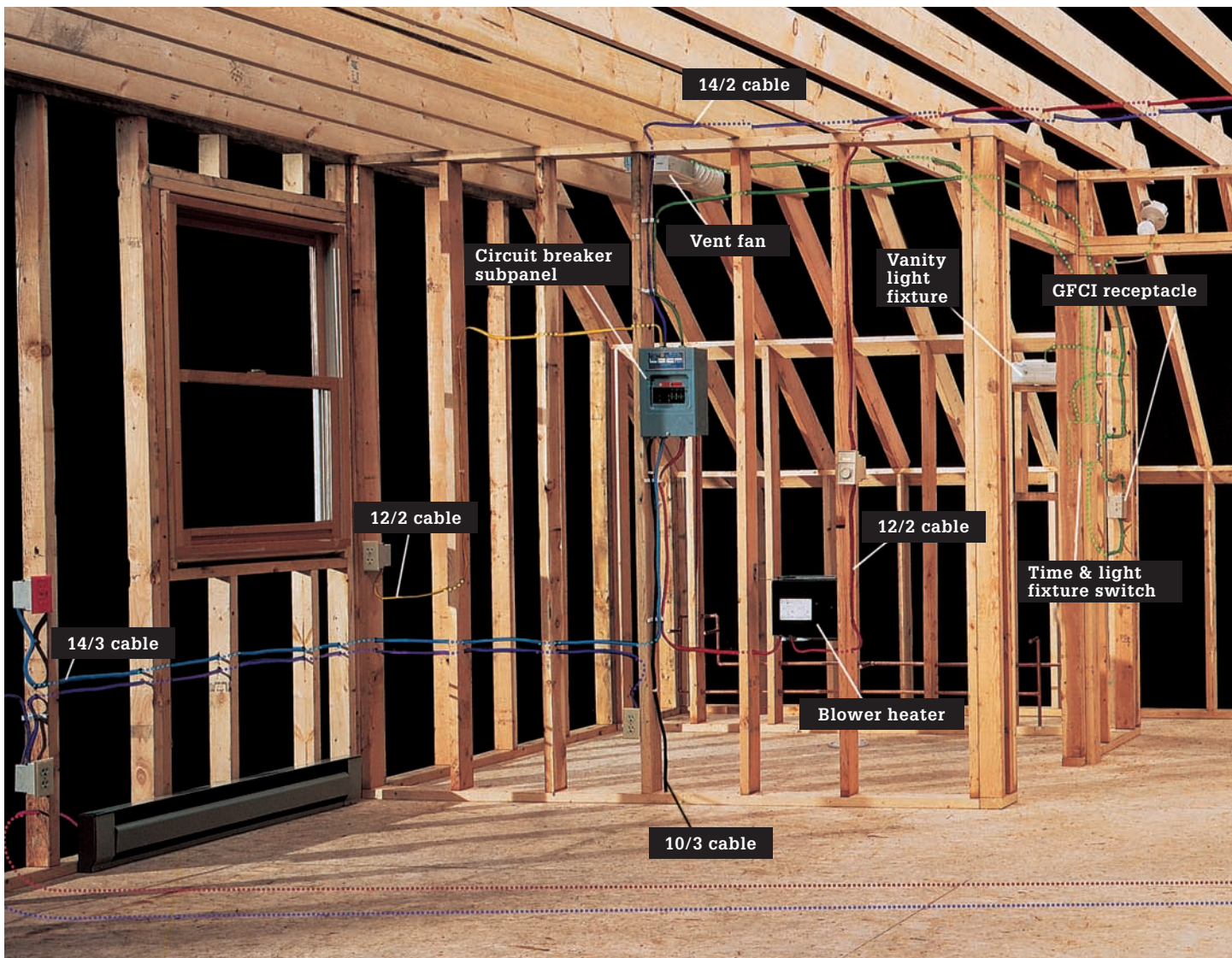Circuit breaker subpanel receives power through a 10-gauge, three-wire feeder cable connected to a 30-amp,



240-volt circuit breaker at the main circuit breaker panel. Larger room additions may require a 60- or 100-amp feeder circuit breaker.

#3: Air-conditioner circuit. This is a 20-amp, 240-volt dedicated circuit. In cooler climates, or in a smaller room, you may need an air conditioner and circuit rated for only 120 volts.

#4: Basic lighting/receptacle circuit. This 15-amp, 120-volt circuit supplies power to most of the fixtures in the bedroom and study areas.

#5: Heater circuit. This 20-amp, 240-volt circuit supplies power to the bathroom blower-heater and to the baseboard

heaters. Depending on the size of your room and the wattage rating of the baseboard heaters, you may need a 30-amp, 240-volt heating circuit.

Telephone outlet is wired with 22-gauge four-wire phone cable. If your home phone system has two or more separate lines, you may need to run a cable with eight wires, commonly called four-pair cable.

Cable television jack is wired with coaxial cable running from an existing television junction in the utility area.




Diagram View

The diagram below shows the layout of the five circuits and the locations of their receptacles, switches, fixtures, and devices as shown in the photo on the previous pages. The circuits and receptacles are based on the needs of a 400-sq.-ft. space. An inspector will want to see a diagram like this one before issuing a permit. After you've received approval for your addition, the wiring diagram will serve as your guide as you complete your project.

■ **Circuit #1:** A 20-amp, 120-volt circuit serving the bathroom and closet area. Includes: 12/2 NM cable, double-gang box, timer switch, single-pole switch, 4" x 4" box with single-gang adapter plate, two plastic light fixture boxes, vanity light fixture, closet light fixture, 15-amp single-pole circuit breaker.

■ **Circuit #2:** A 15-amp, 120-volt computer circuit. Includes: 14/2 NM cable, single-gang box, 15-amp receptacle, 15-amp single-pole circuit breaker.

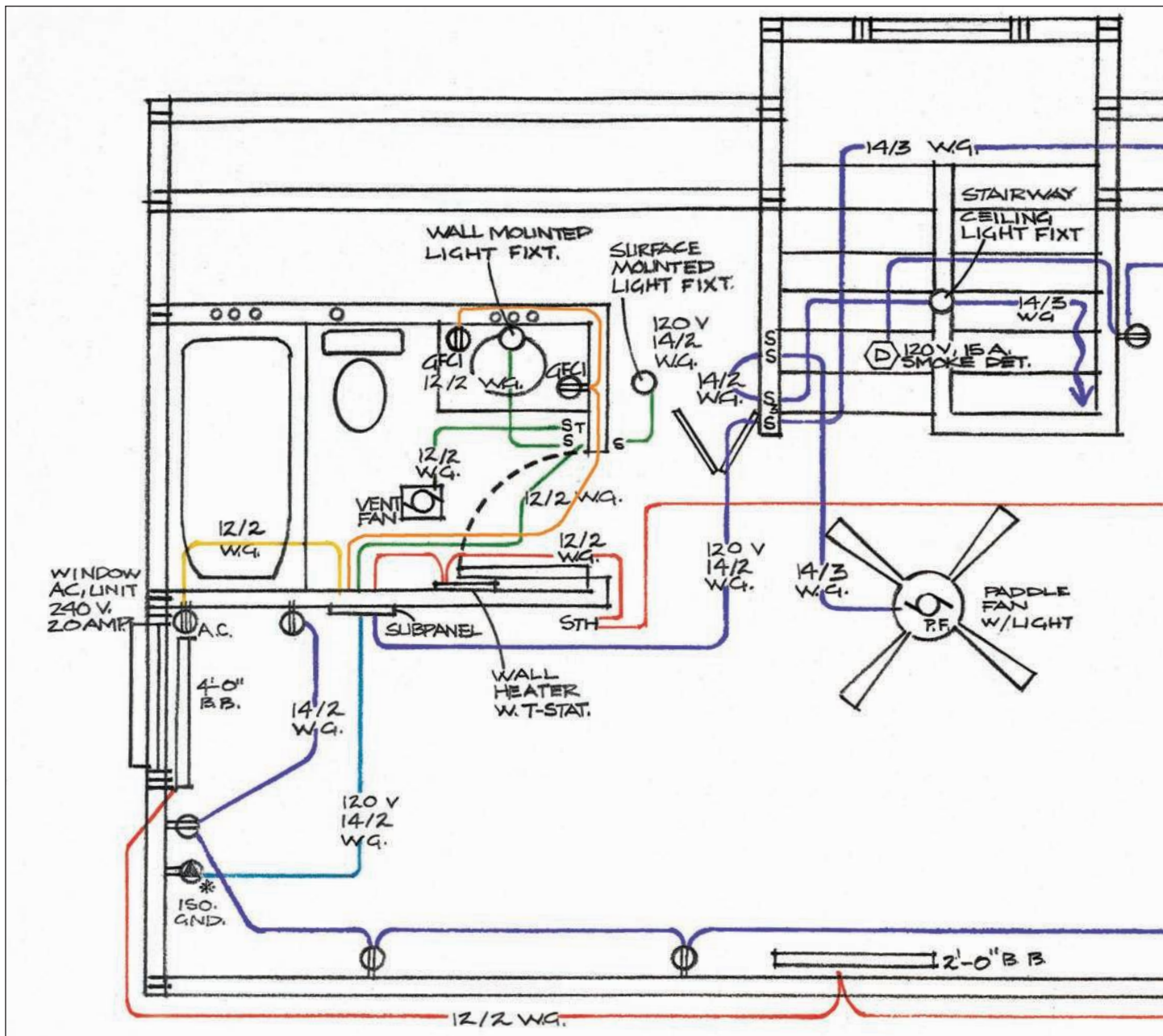■ **Circuit #3:** A 20-amp, 240-volt air-conditioner circuit. Includes: 12/2 NM cable; single-gang box;




20-amp, 240-volt receptacle (singleplex style); 20-amp double-pole circuit.

■ **Circuit #4:** A 15-amp, 120-volt basic lighting/receptacle circuit serving most of the fixtures in the bedroom and study areas. Includes: 14/2 and 14/3 NM cable, two double-gang boxes, fan speed-control switch, dimmer switch, single-pole switch, two three-way switches, two plastic light fixture boxes, light fixture for stairway, smoke detector, metal light fixture box with brace bar, ceiling fan with light fixture, 10 single-gang boxes, 4" x 4" box with single-gang adapter plate, 10 duplex receptacles (15-amp), 15-amp single-pole circuit breaker.

■ **Circuit #5:** A 20-amp, 240-volt circuit that supplies power to three baseboard heaters controlled by a wall thermostat and to a bathroom blower-heater controlled by a built-in thermostat. Includes: 12/2 NM cable, 750-watt blower heater, single-gang box, line-voltage thermostat, three baseboard heaters, 20-amp double-pole circuit breaker.


TV **Cable television jack:** Coaxial cable with F-connectors, signal splitter, cable television outlet with mounting brackets.

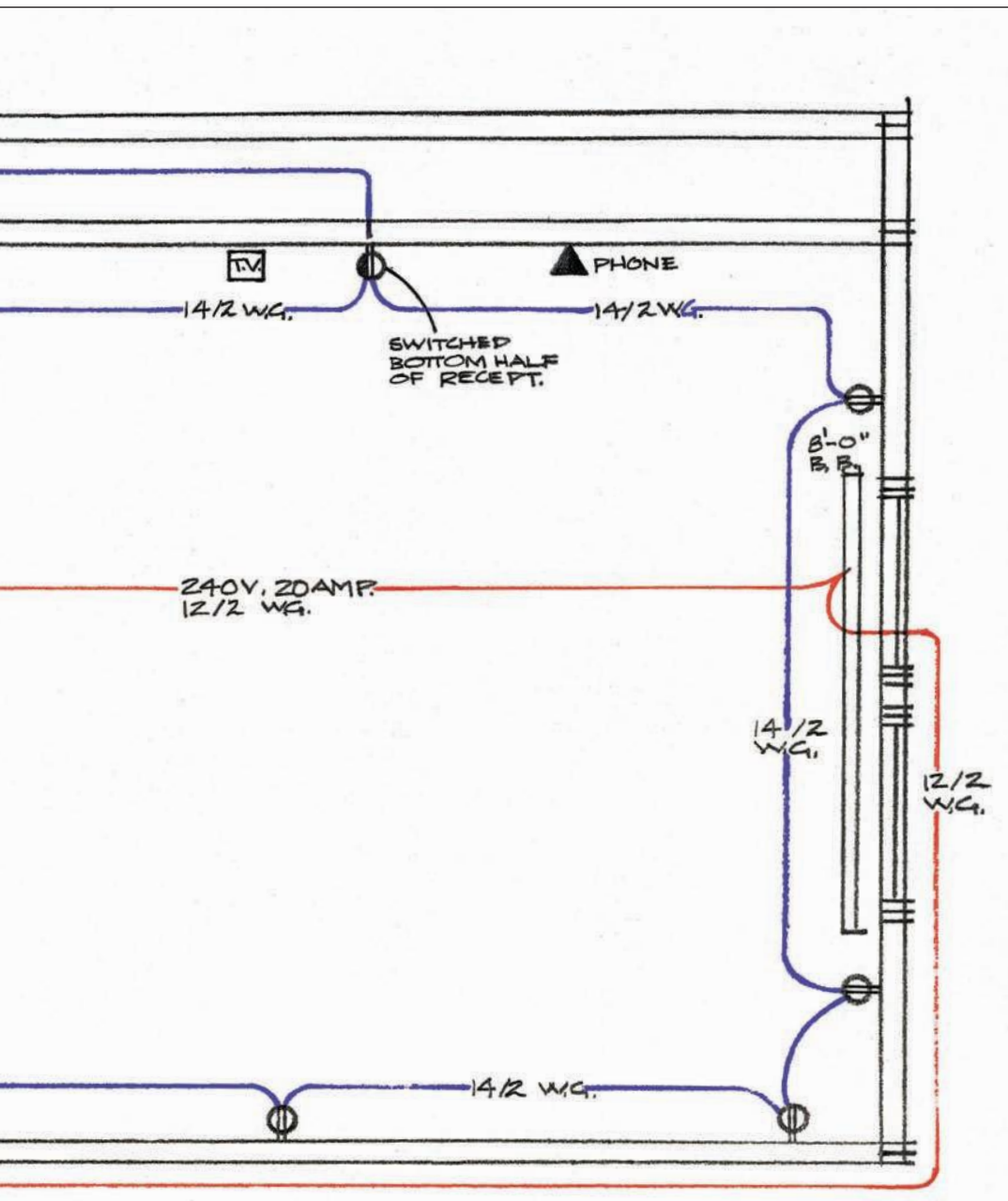■ **Circuit #6:** A 20-amp, 120-volt, GFCI-protected bathroom receptacle circuit for the bathroom. Includes GFCI breaker, 12/2 NM cable, boxes, and 20-amp receptacles.



Wiring a Kitchen



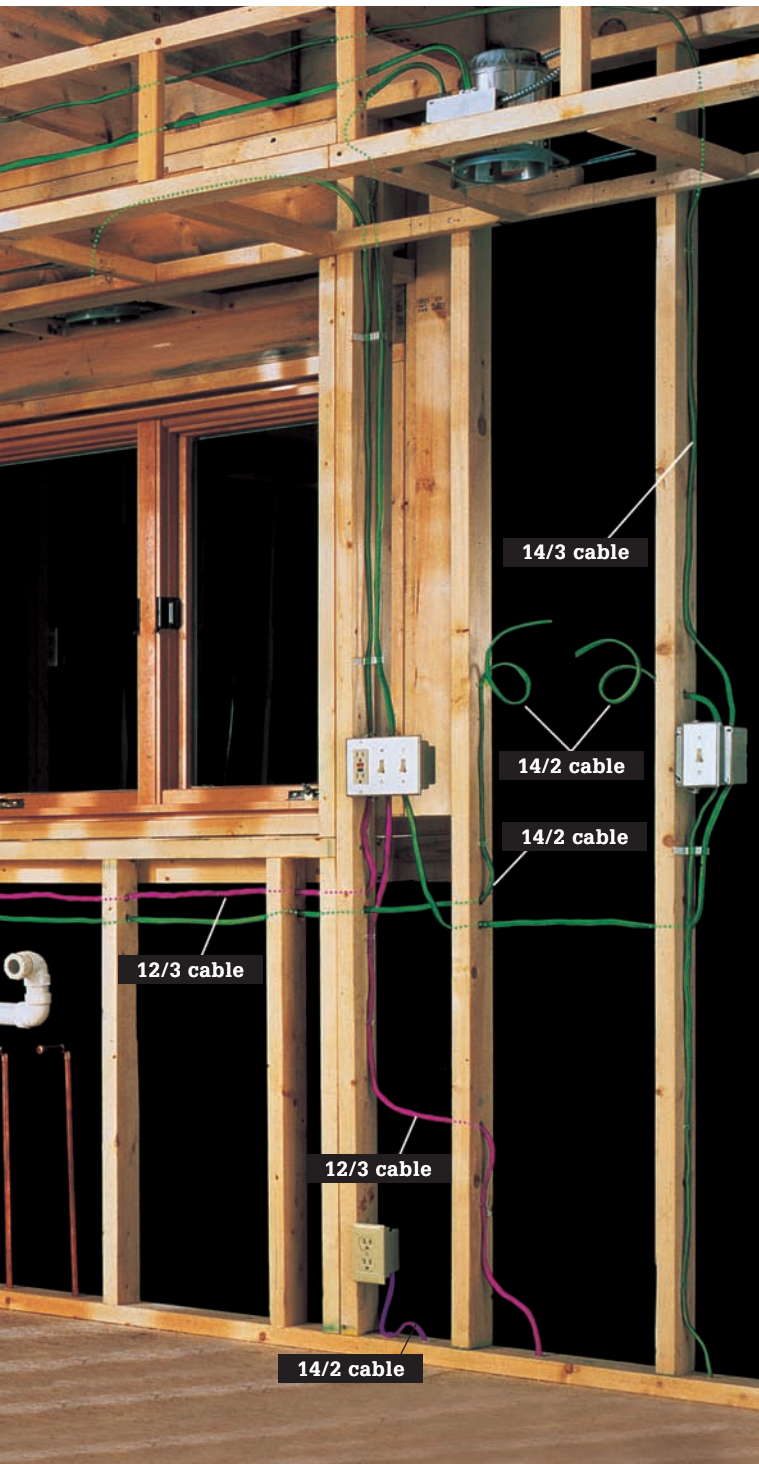

The photo at left shows the circuits you would probably want to install in a total kitchen remodel. Kitchens require a wide range of electrical services, from simple 15-amp lighting circuits to 120/240, 50-amp appliance circuits. This kitchen example has seven circuits, including separate dedicated circuits for a dishwasher and food disposer. Some codes allow the disposer and dishwasher to share a single circuit.

All rough carpentry and plumbing should be in place before beginning any electrical work. As always, divide a project of this scale into manageable steps, and finish one step before moving on. Turn to pages 28 to 29 to see this project represented as a wiring diagram.

Individual Circuits

#1 & #2: Small-appliance circuits. Two 20-amp, 120-volt circuits supply power to countertop and eating areas for small appliances. All general-use receptacles must be on these circuits. One 12/3 cable fed by a 20-amp double-pole breaker wires both circuits. These circuits share one electrical box with the disposer circuit (#5) and another with the basic lighting circuit (#7). Other circuits may also service the area, as with a dedicated refrigerator circuit.


#3: Range circuit. A 40- or 50-amp, 120/240-volt dedicated circuit supplies power to the range/ oven appliance. It is wired with 6/3 copper cable.


#4: Microwave circuit. It is wired with 12/2 cable. Microwaves that use less than 300 watts can be installed on a 15-amp circuit or plugged into the small-appliance circuits.

#5: Food disposer/dishwasher circuit. A dedicated 15-amp, 120-volt circuit supplies power to the disposer. It is wired with 14/2 cable. Some local codes may allow the disposer to be on the same circuit as the dishwasher if it is a 20-amp circuit.

#6: Basic lighting circuit. A 15-amp, 120-volt circuit powers the ceiling fixture, recessed fixtures, and undercabinet task lights. 14/2 and 14/3 cables connect the fixtures and switches in the circuit. Each task light has a self-contained switch.

Diagram View

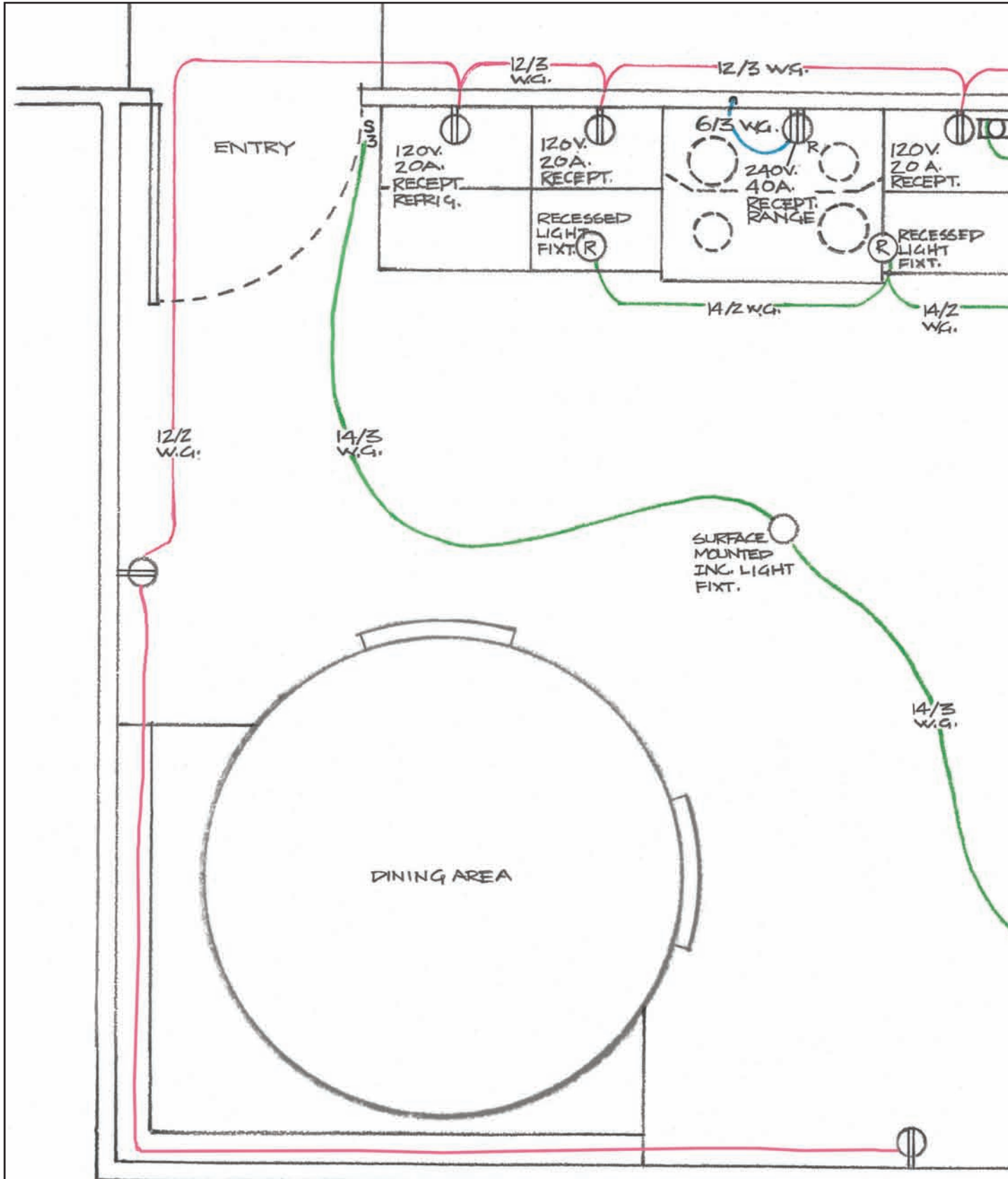

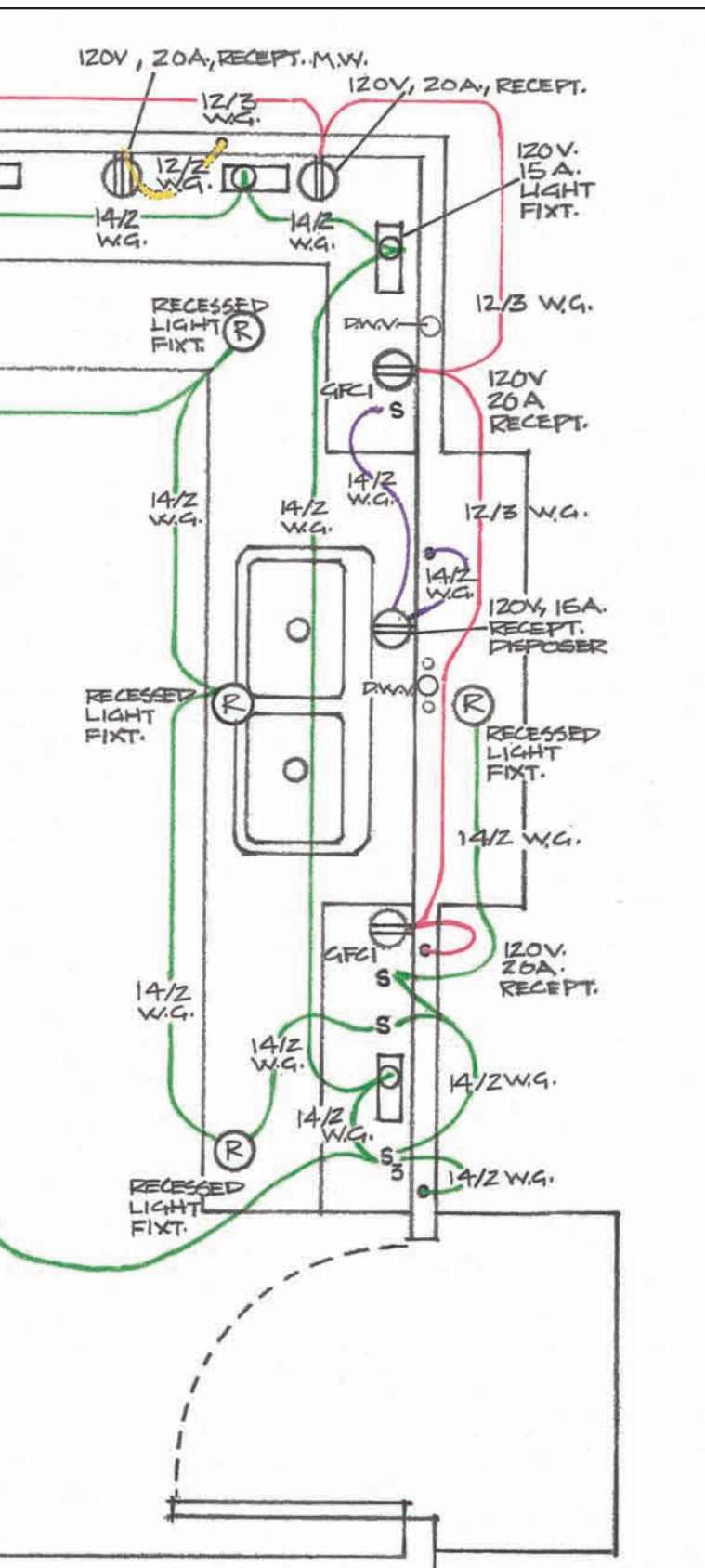

The diagram at left shows the layout of the seven circuits and the locations of their receptacles, switches, fixtures, and devices as shown in the photo on the previous pages. The circuits and receptacles are based on the needs of a 175-sq.-ft. space kitchen. An inspector will want to see a diagram like this one before issuing a permit. After you've received approval for your addition, the wiring diagram will serve as your guide as you complete your project.

■ **Circuits #1 & #2:** Two 20-amp, 120-volt small-appliance circuits wired with one cable. All general-use receptacles must be on these circuits, and they must be GFCI units. Includes: two GFCI receptacles rated for 20 amps, five electrical boxes that are 4" x 4", and 12/3 cable.

■ **Circuit #3:** A 50-amp, 120/240-volt dedicated circuit for the range. Includes: a 4" x 4" box; a 120/240-volt, 50-amp range receptacle; and 6/3 NM copper cable.

■ **Circuit #4:** A 20-amp, 120-volt dedicated circuit for the microwave. Includes: a 20-amp duplex receptacle, a single-gang box, and 12/2 NM cable.

■ **Circuit #5:** A 15-amp, 120-volt dedicated circuit for the food disposer. Includes: a 15-amp duplex receptacle, a single-pole switch (installed in a double-gang box with a GFCI receptacle from the small-appliance circuits), one single-gang box, and 14/2 cable.

■ **Circuit #6:** A 15-amp, 120-volt basic lighting circuit serving all of the lighting needs in the kitchen. Includes: two single-pole switches, two three-way switches, single-gang box, 4" x 4" box, triple-gang box (shared with one of the GFCI receptacles from the small-appliance circuits), plastic light fixture box with brace, ceiling light fixture, four fluorescent undercabinet light fixtures, six recessed light fixtures, 14/2 and 14/3 cables.


To light


To fan

TWO-WIRE CABLE

THREE-WIRE CABLE
(NEUTRAL NOT USED)

TWO-WIRE CABLE

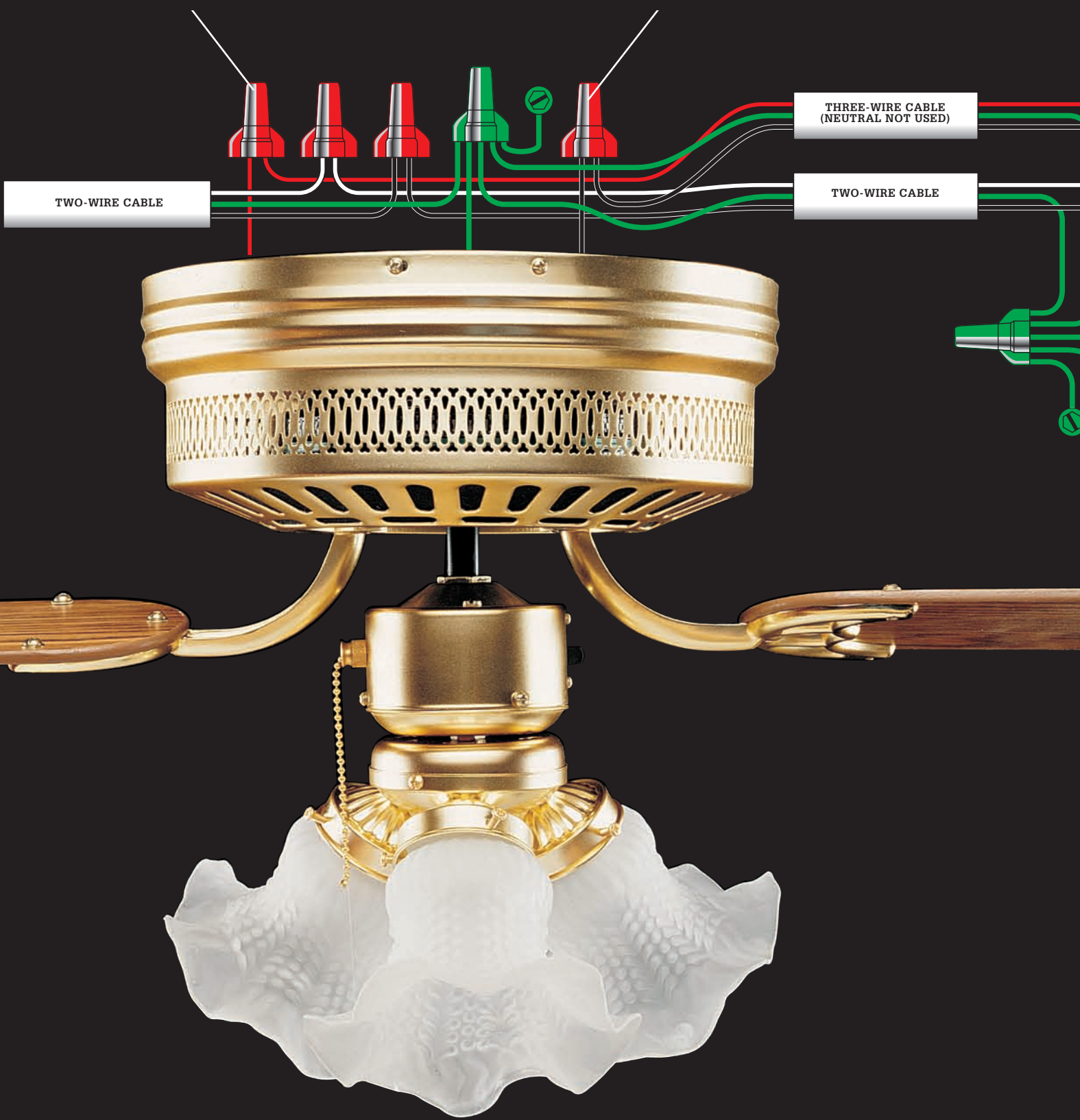

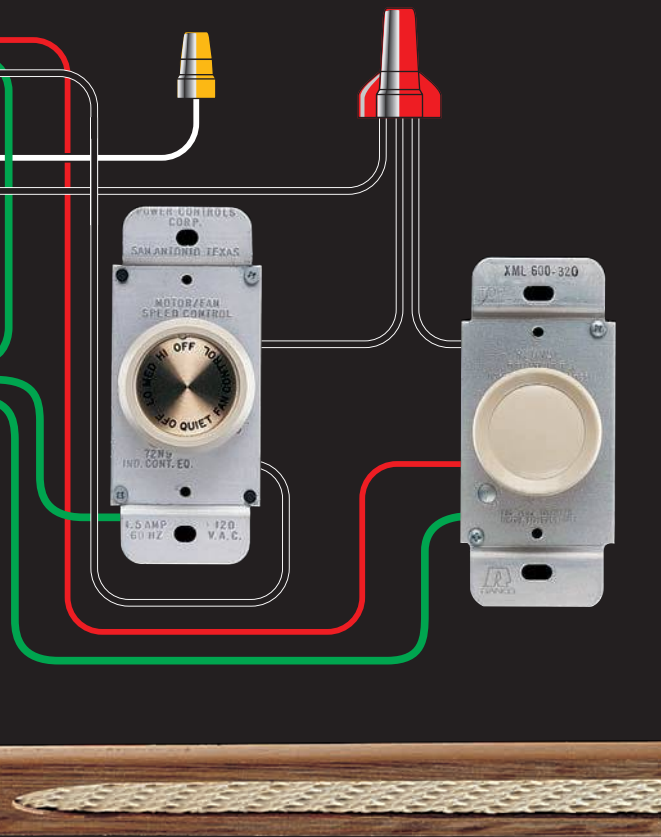

Circuit Maps

The circuit maps on the following pages show the most common wiring variations for typical electrical devices. Most new wiring you install will match one or more of the maps shown. Find the maps that match your situation and use them to plan your circuit layouts.

The 120-volt circuits shown on the following pages are wired for 15 amps using 14-gauge wire and receptacles rated at 15 amps. If you are installing a 20-amp circuit, substitute 12-gauge cables and use receptacles rated for 15 or 20 amps.

In configurations where a white wire serves as a hot wire instead of a neutral, both ends of the wire are coded with black tape to identify it as hot. In addition, each of the circuit maps shows a box grounding screw. This grounding screw is required in all metal boxes, but plastic electrical boxes do not need to be grounded.

You should remember two new code requirements when wiring switches. (1) Provide a neutral wire at every switch box. This may require using 3-wire cable or two 2-wire cables where you may have used one 2-wire cable in the past. (2) Use a black or red wire to supply power from a switch to a light or switched receptacle.

Note: For clarity, all grounding conductors in the circuit maps are colored green. In practice, the grounding wires inside sheathed cables usually are bare copper.



In this chapter:

- Common Household Circuits

Common Household Circuits

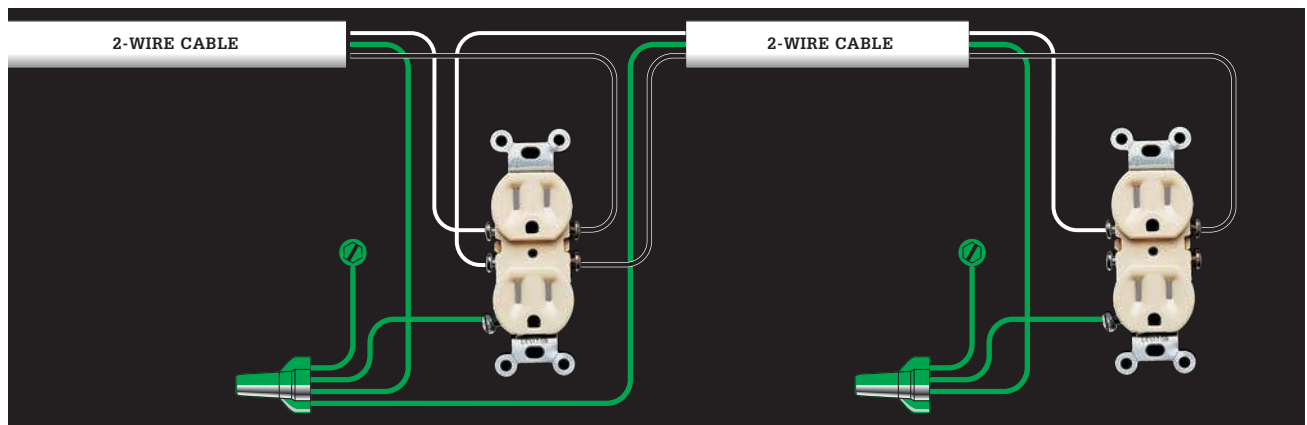
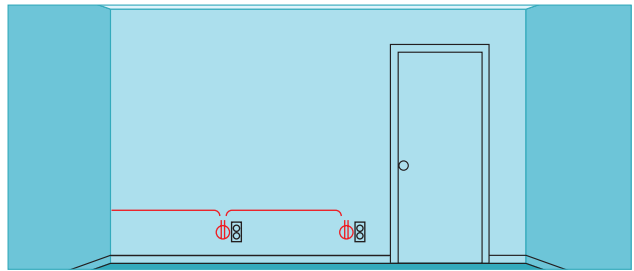
1. 120-VOLT DUPLEX RECEPTACLES WIRED IN SEQUENCE

Use this layout to link any number of duplex receptacles in a basic lighting/receptacle circuit. The last receptacle in the cable run is connected like the receptacle shown at the right side of the circuit map below. All other receptacles are wired like the receptacle shown on the left side. This configuration or layout requires two-wire cables.



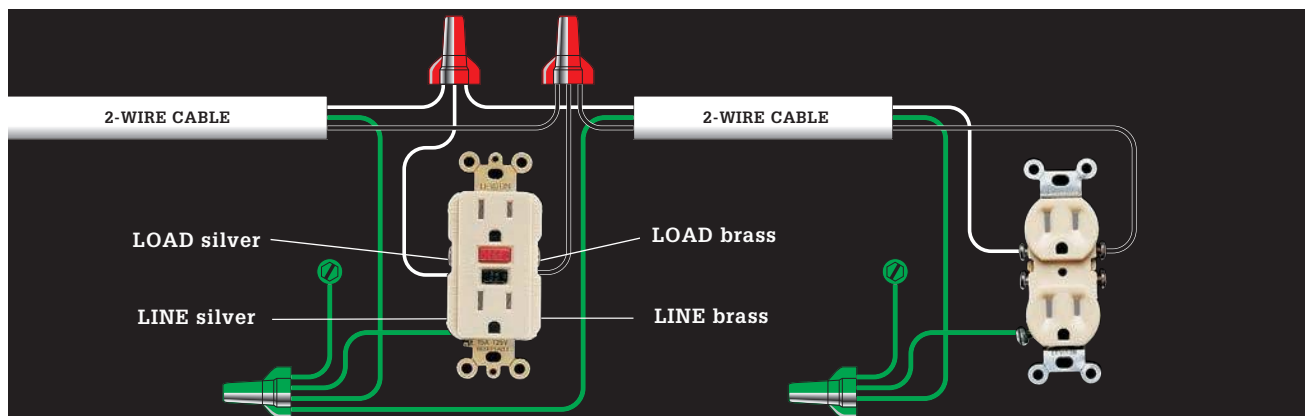
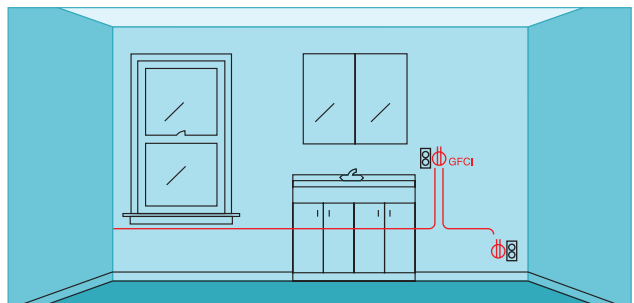
2. GFCI RECEPTACLES (SINGLE-LOCATION PROTECTION)

Use this layout when receptacles are within 6 ft. of a water source, such as those in kitchens and bathrooms. To prevent nuisance tripping caused by normal power surges, GFCIs should be connected only at the line screw terminal so they protect a single location, not the fixtures on the load side of the circuit. Requires two-wire cables. Where a GFCI must protect other fixtures, use circuit map 3. Remember that bathroom receptacles should usually be on a dedicated 20-amp circuit and that all bathroom receptacles must be GFCI-protected.



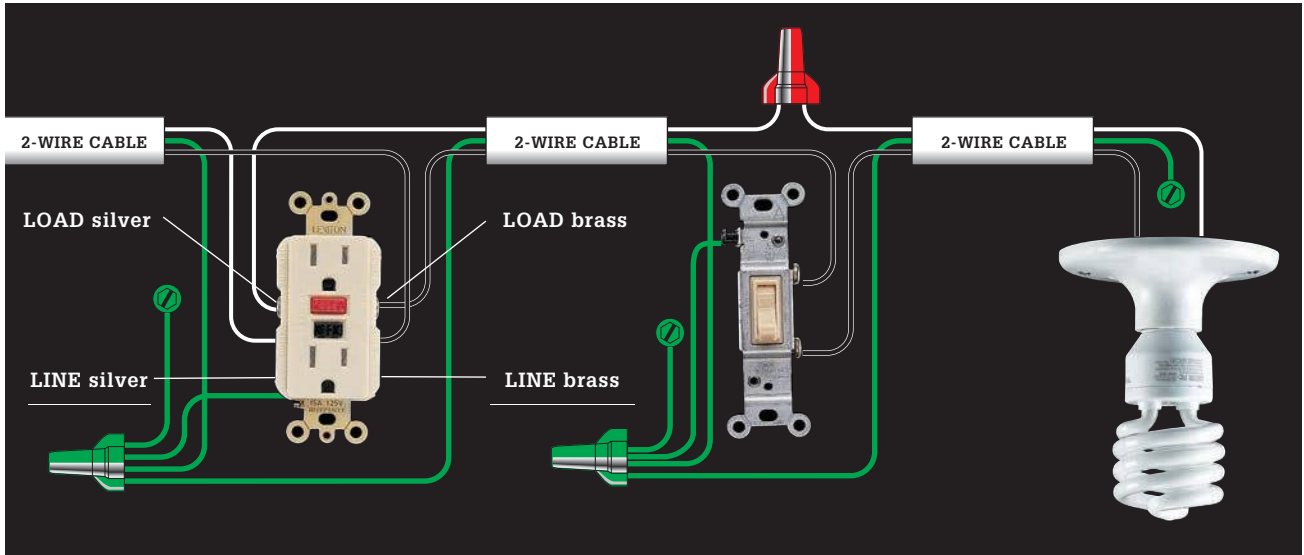
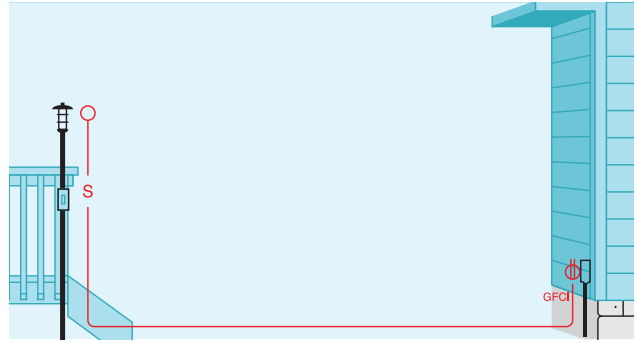
3. GFCI RECEPTACLE, SWITCH & LIGHT FIXTURE (WIRED FOR MULTIPLE-LOCATION PROTECTION)

In some locations, such as an outdoor circuit, it is a good idea to connect a GFCI receptacle so it also provides shock protection to the wires and fixtures that continue to the end of the circuit. Wires from the power source are connected to the line screw terminals; outgoing wires are connected to load screws. Requires two-wire cables.



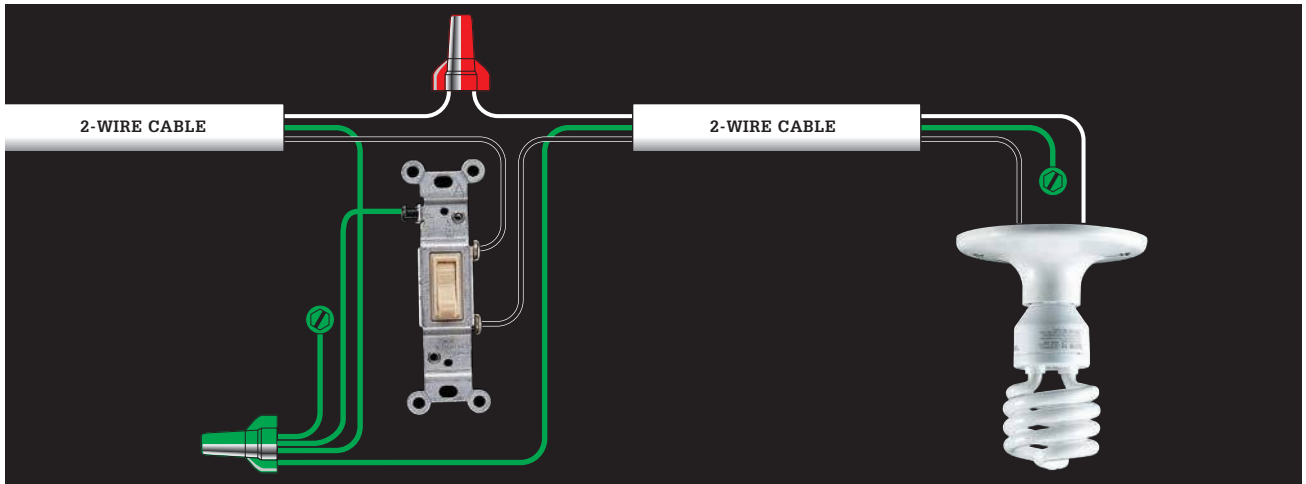
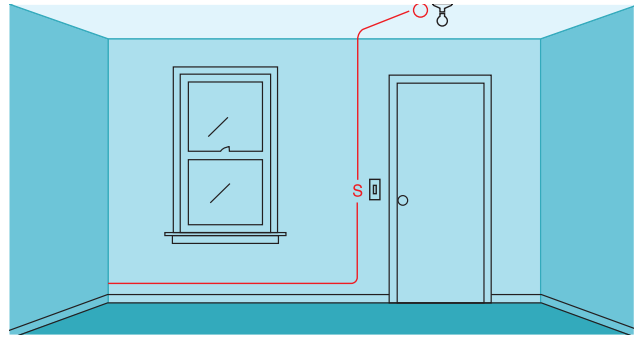
4. SINGLE-POLE SWITCH & LIGHT FIXTURE (LIGHT FIXTURE AT END OF CABLE RUN)

Use this layout for light fixtures in basic lighting/receptacle circuits throughout the home. It is often used as an extension to a series of receptacles (circuit map 1). Requires two-wire cables.



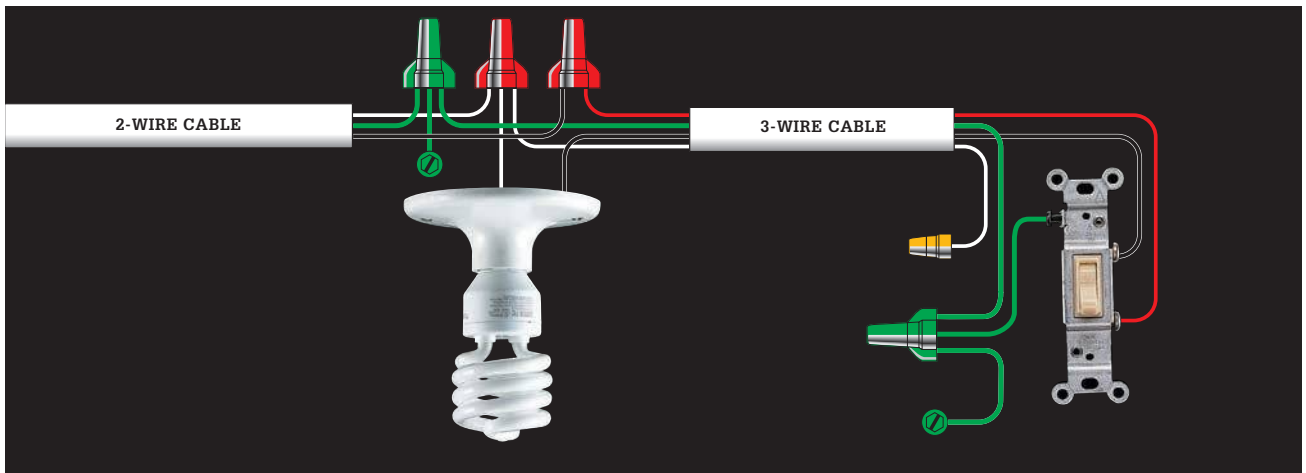
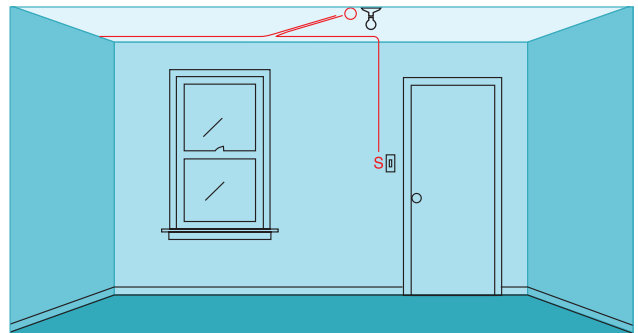
5. SINGLE-POLE SWITCH & LIGHT FIXTURE (SWITCH AT END OF CABLE RUN)

Use this layout, sometimes called a switch loop, where it is more practical to locate a switch at the end of the cable run. In the last length 3-wire cable is used to make a hot conductor available in each direction. Requires two-wire and three-wire cables.



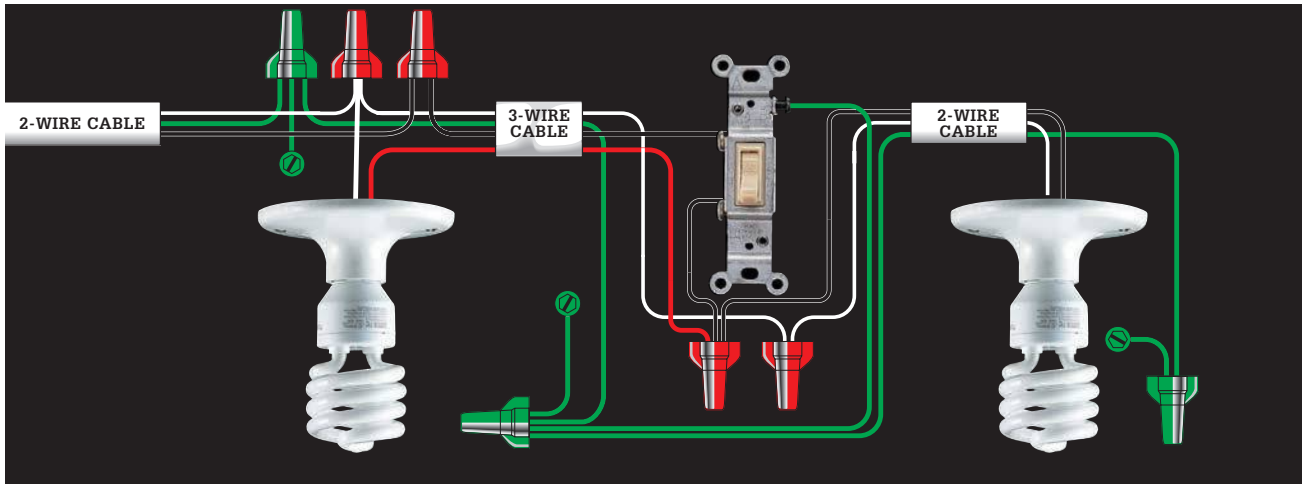
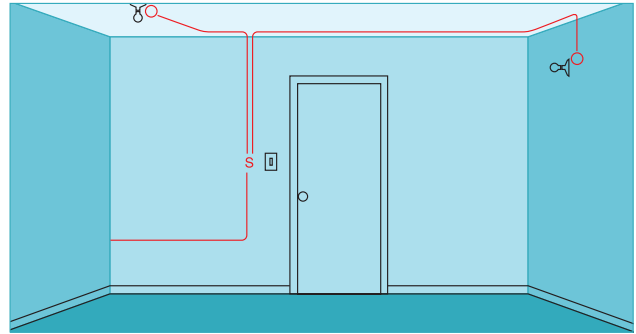
6. SINGLE-POLE SWITCH & TWO LIGHT FIXTURES (SWITCH BETWEEN LIGHT FIXTURES, LIGHT AT START OF CABLE RUN)

Use this layout when you need to control two fixtures from one single-pole switch and the switch is between the two lights in the cable run. Power feeds to one of the lights. Requires two-wire and three-wire cables.



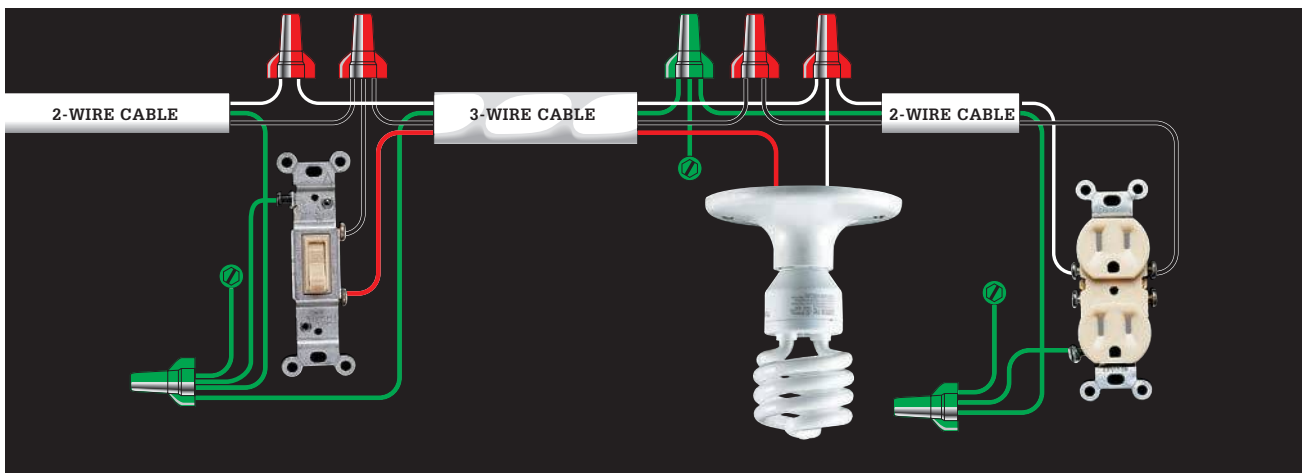
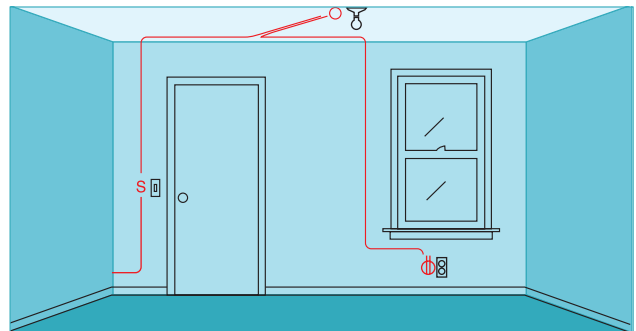
7. SINGLE-POLE SWITCH & LIGHT FIXTURE, DUPLEX RECEPTACLE (SWITCH AT START OF CABLE RUN)

Use this layout to continue a circuit past a switched light fixture to one or more duplex receptacles. To add multiple receptacles to the circuit, see circuit map 1. Requires two-wire and three-wire cables.



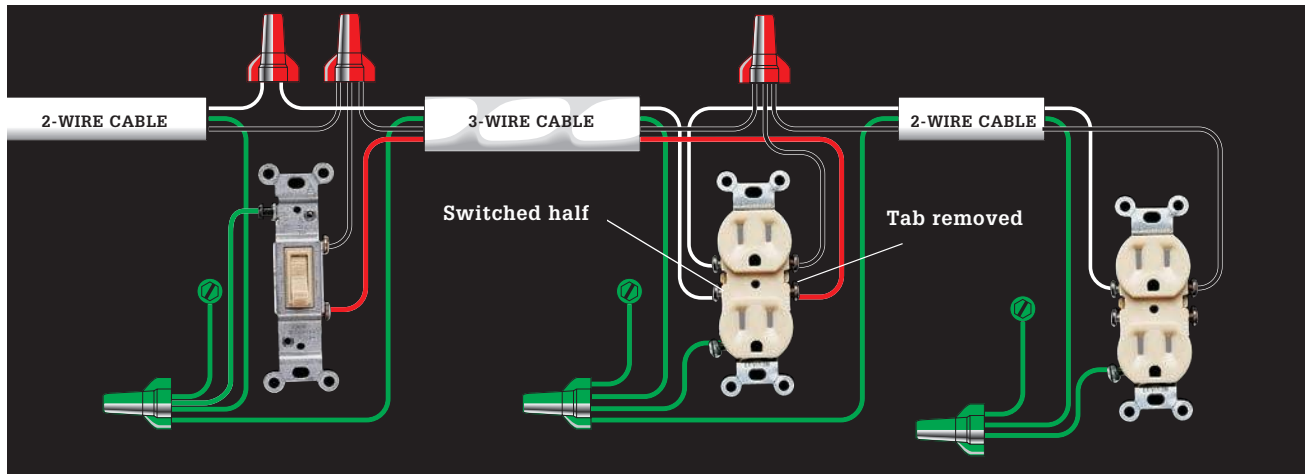
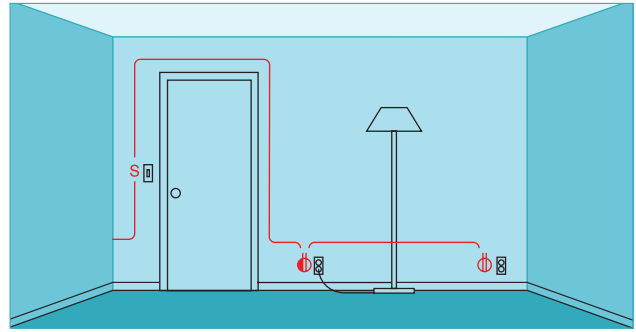
8. SWITCH-CONTROLLED SPLIT DUPLEX RECEPTACLE, DUPLEX RECEPTACLE (SWITCH AT START OF CABLE RUN)

This layout lets you use a wall switch to control a lamp plugged into a wall receptacle. This configuration is required by code for any room that does not have a switch-controlled wall or ceiling fixture. Only the bottom half of the first receptacle is controlled by the wall switch; the top half of the receptacle and all additional receptacles on the circuit are always hot. Requires two-wire and three-wire cables. Some electricians help people identify switched receptacles by installing them upside down.



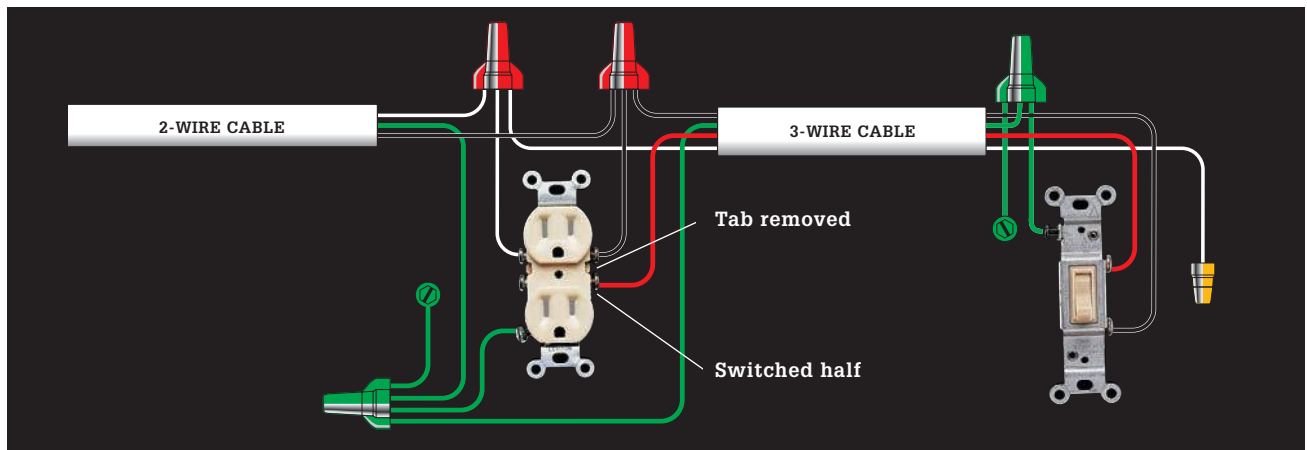
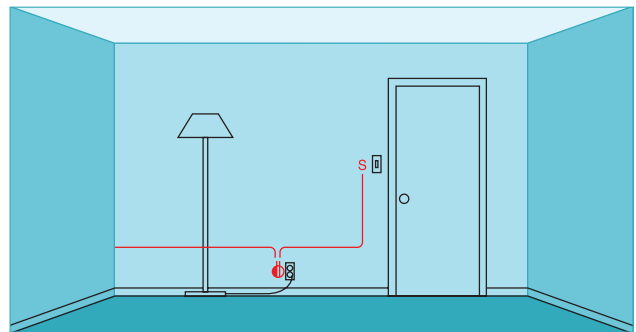
9. SWITCH-CONTROLLED SPLIT RECEPTACLE (SWITCH AT END OF CABLE RUN)

Use this switch loop layout to control a split receptacle (see circuit map 7) from an end-of-run circuit location. The bottom half of the receptacle is controlled by the wall switch, while the top half is always hot. Requires two-wire and three-wire cable. Some electricians help people identify switched receptacles by installing them upside down.



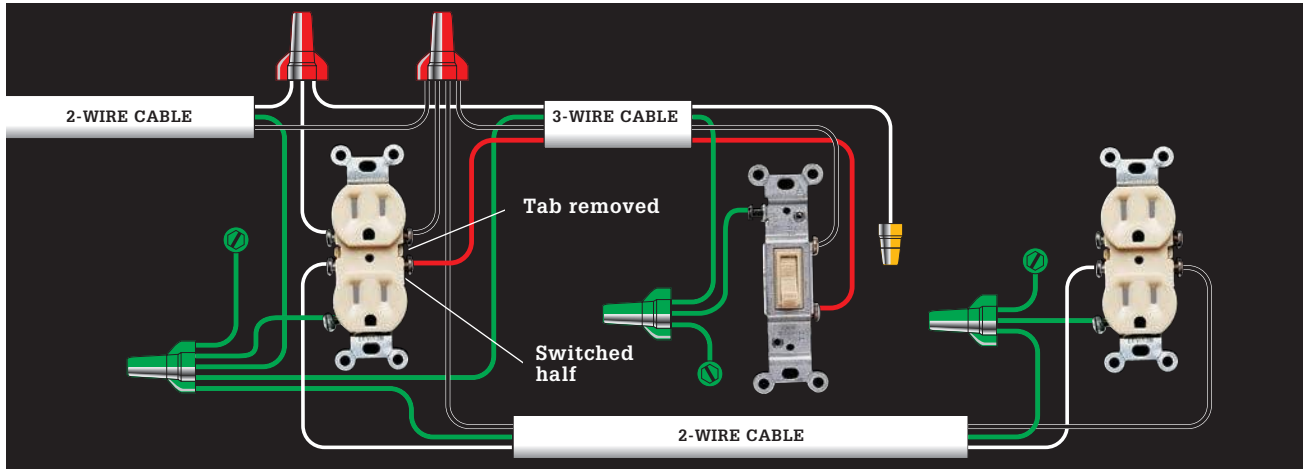
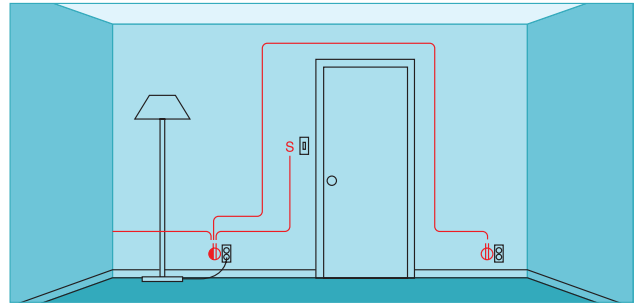
10. SWITCH-CONTROLLED SPLIT RECEPTACLE, DUPLEX RECEPTACLE (SPLIT RECEPTACLE AT START OF RUN)

Use this variation of circuit map 7 where it is more practical to locate a switch-controlled receptacle at the start of a cable run. Only the bottom half of the first receptacle is controlled by the wall switch; the top half of the receptacle, and all other receptacles on the circuit, are always hot. Requires two-wire and three-wire cables. Some electricians help people identify switched receptacles by installing them upside down.



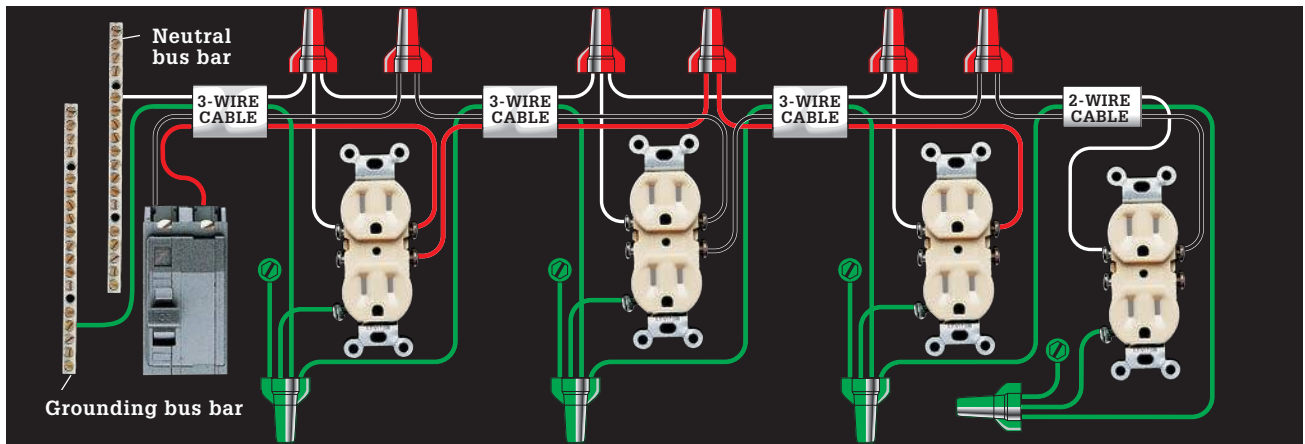
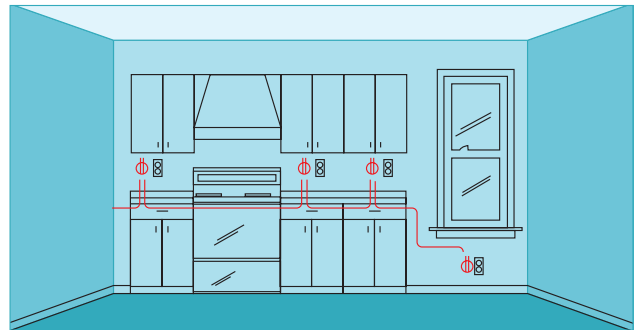
11. DOUBLE RECEPTACLE CIRCUIT WITH SHARED NEUTRAL WIRE (RECEPTACLES ALTERNATE CIRCUITS)

This layout features two 120-volt circuits wired with one three-wire cable connected to a double-pole circuit breaker. The black hot wire powers one circuit; the red wire powers the other. The white wire is a shared neutral that serves both circuits. When wired with 12/2 and 12/3 cable and receptacles rated for 20 amps, this layout can be used for the two small-appliance circuits required in a kitchen. Remember to use a GFCI circuit breaker if you use this circuit for kitchen counter top receptacles.



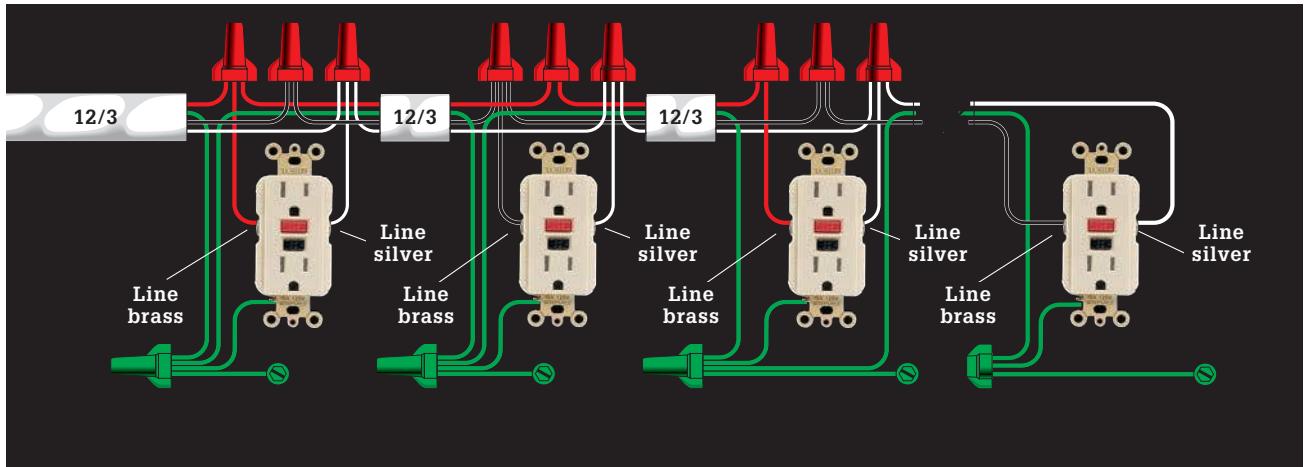
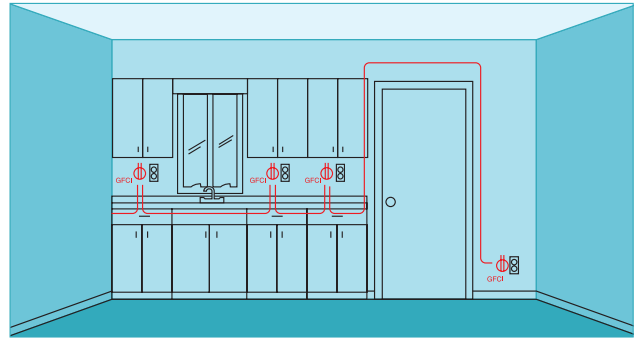
12. DOUBLE RECEPTACLE SMALL-APPLIANCE CIRCUIT WITH GFCIs & SHARED NEUTRAL WIRE

Use this layout variation of circuit map 10 to wire a double receptacle circuit when code requires that some of the receptacles be GFCIs. The GFCIs should be wired for single-location protection (see circuit map 2). Requires three-wire and two-wire cables.



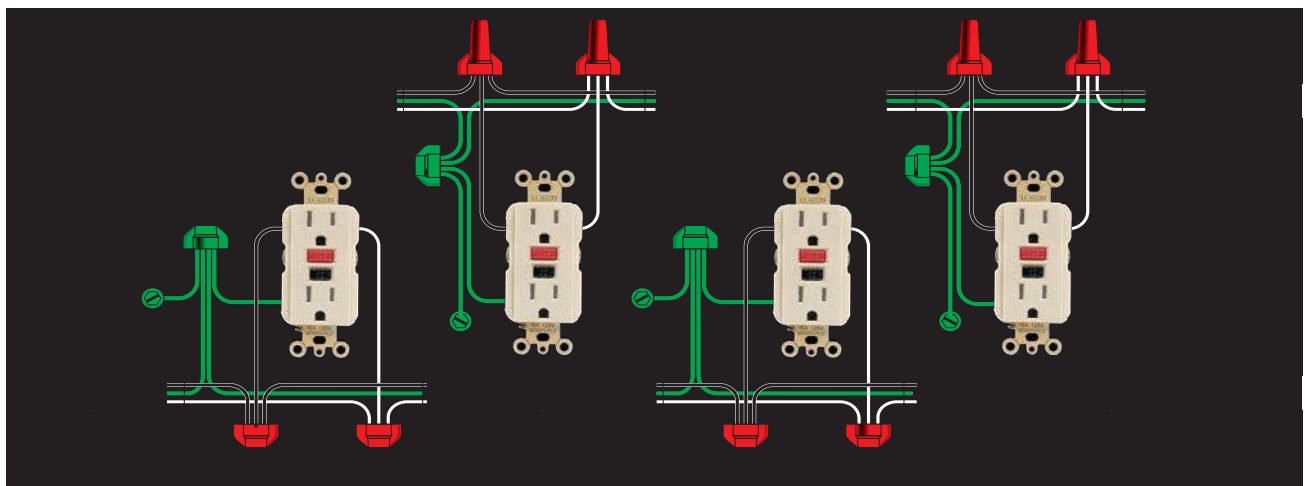
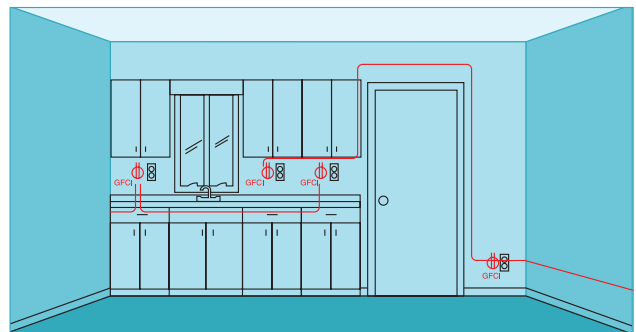
13. DOUBLE RECEPTACLE SMALL-APPLIANCE CIRCUIT WITH GFCIs & SEPARATE NEUTRAL WIRES

If the room layout or local codes do not allow for a shared neutral wire, use this layout instead. The GFCIs should be wired for single-location protection (see circuit map 2). Requires two-wire cable.



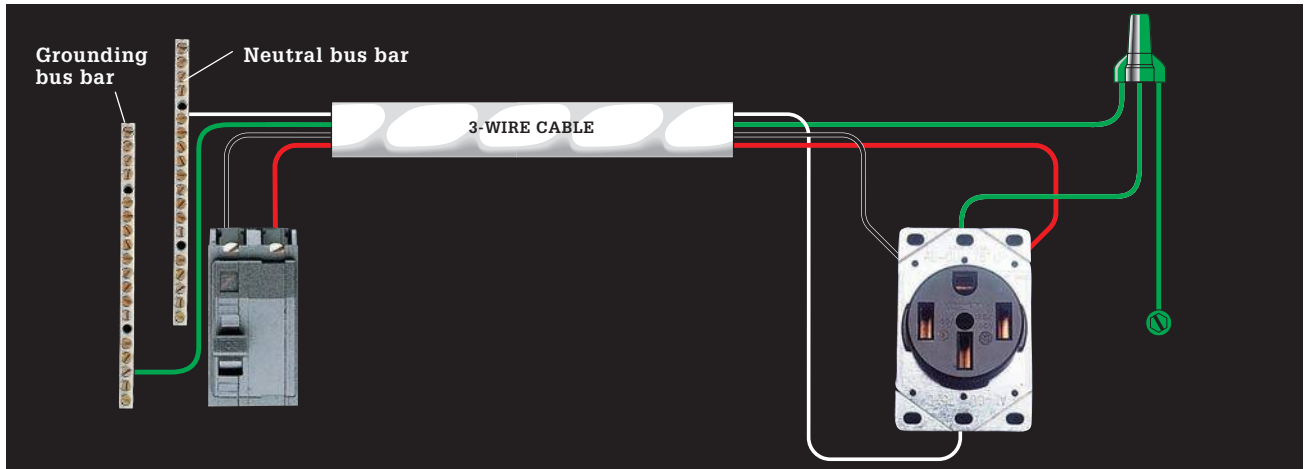
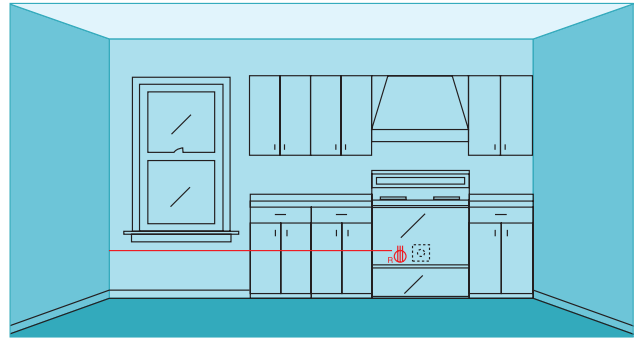
14. 120/240-VOLT RANGE RECEPTACLE

This layout is for a 40- or 50-amp, 120/240-volt dedicated appliance circuit wired with 8/3 or 6/3 cable, as required by code for a large kitchen range. The black and red circuit wires, connected to a double-pole circuit breaker in the circuit breaker panel, each bring 120 volts of power to the setscrew terminals on the receptacle. The white circuit wire attached to the neutral bus bar in the circuit breaker panel is connected to the neutral setscrew terminal on the receptacle.



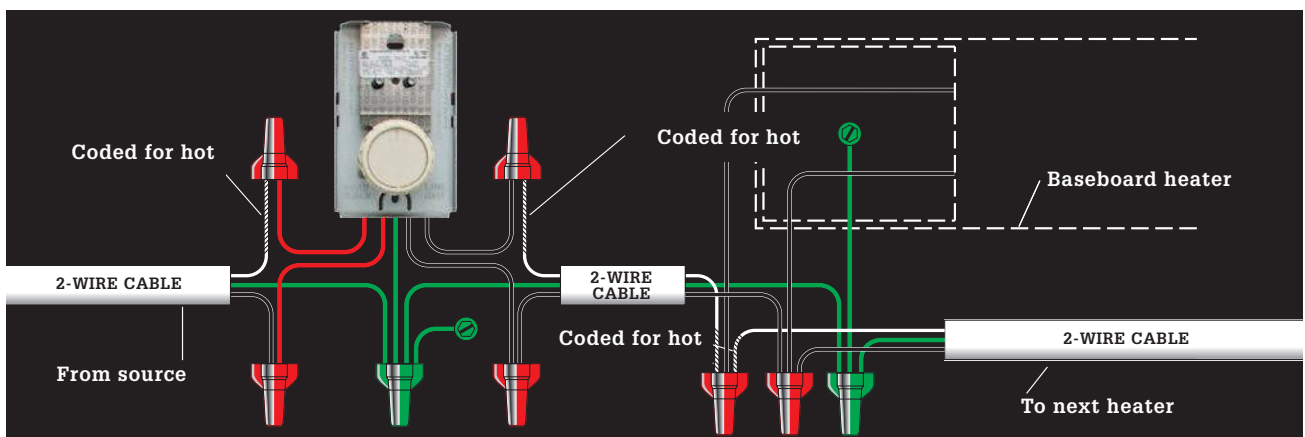
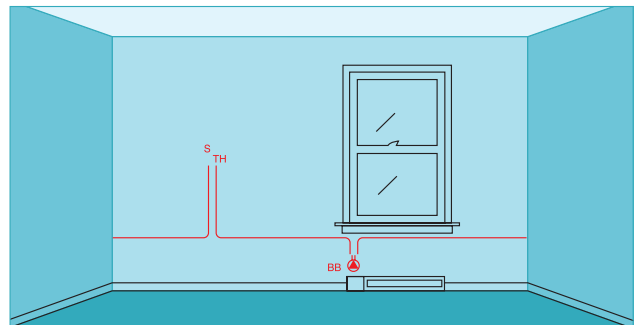
15. 240-VOLT BASEBOARD HEATERS, THERMOSTAT

This layout is typical for a series of 240-volt baseboard heaters controlled by a wall thermostat. Except for the last heater in the circuit, all heaters are wired as shown below. The last heater is connected to only one cable. The sizes of the circuit and cables are determined by finding the total wattage of all heaters. Requires two-wire cable.



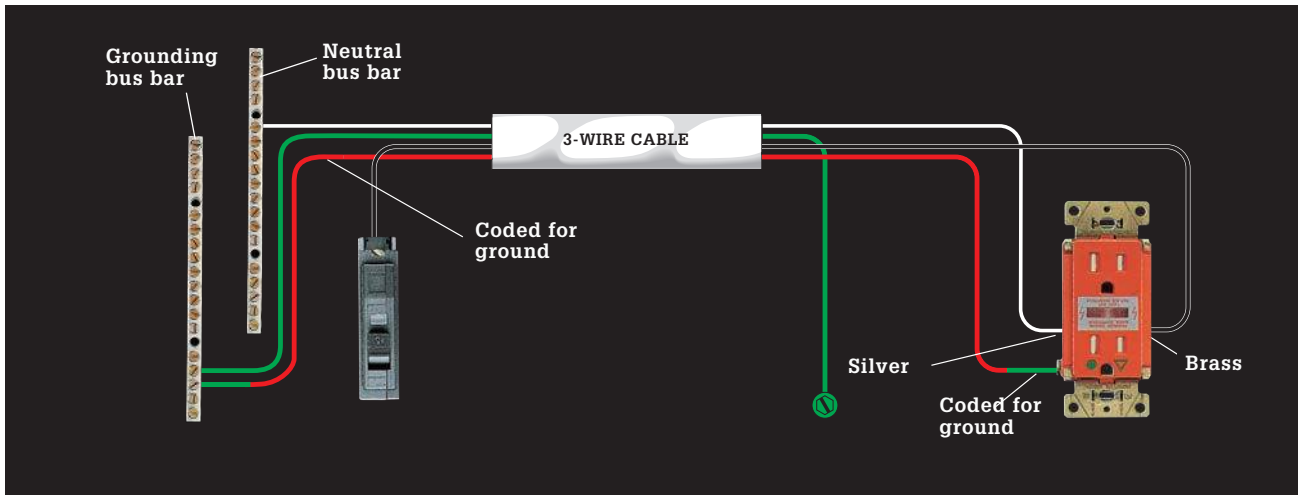
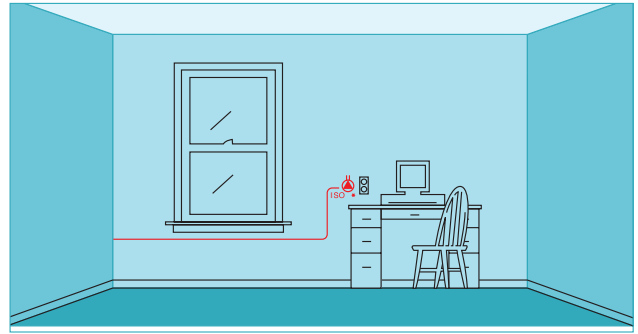
16. DEDICATED 120-VOLT COMPUTER CIRCUIT, ISOLATED-GROUND RECEPTACLE

This 15-amp isolated-ground circuit provides extra protection against surges and interference that can harm electronics. It uses 14/3 cable with the red wire serving as an extra grounding conductor. The red wire is tagged with green tape for identification. It is connected to the grounding screw on an isolated-ground receptacle and runs back to the grounding bus bar in the circuit breaker panel without touching any other house wiring.



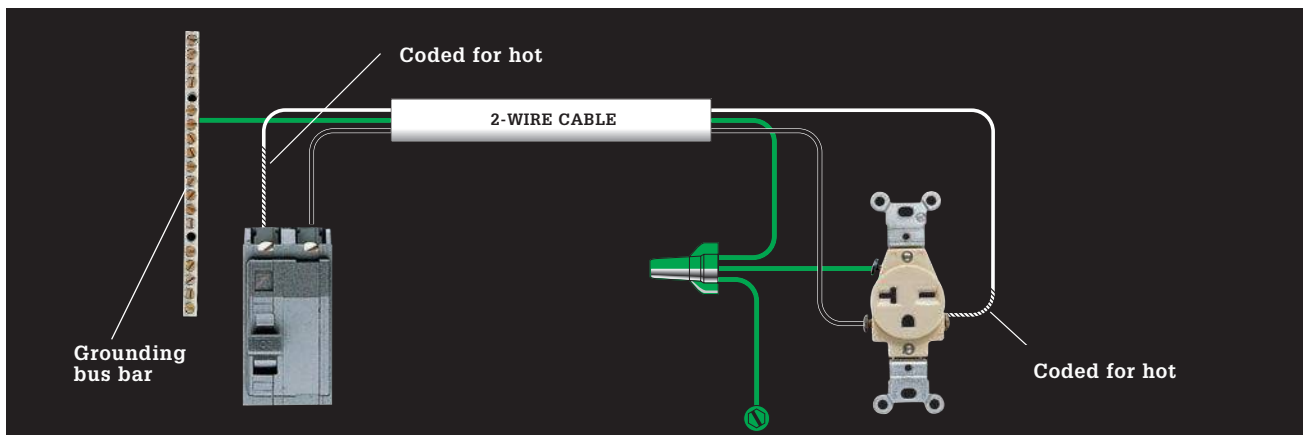
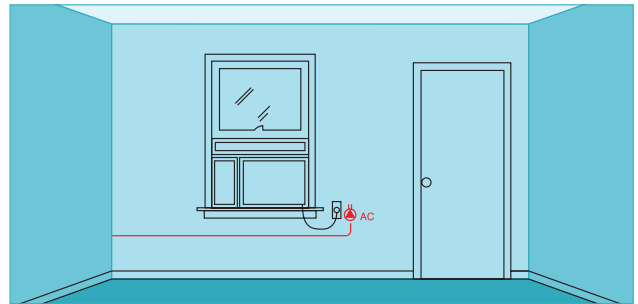
17. 240-VOLT APPLIANCE RECEPTACLE

This layout represents a 20-amp, 240-volt dedicated appliance circuit wired with 12/2 cable, as required by code for a large window air conditioner. Receptacles are available in both singleplex (shown) and duplex styles. The black and the white circuit wires connected to a double-pole breaker each bring 120 volts of power to the receptacle (combined, they bring 240 volts). The white wire is tagged with black tape to indicate it is hot.



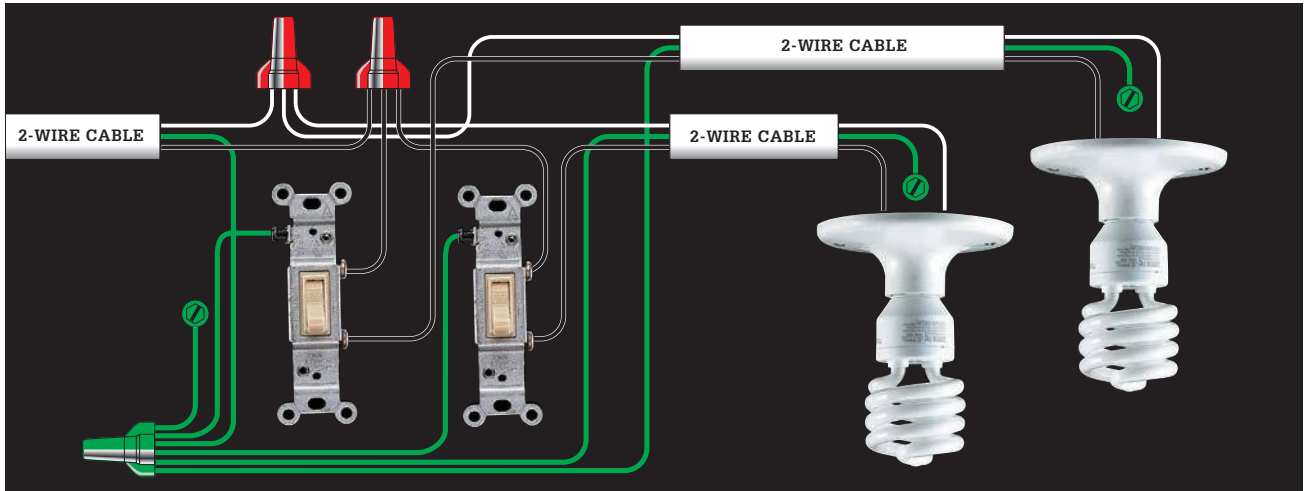
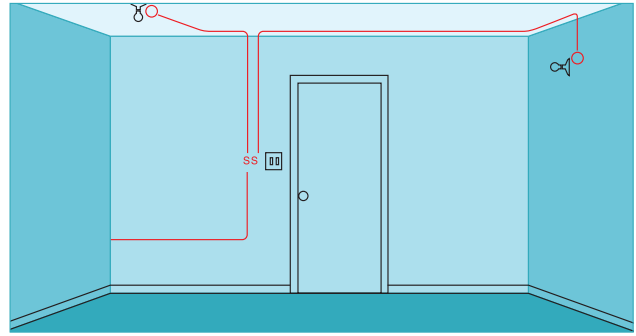
18. GANGED SINGLE-POLE SWITCHES CONTROLLING SEPARATE LIGHT FIXTURES

This layout lets you place two switches controlled by the same 120-volt circuit in one double-gang electrical box. A single-feed cable provides power to both switches. A similar layout with two feed cables can be used to place switches from different circuits in the same box. Requires two-wire cable.



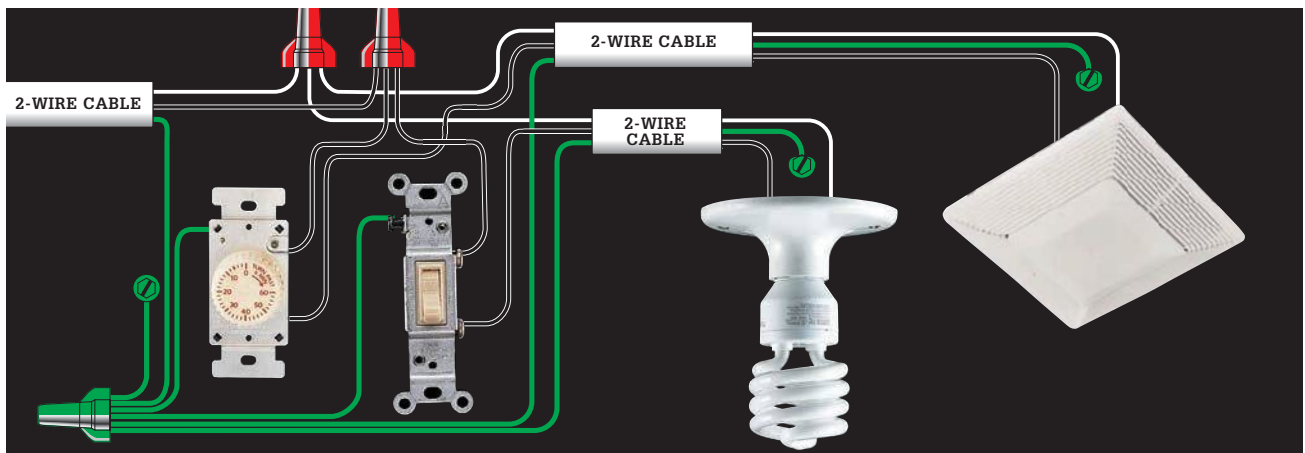
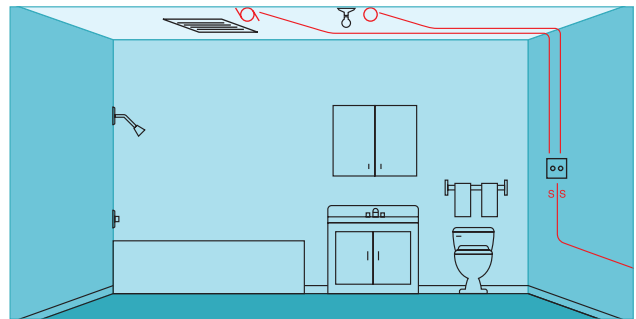
19. GANGED SWITCHES CONTROLLING A LIGHT FIXTURE AND A VENT FAN

This layout lets you place two switches controlled by the same 120-volt circuit in one double-gang electrical box. A single-feed cable provides power to both switches. A standard switch controls the light fixture, and a time-delay switch controls the vent fan.



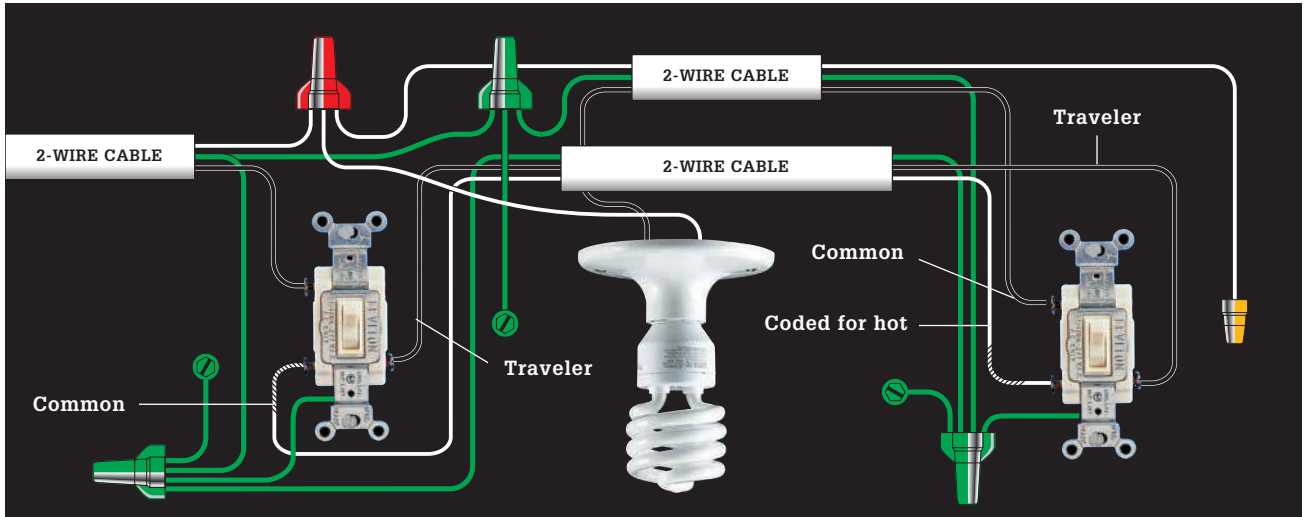
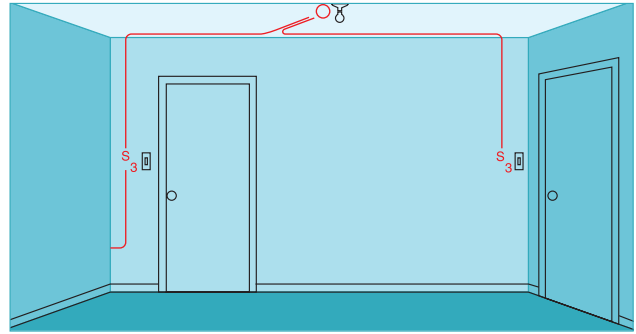
20. THREE-WAY SWITCHES & LIGHT FIXTURE (FIXTURE BETWEEN SWITCHES)

This layout for three-way switches lets you control a light fixture from two locations. Each switch has one common screw terminal and two traveler screws. Circuit wires attached to the traveler screws run between the two switches, and hot wires attached to the common screws bring current from the power source and carry it to the light fixture. Requires parallel runs of 2-wire cable.



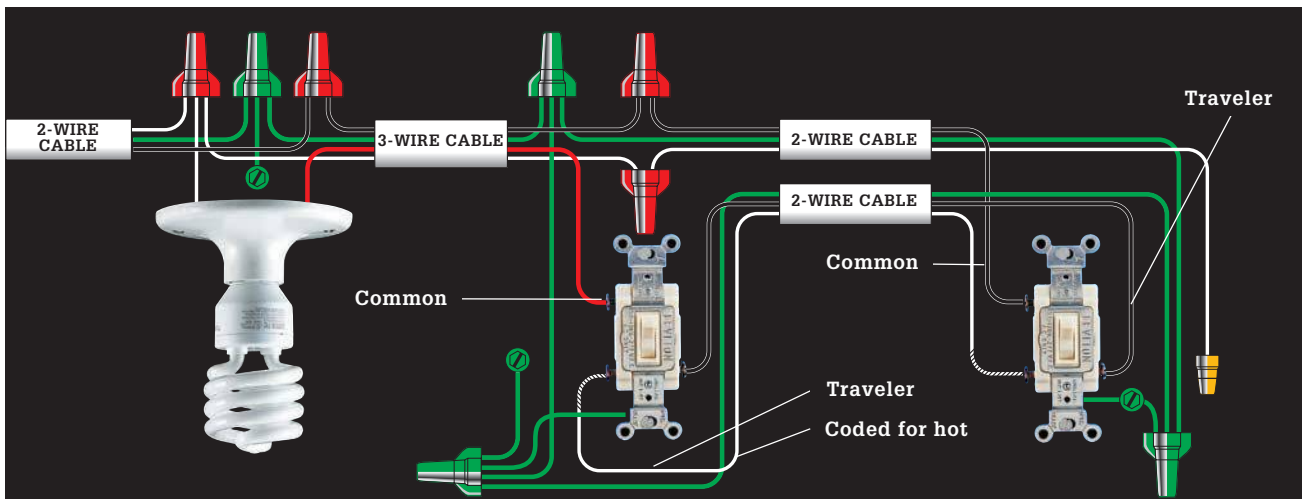
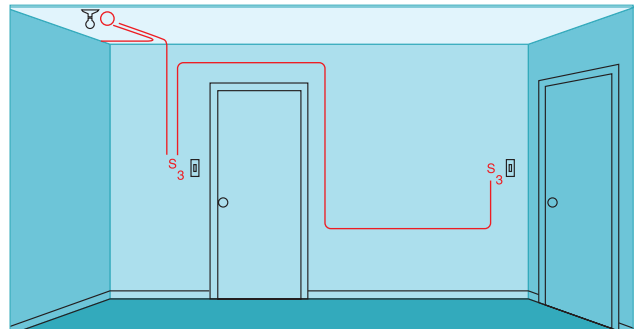
21. THREE-WAY SWITCHES & LIGHT FIXTURE (FIXTURE AT START OF CABLE RUN)

Use this layout variation of circuit map 19 where it is more convenient to locate the fixture ahead of the three-way switches in the cable run. Requires two-wire and three-wire cables.



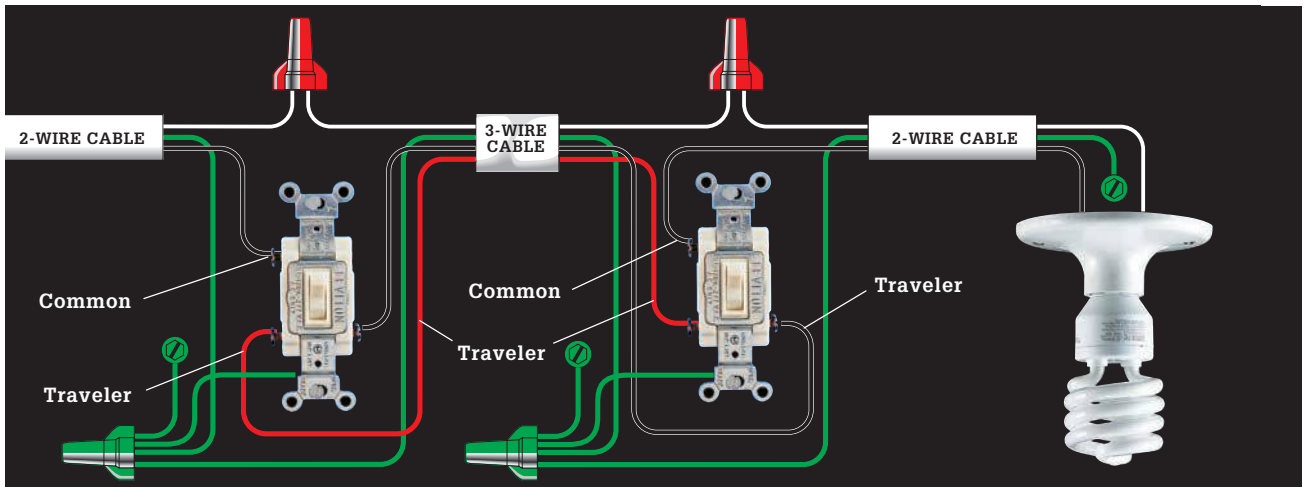
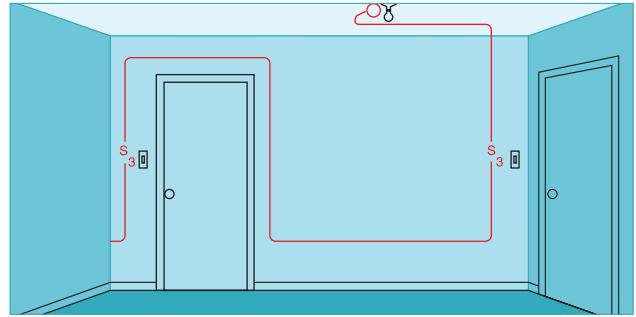
22. THREE-WAY SWITCHES & LIGHT FIXTURE (FIXTURE AT END OF CABLE RUN)

This variation of the three-way switch layout (circuit map 20) is used where it is more practical to locate the fixture at the end of the cable run. Requires two-wire and three-wire cables.



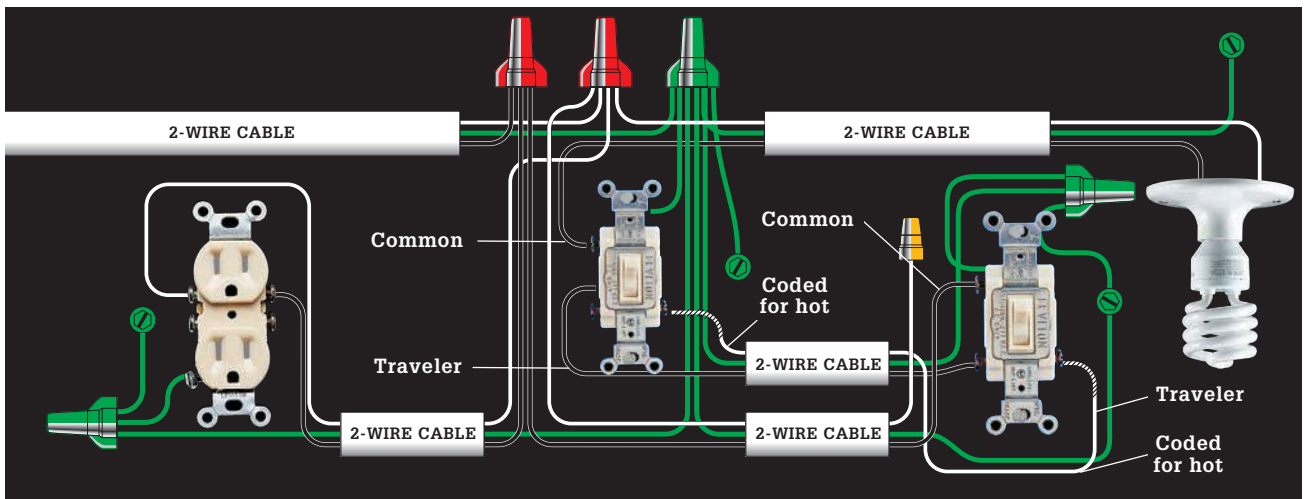
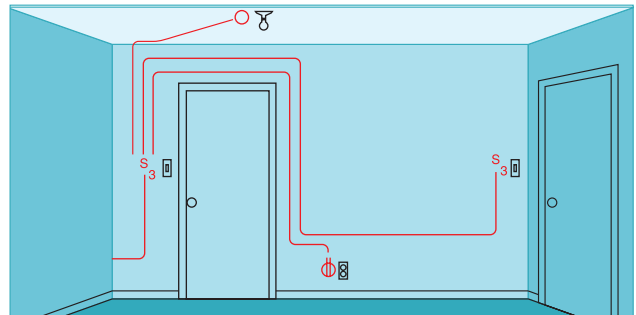
23. THREE-WAY SWITCHES & LIGHT FIXTURE WITH DUPLEX RECEPTACLE

Use this layout to add a receptacle to a three-way switch configuration (circuit map 21). Requires two-wire and parallel runs of two-wire cables.



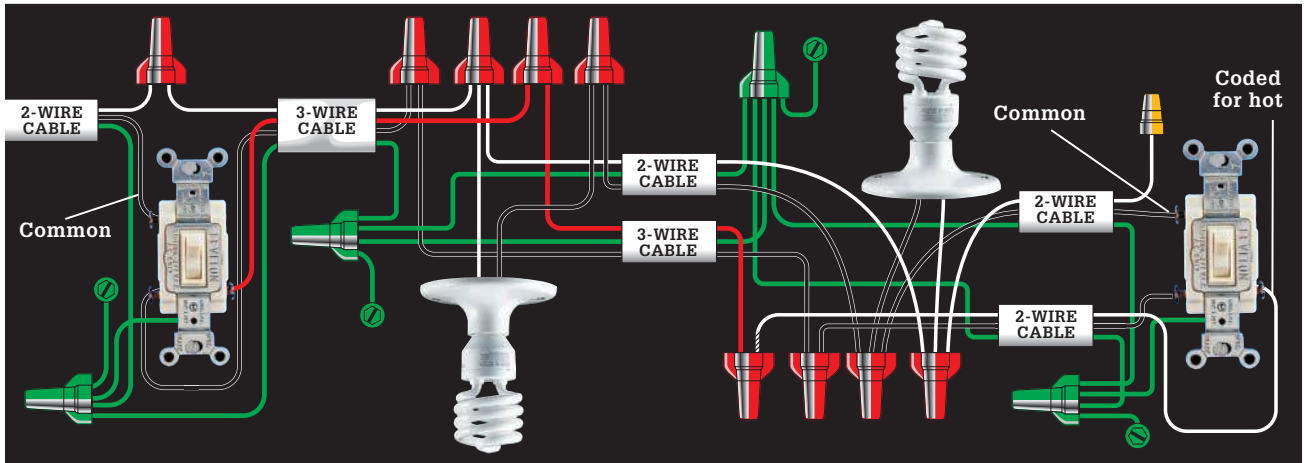
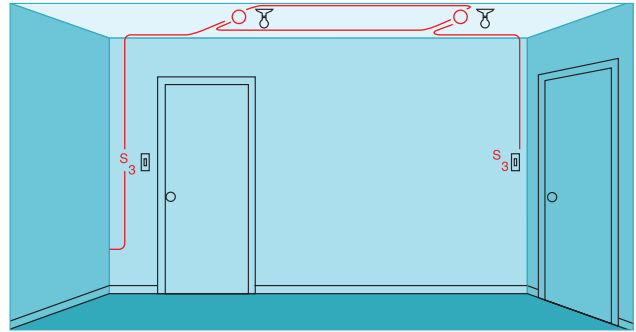
24. THREE-WAY SWITCHES & MULTIPLE LIGHT FIXTURES (FIXTURES BETWEEN SWITCHES)

This is a variation of circuit map 20. Use it to place multiple light fixtures between two three-way switches where power comes in at one of the switches. Requires two- and three-wire cable.



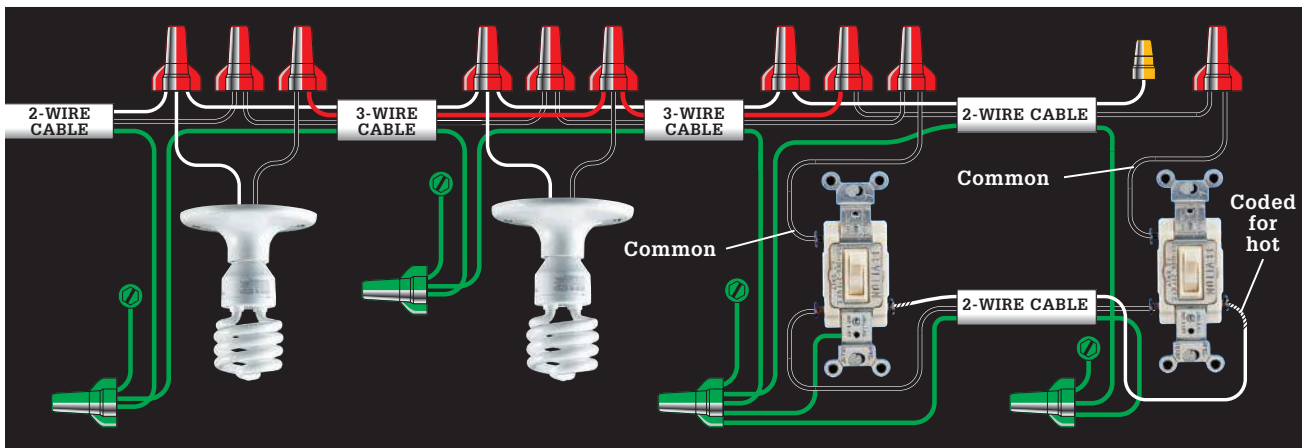
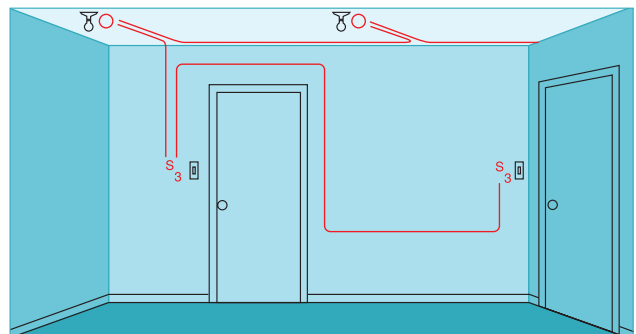
25. THREE-WAY SWITCHES & MULTIPLE LIGHT FIXTURES (FIXTURES AT BEGINNING OF RUN)

This is a variation of circuit map 21. Use it to place multiple light fixtures at the beginning of a run controlled by two three-way switches. Power comes in at the first fixture. Requires two- and three-wire cable.



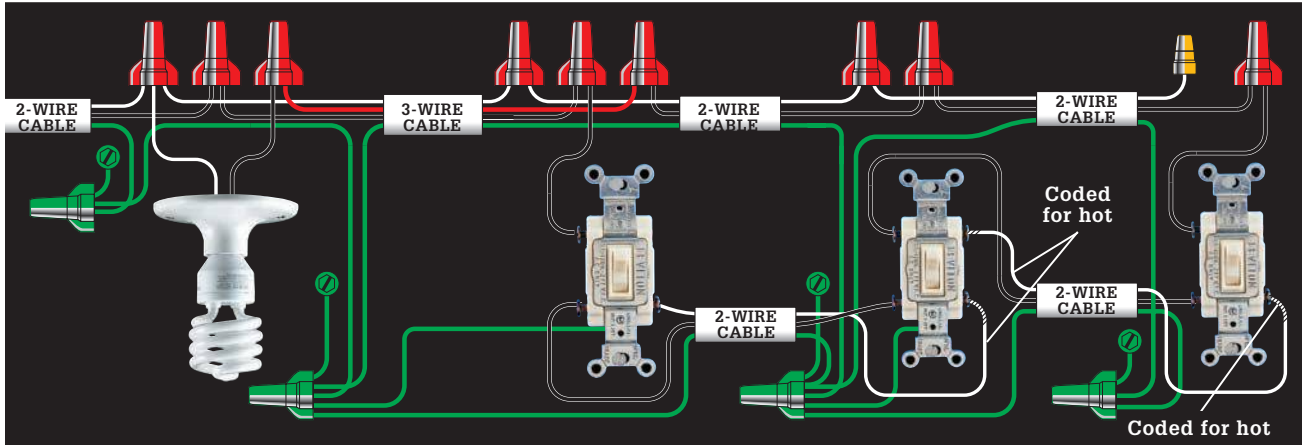
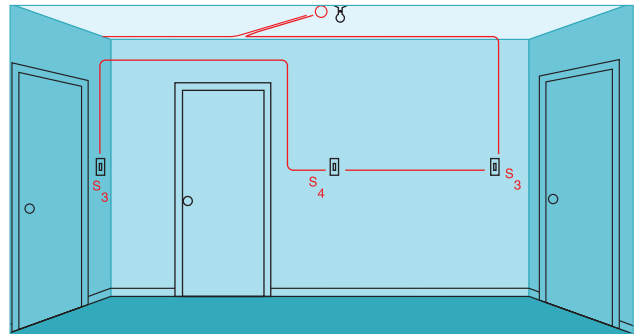
26. FOUR-WAY SWITCH & LIGHT FIXTURE (FIXTURE AT START OF CABLE RUN)

This layout lets you control a light fixture from three locations. The end switches are three-way, and the middle is four-way. A pair of three-wire cables enter the box of the four-way switch. The white and red wires from one cable attach to the top pair of screw terminals (line 1), and the white and red wires from the other cable attach to the bottom screw terminals (line 2). Requires two three-way switches and one four-way switch and two-wire and three-wire cables.



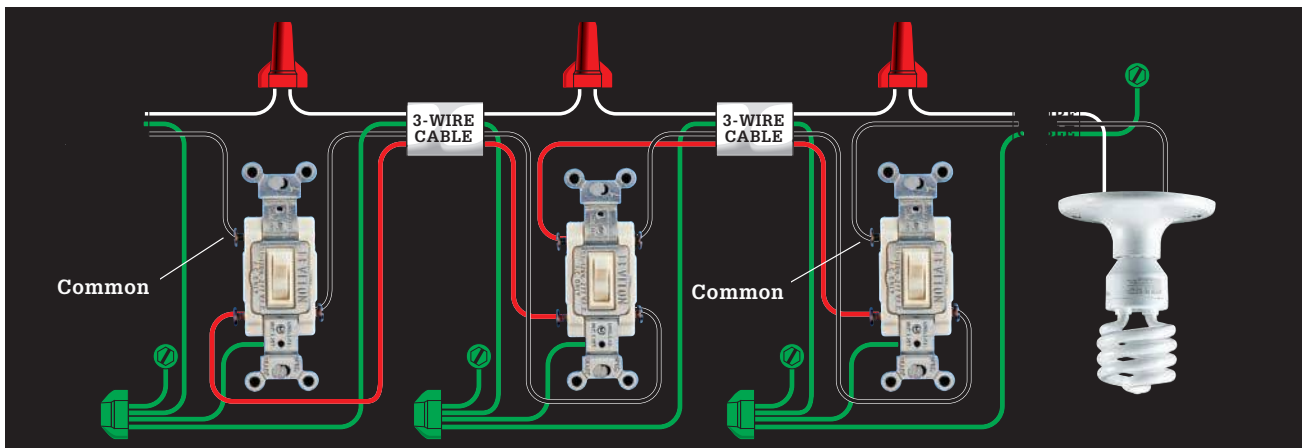
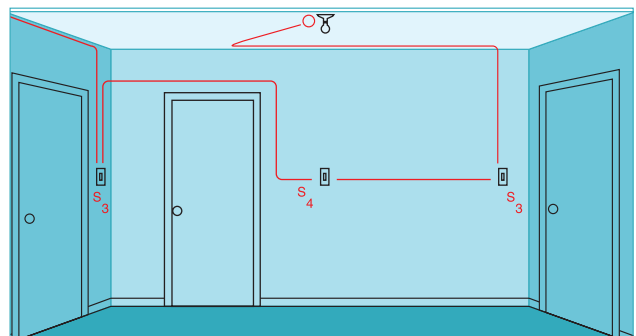
27. FOUR-WAY SWITCH & LIGHT FIXTURE (FIXTURE AT END OF CABLE RUN)

Use this layout variation of circuit map 26 where it is more practical to locate the fixture at the end of the cable run. Requires two three-way switches and one four-way switch and two-wire and three-wire cables.



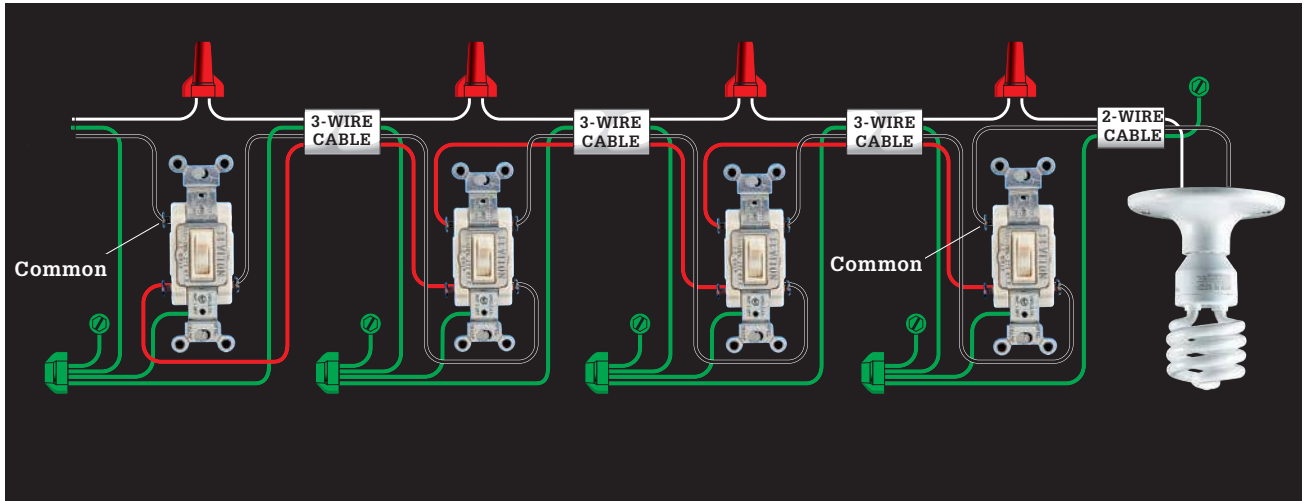
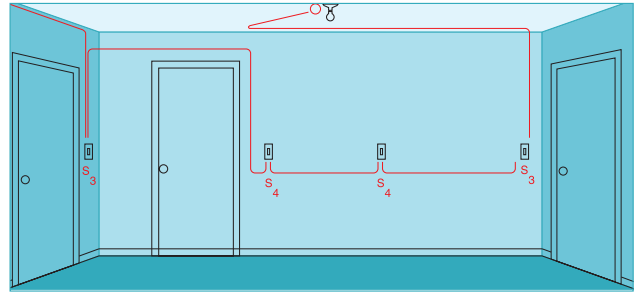
28. MULTIPLE FOUR-WAY SWITCHES CONTROLLING A LIGHT FIXTURE

This alternate variation of the four-way switch layout (circuit map 27) is used where three or more switches will control a single fixture. The outer switches are three-way, and the middle are four-way. Requires two three-way switches and two four-way switches and two-wire and three-wire cables.



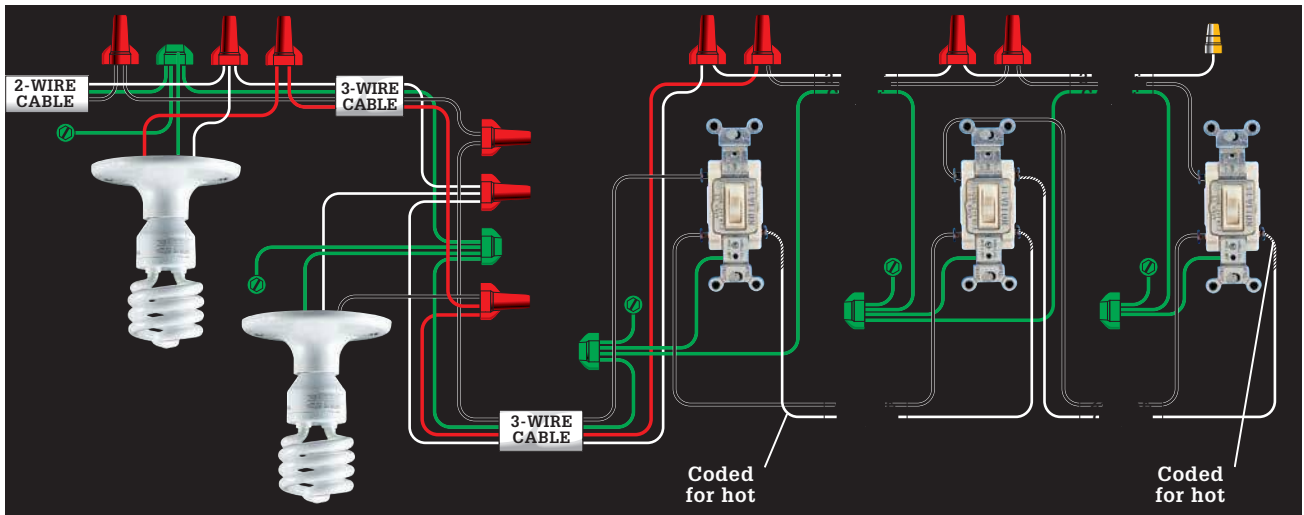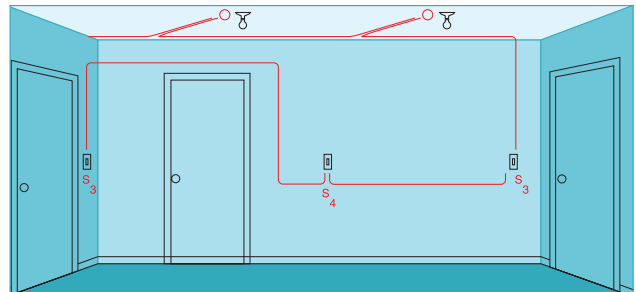
29. FOUR-WAY SWITCHES & MULTIPLE LIGHT FIXTURES

This variation of the four-way switch layout (circuit map 26) is used where two or more fixtures will be controlled from multiple locations in a room. Outer switches are three-way, and the middle switch is a four-way. Requires two three-way switches and one four-way switch and two-wire and three-wire cables.



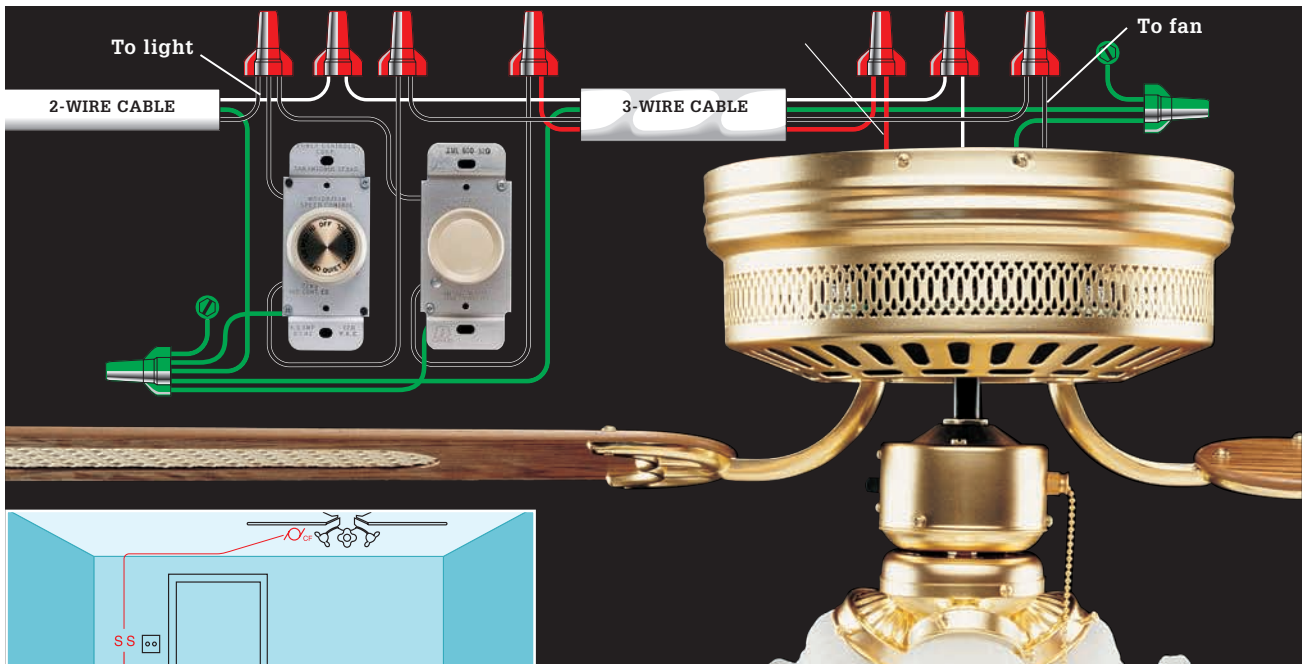
30. CEILING FAN/LIGHT FIXTURE CONTROLLED BY GANGED SWITCHES (FAN AT END OF CABLE RUN)

This layout is for a combination ceiling fan/light fixture controlled by a speed-control switch and dimmer in a double-gang switch box. Requires two-wire and three-wire cables.



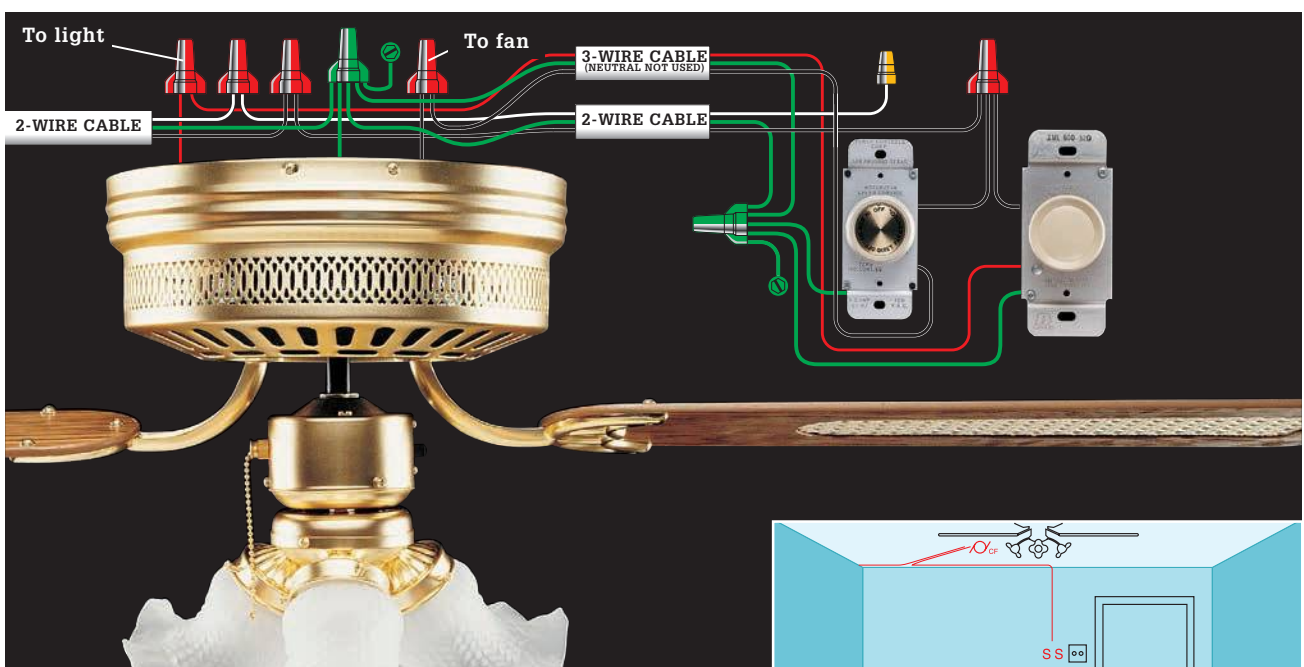31. CEILING FAN/LIGHT FIXTURE CONTROLLED BY GANGED SWITCHES (SWITCHES AT END OF CABLE RUN)

Use this switch loop layout variation when it is more practical to install the ganged speed control and dimmer switches for the ceiling fan at the end of the cable run. Requires two-wire and parallel runs of two-wire cables.



GFCI & AFCI Breakers

Understanding the difference between GFCI (ground-fault circuit interrupter) and AFCI (arc fault circuit interrupter) is tricky for most homeowners. Essentially it comes down to this: Arc-fault interrupters keep your house from burning down; ground-fault interrupters keep people from being electrocuted.

The National Electric Code (NEC) requires that an AFCI breaker be installed on most branch circuits that supply outlets or fixtures in newly constructed homes. The NEC also requires adding AFCI protection to these circuits when you add new circuits and modify or extend existing circuits. They're a prudent precaution in any home, especially if it has older wiring. AFCI breakers will not interfere with the operation of GFCI receptacles, so it is safe to install an AFCI breaker on a circuit that contains GFCI receptacles. For a discussion on codes that concern AFCI and GFCI breakers see pages 120 to 121.

GROUND-FAULT CIRCUIT-INTERRUPTERS

A GFCI is an important safety device that disconnects a circuit in the event of a ground fault (when current takes a path other than the neutral back to the panel).

On new construction, GFCI protection is required for receptacles in these locations: kitchen counter tops, bathrooms, garages, unfinished basements, crawlspaces, outdoors, within six feet of sinks, and in unfinished accessory buildings such as storage and work sheds. In general it is a good practice to protect all receptacle and fixture locations that could encounter damp or wet circumstances.

Tools & Materials ▶

| | |
|-----------------------|----------------------|
| Insulated screwdriver | Combination tool |
| Circuit tester | AFCI or GFCI breaker |

ARC-FAULT CIRCUIT INTERRUPTERS

AFCIs detect arcing (sparks) that can cause fires between and along damaged wires. AFCI protection is required for 15- and 20-amp, 120-volt circuits that serve living rooms, family rooms, dens, parlors, libraries, dining rooms, bedrooms, sun rooms, kitchens, laundry areas, closets, and hallways. AFCI protection is not required for circuits serving bathrooms, garages, the exterior of the home, appliances such as furnaces and air handlers.

The easiest way to provide AFCI protection for a circuit is to install an AFCI circuit breaker labeled as a “combination” device in the electrical panel. The 2014 NEC allows several alternate methods of providing AFCI protection, but you should consult an electrician before using these alternate methods. You should install combination AFCI circuit breakers when installing new circuits that require AFCI protection. You should install either combination AFCI circuit breakers or AFCI receptacles when you modify, replace, or extend an existing circuit that requires AFCI protection.



AFCI breakers (left) are similar in appearance to GFCI breakers (right), but they function differently. AFCI breakers trip when they sense an arc fault. GFCI breakers trip when they sense fault between the hot wire and the ground.



An AFCI-protected receptacle


How to Install an AFCI or GFCI Breaker




1 **Locate the breaker for the circuit** you'd like to protect. Turn off the main circuit breaker. Remove the cover from the panel, and test to ensure that power is off. Remove the breaker you want to replace from the panel. Remove the black wire from the LOAD terminal of the breaker.



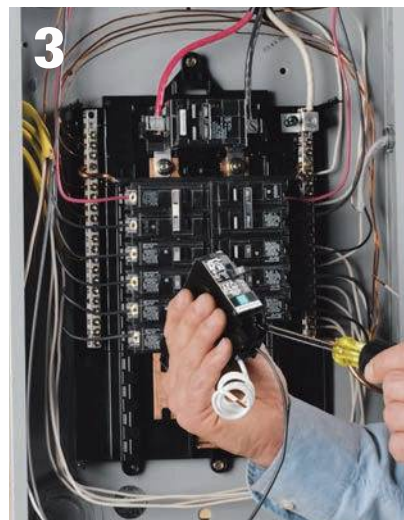
2 **Find the white wire on the circuit** you want to protect, and remove it from the neutral bus bar.



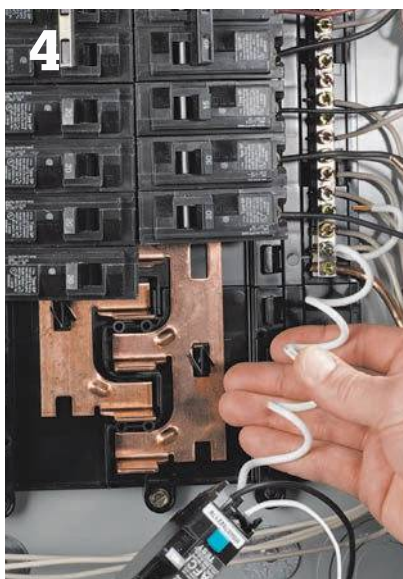
3 **Flip the handle** of the new AFCI or GFCI breaker to OFF. Loosen both of the breaker's terminal screws. Connect the white circuit wire to the breaker terminal labeled PANEL NEUTRAL. Connect the black circuit wire to the breaker terminal labeled LOAD POWER.



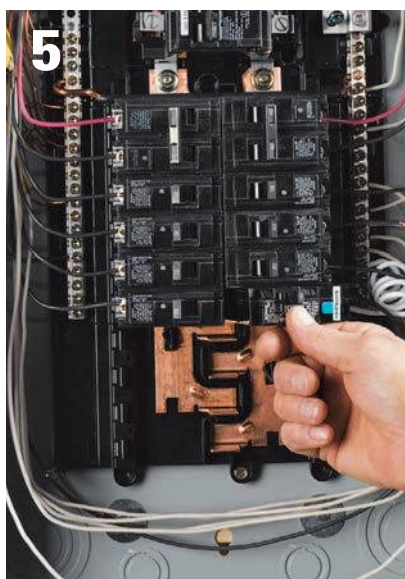4 **Connect the new breaker's coiled white wire** to the neutral bus bar on the service panel.



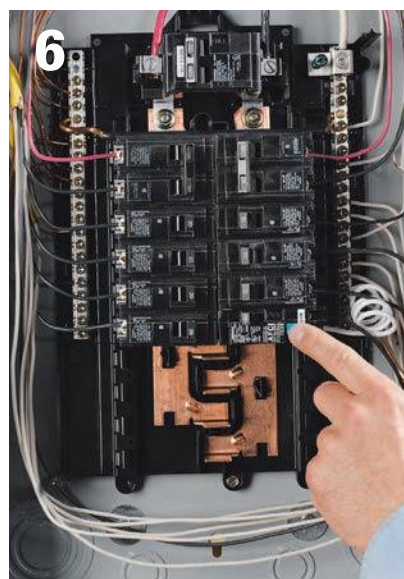5 **Make sure all the connections are tight.** Snap the new breaker into the bus bar.



6 **Turn the main breaker on.** Turn off and unplug all fixtures and appliances on the AFCI or GFCI breaker circuit. Turn the AFCI or GFCI breaker on. Press the test button. If the breaker is wired correctly, the breaker trips open. If it doesn't trip, check all connections or consult an electrician. Replace the panel cover.

Replacing a Service Panel

Only a generation ago, fuse boxes were commonplace. But as our demands for power increased, homeowners replaced the 60-amp boxes with larger, safer, and more reliable circuit breaker panels. Typical new homes were built with perfectly adequate 100-amp load centers. But today, as average home size has risen to more than 2,500 sq. ft. and the number of home electronics has risen exponentially, 100 amps is often inadequate service. As a result, many homeowners have upgraded to 200-amp service, and new single-family homes often include 250 amps or even 400 amp service.

Upgrading your electrical service panel from 100 amps to 200 amps is an ambitious project that requires a lot of forethought. The first step is to obtain a permit. When you are ready to begin, you will need to have your utility company disconnect your house from electrical service at the transformer that feeds your house. When you schedule this, talk to your utility company about the size of your service drop or lateral. That may need to be upgraded too. Not only does this involve working them into your schedule, it means you will have no power during the project. You can rent a portable generator to provide a circuit or two, or you can run a couple extension cords from a friendly neighbor. But unless you are a very fast worker, plan on being

without power for at least one to two days while the project is in process.

Also check with your utility company to make sure you know what equipment is theirs and what belongs to you. In most cases, the electric meter and everything on the street side belongs to the power company, and the meter base and everything on the house side is yours. Be aware that if you tamper with the sealed meter in any way, you likely will be fined. Utility companies will not re-energize your system without approval from your inspecting agency.


Upgrading a service panel is a major project. Do not hesitate to call for help at any point if you're unsure what to do.

Tools & Materials ▶


| | |
|---|----------------------|
| 200-amp load center (service panel) | Weatherhead |
| 200-amp bypass meter base | Service cable |
| Circuit breakers (AFCI if required by local code) | Circuit wires |
| Schedule 80 or RMC conduit and fittings | Plywood backer board |
| | Screwdrivers |
| | Drill/driver |
| | Tape |
| | Allen wrench |
| | Circuit tester |
| | Multimeter |



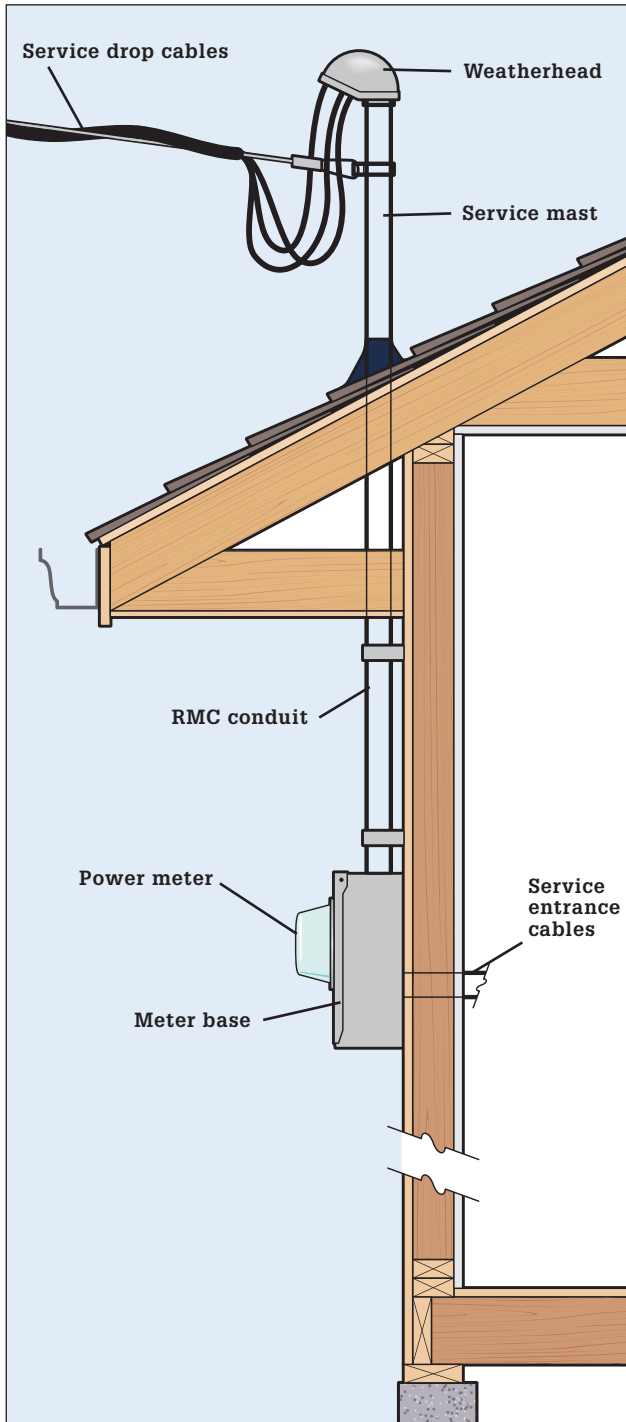Modern homeowners consume more power than our forebears, and it is often necessary to upgrade the electrical service to keep pace. While homeowners are not allowed to make the final electrical service connections, removing the old panel and installing the new panel and meter base yourself can save you hundreds or even thousands of dollars.




Aboveground service drop. In this common configuration, the service cables from the closest transformer (called the service drop) connect to service entrance wires near the weatherhead. This connection is called the service point and is where your property usually begins. The service entrance wires from the weatherhead are routed to a power meter that's owned by your utility company but is housed in a base that's considered your property. From the meter the service entrance wires enter your house through the wall and are routed to the main service panel, where they are connected to the main circuit breaker.

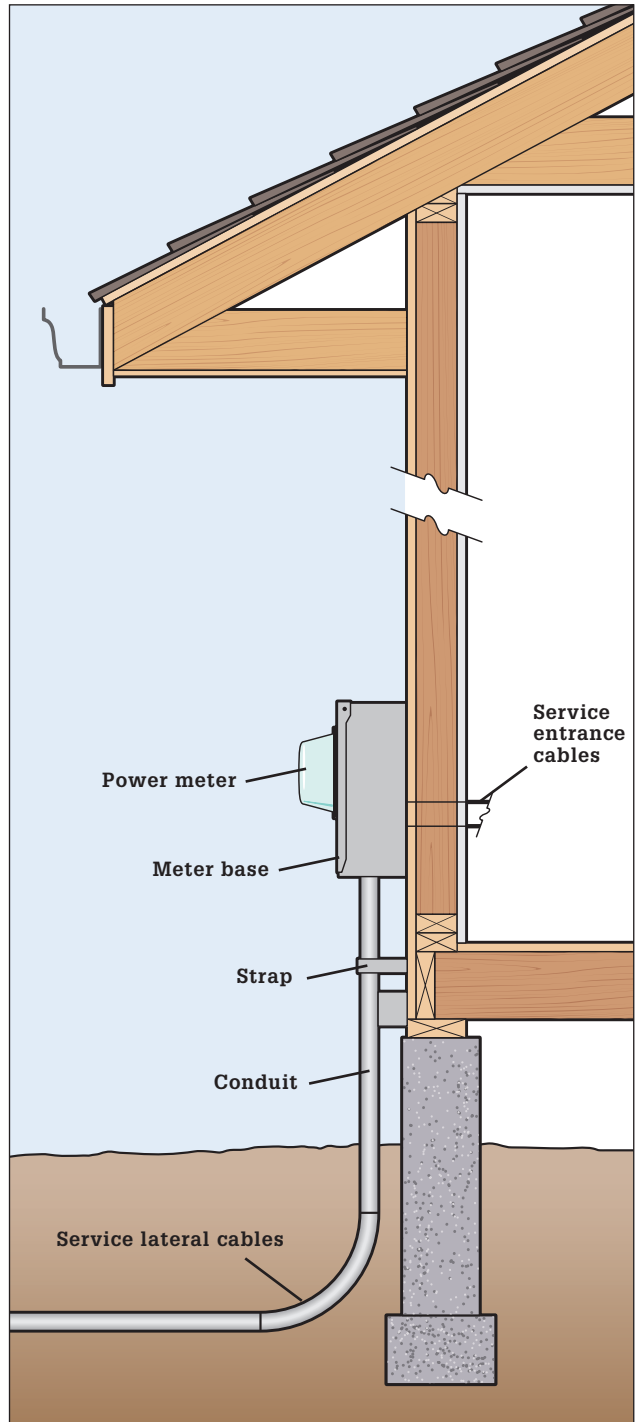

Underground service lateral. Increasingly, homebuilders are choosing to have power supplied to their new homes underground instead of an overhead service drop. Running the cables in the ground eliminates problems with power outages caused by ice accumulation or fallen trees, but it entails a completely different set of cable and conduit requirements. For the homeowner, however, the differences are minimal, because the hookups are identical once the power service reaches the meter.

Locating Your New Panel ▶

Local codes dictate where the main service panel may be placed relative to other parts of your home. Although the codes vary (and always take precedence), national codes stipulate that a service panel (or any other distribution panel) may not be located near flammable materials, in a bathroom, clothes closet or other area designated for storage, above stairway steps, or directly above a workbench or other permanent work station or appliance. The panel also can't be located in a crawl space. If you are installing a new service entry hookup, there are many regulations regarding height of the service drop and the meter. Contact your local inspections office for specific regulations.

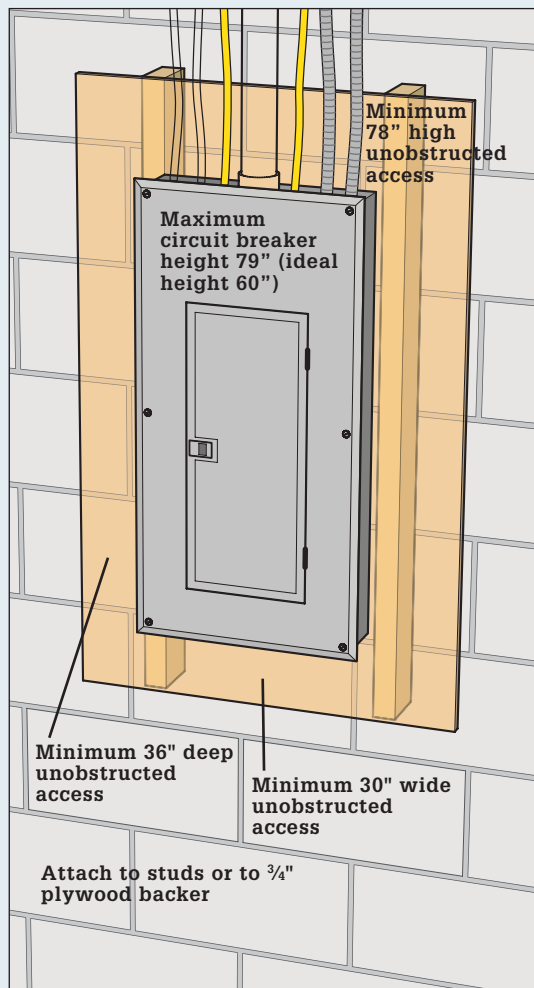

All the equipment you'll need to upgrade your main panel is sold at most larger building centers. It includes (A) a new 200-amp panel; (B) a 200-amp bypass meter base (also called a socket); (C) individual circuit breakers (if your new panel is the same brand as your old one you may be able to reuse the old breakers); (D) new, THW, THHW, THWN-2, RHW, RHW-2, XHHW (2/0 copper seen here); (E) 2" dia. rigid metallic conduit; (F) weatherhead shroud for mast.




The main circuit breaker (called the service equipment) may need to be located outside next to the electric meter if your main panel is too far away from the point where the service cable enters your house. The maximum distance allowed varies widely, from as little as 3 ft. to more than 10 ft. Wiring the service cable through the shutoff has the effect of transforming your main panel into a subpanel, which will impact how the neutral and ground wires are attached (see Subpanels, pages 64 to 65).

How to Replace a Main Panel



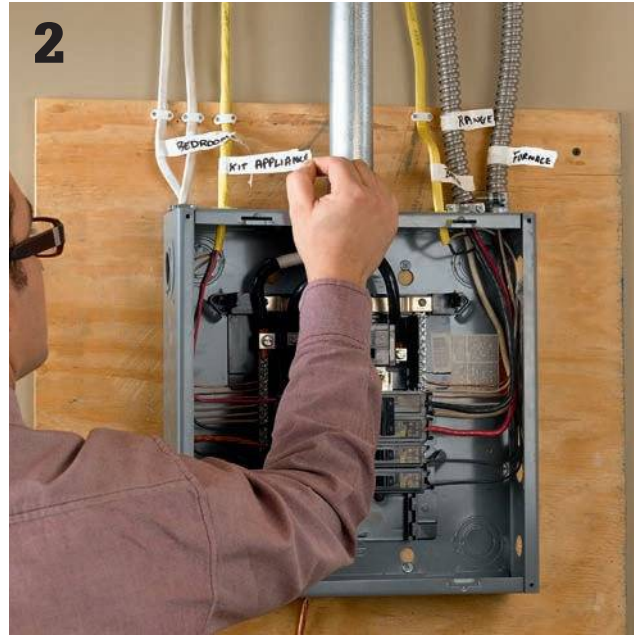
Shut off power to the house at the transformer. This must be done by a technician who is certified by your utility company. Also have the utility worker remove the old meter from the base. It is against the law for a homeowner to break the seal on the meter.



Label all incoming circuit wires before disconnecting them. Labels should be written clearly on tape that is attached to the cables outside of the existing service panel. Test the circuits before starting to make sure they are labeled correctly.




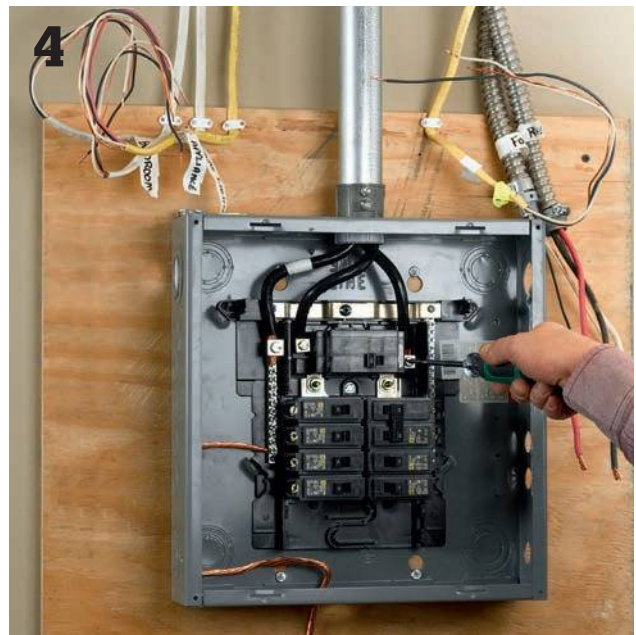Disconnect incoming circuit wires from breakers, grounding bar, and neutral bus bar. Also disconnect cable clamps at the knockouts on the panel box. Retract all circuit wires from the service panel and coil it up neatly, with the labels clearly visible.




Unscrew the lugs securing the service entry cables at the top of the panel. For 240-volt service you will find two heavy-gauge SE cables, probably with black sheathing. Each cable carries 120 volts of electricity. A neutral service cable, usually of smaller gauge than the SE cables, will be attached to the neutral bus bar. This cable returns current to the source.

(continued)

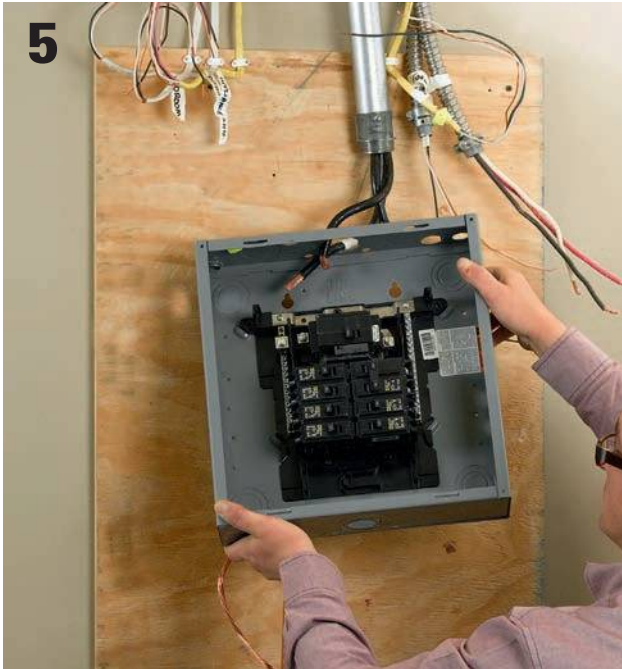

5

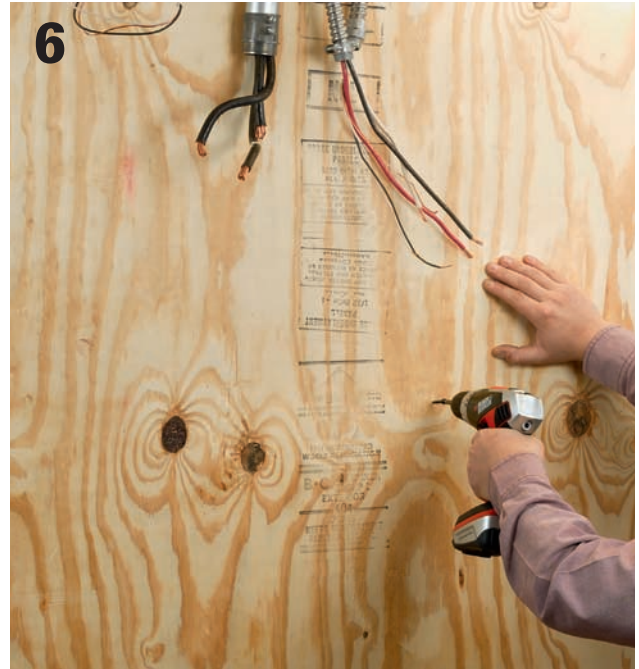Remove the old service panel box. Boxes are rated for a maximum current capacity; and if you are upgrading, the components in the old box will be undersized for the new service levels. The new box will have a greater number of circuit slots as well.




6

Replace the old panel backer board with a larger board in the installation area (see sidebar, page 52). A piece of $\frac{3}{4}$ " plywood is typical. Make sure the board is well secured at wall framing members.



7

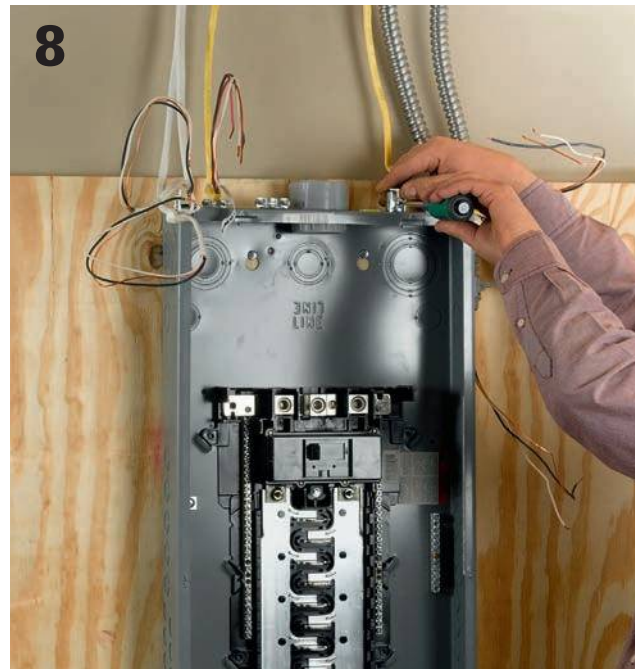Attach the new service panel box to the backer board, making sure that at least two screws are driven through the backer and into wall studs. Drill clearance holes in the back of the box at stud locations if necessary. Use roundhead screws that do not have tapered shanks so the screwhead seats flat against the panel.



8

Attach properly sized cable clamps to the box at the knockout holes. Install one cable per knockout in this type of installation and plan carefully to avoid removing knockouts that you do not need to remove (if you do make a mistake, you can fill the knockout hole with a plug).

Splicing in the Box ▶

Some wiring codes allow you to make splices inside the panel box if the circuit wire is too short. Use the correct wire cap and wind electrical tape over the conductors where they enter the cap. If your municipality does not allow splices in the panel box, you'll have to rectify a short cable by splicing it in a junction box before it reaches the panel and then replacing the cable with a longer section for the end of the run. Make sure each circuit line has at least 12" of slack.



9



Attach the white neutral from each circuit cable to the neutral bus bar. Most panels have a preinstalled neutral bus bar, but in some cases you may need to purchase the bar separately and attach it to the panel back. The panel should also have a separate grounding bar that you also may need to purchase separately. Attach the grounds as well.

10



Attach the hot lead wire to the terminal on the circuit breaker, and then snap the breaker into an empty slot. When loading slots, start at the top of the panel and work your way downward. It is important that you balance the circuits as you go to equalize the amperage. For example, do not install all the 15-amp circuits on one side and all the 20-amp circuits on the other.

11




Create an accurate circuit index and affix it to the inside of the service panel door. List all loads that are on the circuit as well as the amperage. Once you have restored power to the new service panel (see step 18), test out each circuit to make sure you don't have any surprises. With the main breakers on, shut off all individual circuit breakers, and then flip each one on by itself. Walk through your house and test every switch and receptacle to confirm the loads on that circuit.

(continued)



12

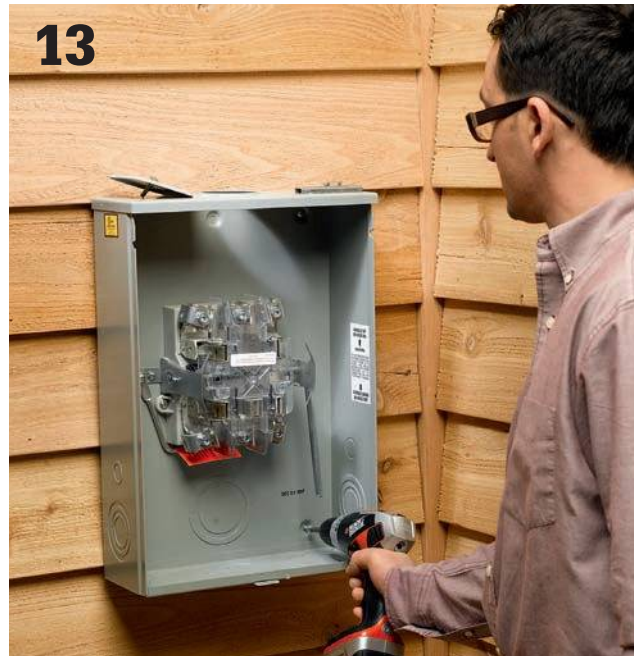Install grounding conductors (see pages 58 to 59). Local codes are very specific about how the grounding and bonding needs to be accomplished. For example, some require multiple rods driven at least 6 ft. apart. Discuss your grounding requirements thoroughly with your inspector or an electrician before making your plan.



13

Replace the old meter base (have the utility company remove the meter when they shut off power to the house, step 1). Remove the old meter base, also called a socket, and install a new base that's rated for the amperage of your new power service. Here, a 200-amp bypass meter base is being installed.




14

Update the conduit that runs from your house to the bottom of the meter base. This should be 2" rigid conduit in good repair. Attach the conduit to the base and wall with the correct fittings. Rigid metal conduit is a good option, but Schedule 80 PVC is probably the best choice for housing the service entrance wires.




15

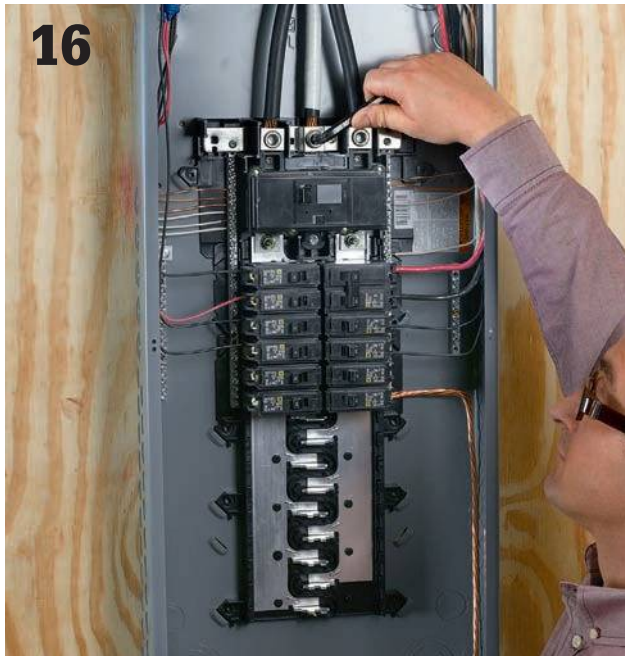Install new service entrance wires. Each wire carries 120 volts from the meter to the service wire lugs at the top of your service panel. Code is very specific about how these connections are made. In most cases, you'll need to tighten the terminal nuts with a specific amount of torque that requires a torque wrench to measure. Also attach the sheathed neutral wire to the neutral/grounding lug.



16

Attach the SE wires to the lugs connected to the main breakers at the top of your service entry panel. Do not remove too much insulation on the wires—leaving the wires exposed is a safety hazard. The neutral service entry wire is attached either directly to the neutral bus bar or to a metal bridge that is connected to the neutral bonding bus bar. Install the green grounding screw provided with the panel.


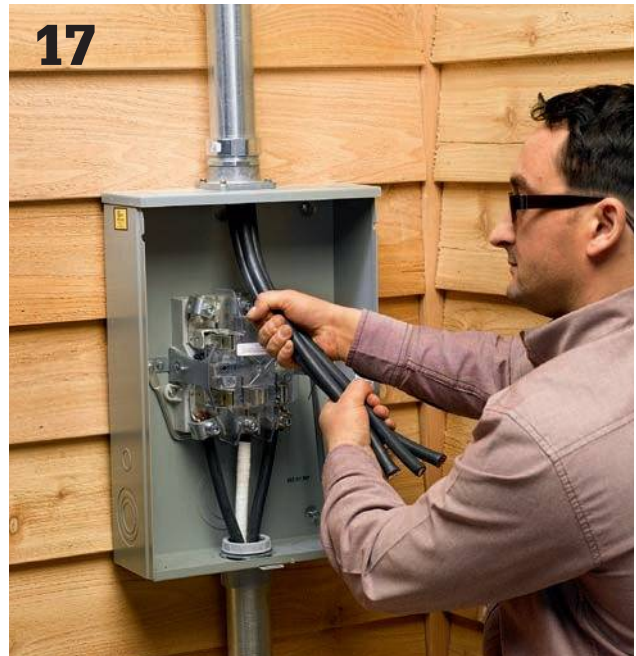


17

Install service entrance wires from the meter to the weatherhead, where the connections to the service drop wires are made. Only an agent for your public utility company may make the hookup at the weatherhead.

Tall Mast, Short Roof ▶

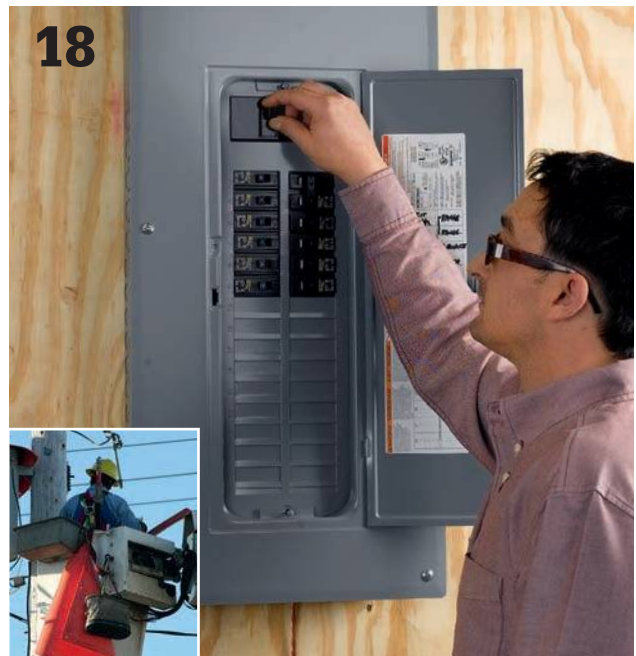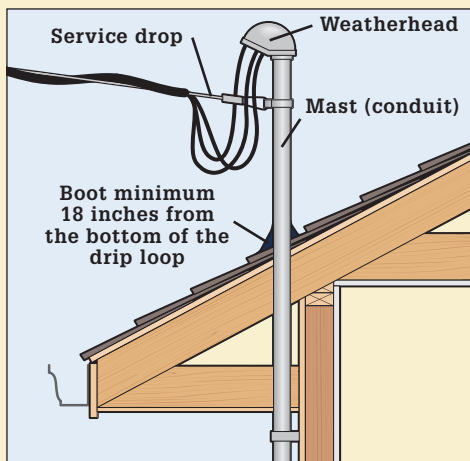The service drop must occur at least 10 ft. above ground level, and as much as 14 ft. in some cases. Occasionally, this means that you must run the conduit for the service mast up through the eave of your roof and seal the roof penetration with a boot.



18

Have the panel and all connections inspected and approved by your local building department, and then contact the public utility company to make the connections at the power drop. Once the connections are made, turn the main breakers on and test all circuits.


Grounding & Bonding a Wiring System

All home electrical systems must be bonded and grounded according to code standards. This entails two tasks: the metal water and gas pipes must be connected electrically to create a continuous low resistance path back to the main electrical panel; and the main electrical panel must be grounded to a grounding electrode such as a ground rod or rods driven into the earth near the foundation of your house. Although the piping system is bonded to the ground through your main electrical service panel, the panel grounding and the piping bonding are unrelated when it comes to function. The grounding wire that runs from your electrical panel to grounding electrode helps even out voltage increases that often occur because of lightning and other causes. The wires that bond your metal piping are preventative, and they only become important in the unlikely event that an electrical conductor energizes the pipe. In that case, correct bonding of the piping system will ensure that the current does not remain in the system, where it could electrocute anyone who touches a part of the system, such as a faucet handle. Bonding is done relatively efficiently at the water heater, as the gas piping and water piping generally there.

Gas pipe in older homes is usually steel or copper. The bonding connection point for these pipes can be at any accessible location, such as at the water heater or at the gas meter. Gas pipe in some new homes is a flexible material called corrugated stainless steel tubing (CSST). The bonding point for CSST must be at the first piece of steel or copper pipe where the gas service enters the home. This is because lightning can blow holes in CSST, causing a gas leak.


Tools & Materials ▶

| | |
|-------------------|----------------|
| Hammer | 3 pipe |
| Straight edge | ground clamps |
| screwdriver | Eye and ear |
| Drill | protection |
| ½" drill bit | Work gloves |
| A length of | Grounding rods |
| ground wire | 5-lb. maul |
| Some wire staples | Caulk |

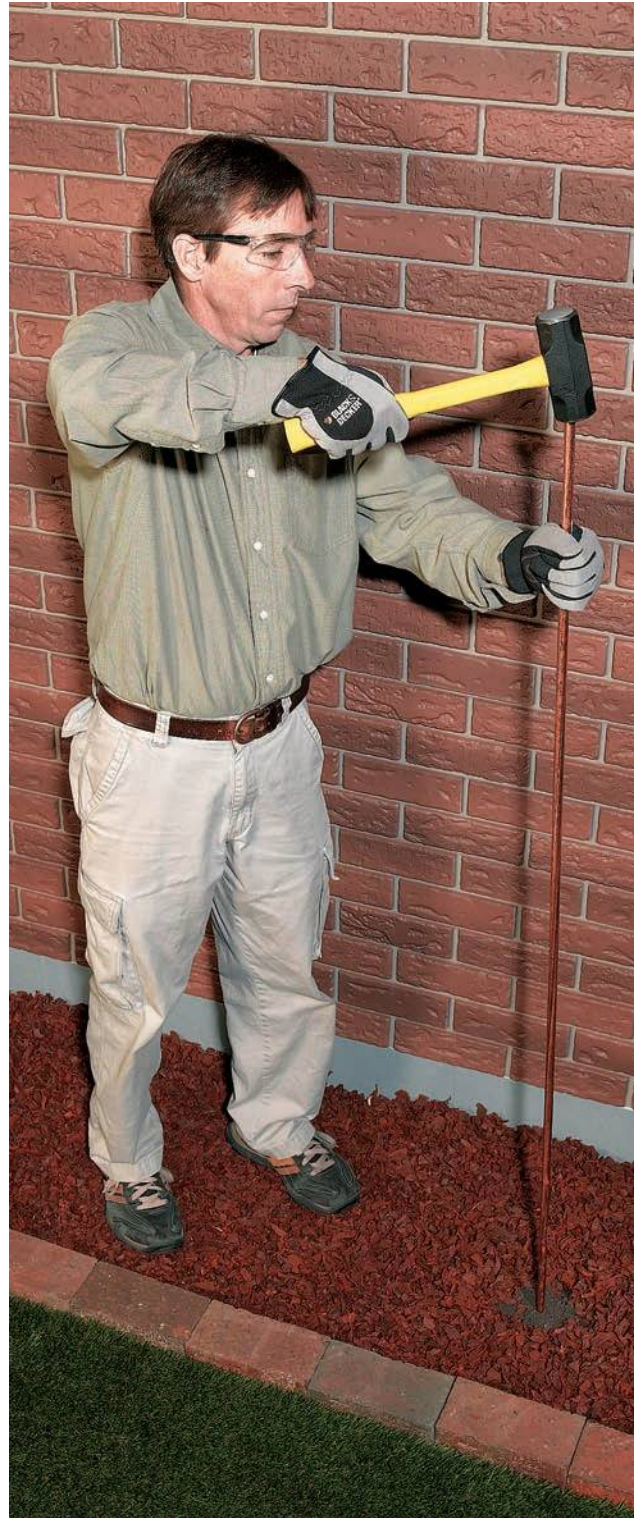

A pair of 8-ft.-long metal ground rods are driven into the earth next to your house to provide a path to ground for your home wiring system.

How to Bond Metallic Piping

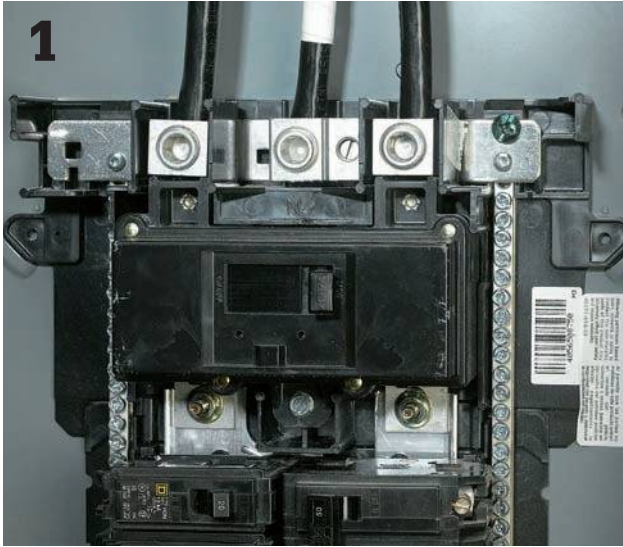

1 **Determine the amperage rating** of your electrical service by looking at your main breakers. The system amperage (usually 100 or 200 amps) determines the required gauge of the bonding wire you need. #4 copper wire is sufficient for service not exceeding 200 amps. Smaller, less expensive copper wire is allowed for services between 100 and 175 amps. Check with your electrical inspector if you want to use wire smaller than #4.



2 **Run the bonding wire** from a point near your water heater (a convenient spot if you have a gas-fueled water heater) to an exit point where the wire can be bonded to the grounding wire that leads to the exterior grounding electrodes. This is frequently done at the service panel. Run this wire as you would any other cable, leaving approximately 6 to 8 ft. of wire at the water heater. If you are running this wire through the ceiling joists, drill a 1/2" hole as close to the center as possible to not weaken the joist. Staple the wire every 2 ft. if running it parallel to the joists.



3 **Install pipe ground clamps** on each pipe (hot water supply, cold water supply, gas), roughly a foot above the water heater. Do not install clamps near a union or elbow because the tightening of the clamps could break or weaken soldered joints. Also make sure the pipes are free and clear of any paint, rust, or any other contaminant that may inhibit a good clean connection. Do not overtighten the clamps. Use clamps that are compatible with the pipe so that corrosion will not occur. Use copper or brass clamps on copper pipe. Use brass or steel clamps on steel pipe.




4 **Route the ground wire** through each clamp wire hole and then tighten the clamps onto the wire. Do not cut or splice the wire: The same wire should run through all clamps.

(continued)




5 **At the panel,** turn off the main breaker. Open the cover by removing the screws, and set the cover aside. Route the ground wire through a small $\frac{3}{8}$ " hole provided towards the rear of the panel on the top or bottom. You will usually have to knock the plug out of this hole by placing a screwdriver on it from the outside and tapping with a hammer. Make sure the ground wire will not come into contact with the bus bars in the middle of the panel or any of the load terminals on the breakers.

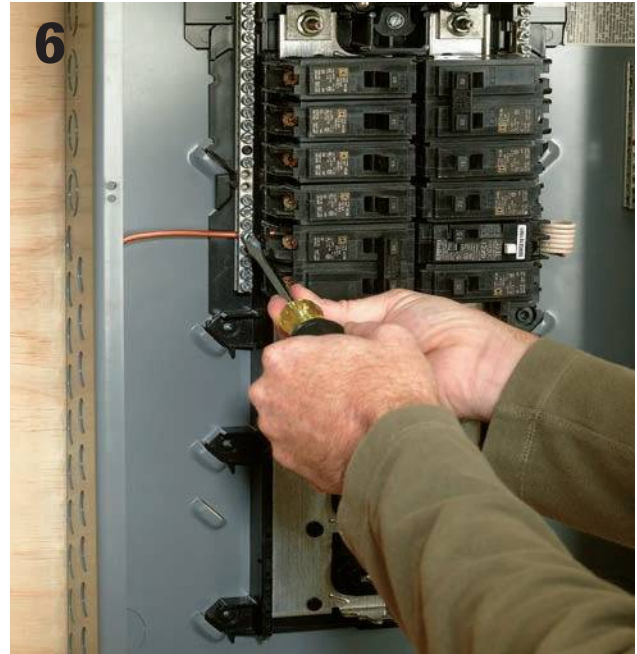

6 **Locate an open hole** on your ground and neutral bus and insert the ground wire. These holes are large enough to accommodate up to a #4 awg wire, but it may be difficult at times. If you're having trouble pushing the wire in, trim a little wire off the end and try with a clean cut piece. Secure the set screw at the lug. Replace the panel cover and turn the main breaker back on.

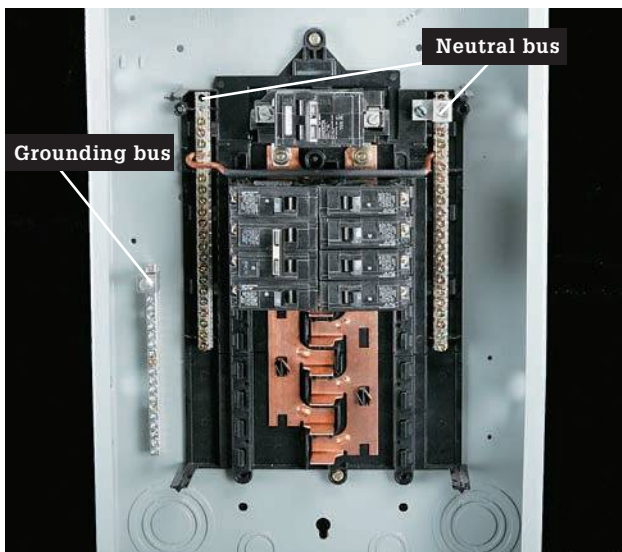Tips for Grounding the Main Service Panel



The neutral and grounding wires should not be connected to the same bus in most subpanels. The grounding bus should be bonded to the subpanel cabinet. The neutral bus should not be bonded to the subpanel cabinet.



Metallic conduit must be physically and electrically connected to panel cabinets. A bonding bushing may be required in some cases, where not all of a knockout is removed.

Ground Rod Installation

The ground rod is an essential part of the grounding system. Its primary function is to create a path to ground for electrical current, such as lightning, line surges, and unintentional contact with high voltage lines. If you upgrade your electrical service you likely will need to upgrade your grounding wire and rods to meet code.

Note: Different municipalities have different requirements for grounding, so be sure to check with the AHJ (Authority Having Jurisdiction) first before attempting to do this yourself.

Call before you dig! Make sure the area where you will be installing the ground rods is free and clear from any underground utilities.

Exercise Your Breakers ▶

Your breakers (including the main) should be “exercised” once a year to ensure proper mechanical function. Simply turn them off and then back on. A convenient time to perform the exercise is at daylight savings time, when you’ll need to reset all of your clocks anyway.

How to Install a Grounding Electrode System

1




Begin by purchasing two copper-coated steel ground rods $\frac{5}{8}$ " diameter by 8' long. Grounding rods have a driving point on one end and a striking face on the other end.

2



Drill a $\frac{5}{16}$ " hole in the rim joist of your house, as close as practical to the main service panel to the outside of the house above the ground level at least 6".


(continued)

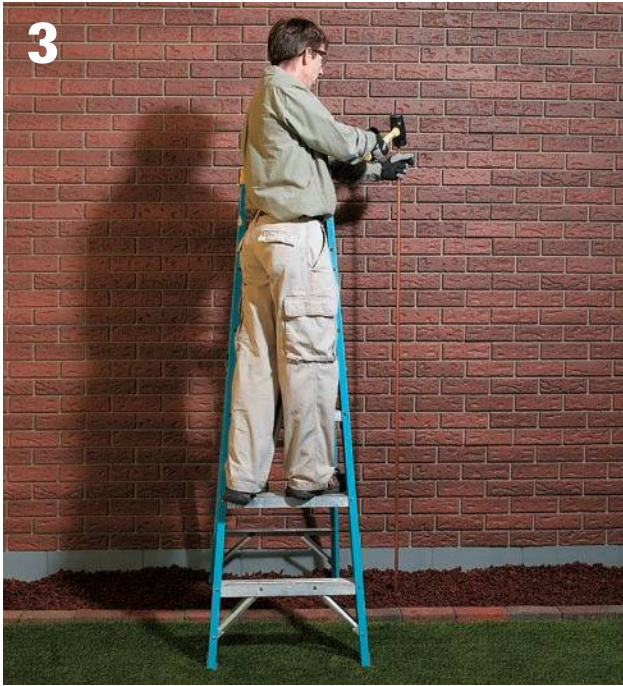


3 About a foot from the foundation of the house, pound one ground rod into the earth with a five-pound maul. If you encounter a rock or other obstruction, you can pound the ground rod at an angle as long as it does not exceed 45°. Drive until only 3" or 4" of the rod is above ground. Measure at least 6 ft. from the first ground rod and pound in another one.



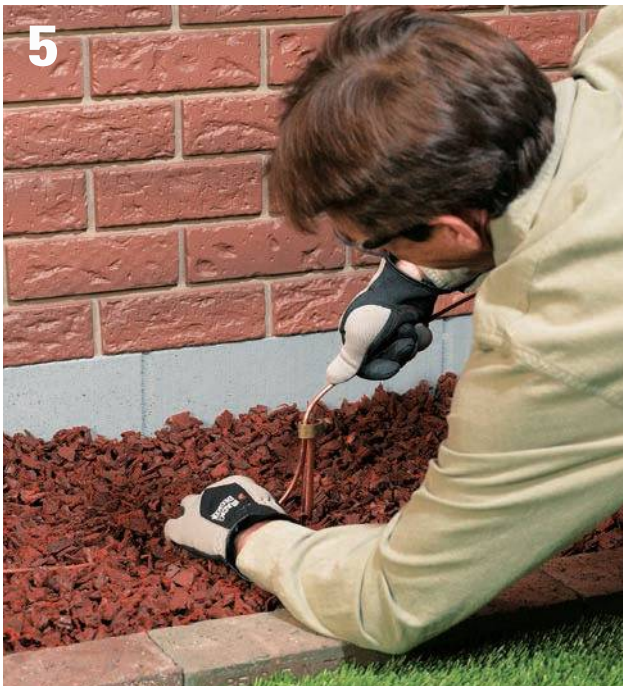4 Run uninsulated #4 copper wire from the ground bus in your main service panel through the hole in the rim joist and to the exterior of the house, leaving enough wire to connect the two ground rods together.



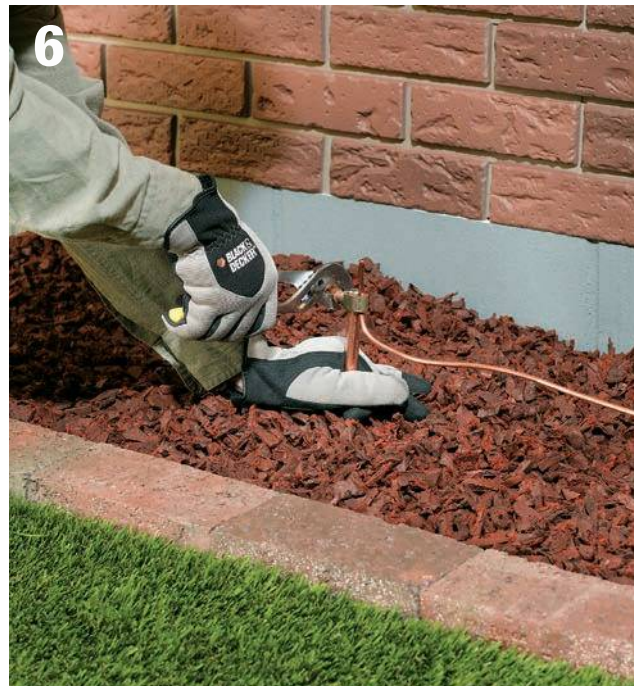5 Using a brass clamp commonly referred to as an acorn, connect the wire to the first ground rod, pulling the wire taut so no slack exists. Continue pulling the wire to reach the second grounding rod, creating a continuous connection.



6 Connect the second ground rod with another acorn to the uncut grounding wire previously pulled through the first acorn. Trim the excess wire.



7 Dig out a few inches around each rod to create clearance for the five-pound maul. Creating a shallow trench beneath the grounding wire between the rods is also a good idea. Drive each rod with the maul until the top of the rod is a few inches below grade.




8 Inject caulk into the hole in the rim joist on both the interior and exterior side.

Tips for Grounding



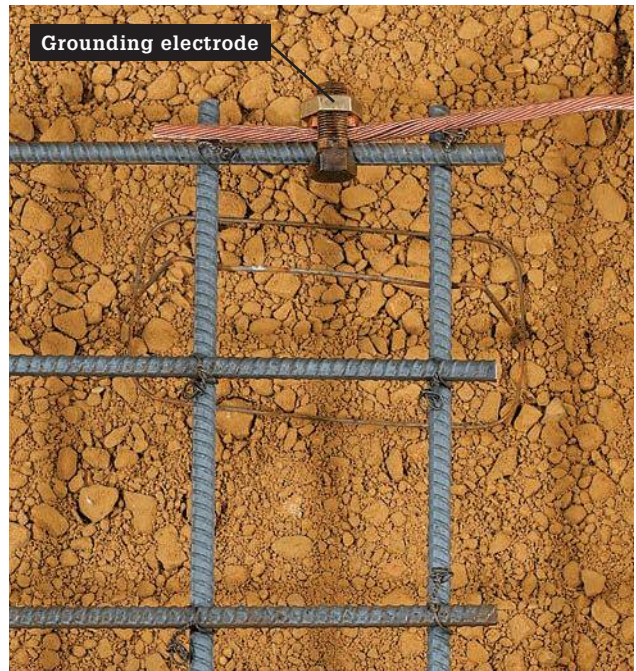A listed metal strap may be used to ground indoor communication wires such as telephone and cable TV if an intersystem bonding terminal is not available.



A piece of reinforcing bar encased in a concrete footing is a common grounding electrode in new construction. Called an ufer, the electrode must be No. 4 or larger rebar and at least 20 ft. long. (Shown prior to pouring concrete.)

Installing a Subpanel

Install circuit breaker subpanels if the main circuit breaker panel does not have enough open breaker slots for the new circuits you are planning. Subpanels serve as a second distribution center for connecting circuits. They receive power from a double-pole circuit breaker you install in the main circuit breaker panel.

If the main service panel is so full that there is no room for the double-pole subpanel breaker, you can reconnect some of the existing 120-volt circuits to special slimline breakers (photos below).

Plan your subpanel installation carefully, making sure your electrical service supplies enough power to support the extra load of the new subpanel circuits. Assuming your main service is adequate, consider installing an oversized subpanel breaker in the main panel to provide enough extra amps to meet the needs of future wiring projects.


Also consider the physical size of the subpanel, and choose one that has enough extra slots to hold circuits you may want to install later. The smallest panels have room for up to six single-pole breakers

(or three double-pole breakers), while the largest models can hold 20 single-pole breakers or more.


Subpanels often are mounted near the main circuit breaker panel. Or, for convenience, they can be installed close to the areas they serve, such as in a new room addition or a garage. In a finished room, a subpanel can be painted or housed in a decorative cabinet so it is less of a visual distraction. If it is covered, make sure the subpanel is easily accessible and clearly identified.

Tools & Materials ▶

| | |
|------------------|-----------------------------|
| Hammer | Cable clamps |
| Screwdriver | Three-wire NM cable |
| Circuit tester | Cable staples |
| Cable ripper | Double-pole circuit breaker |
| Combination tool | Circuit breaker subpanel |
| Screws | Slimline circuit breakers |

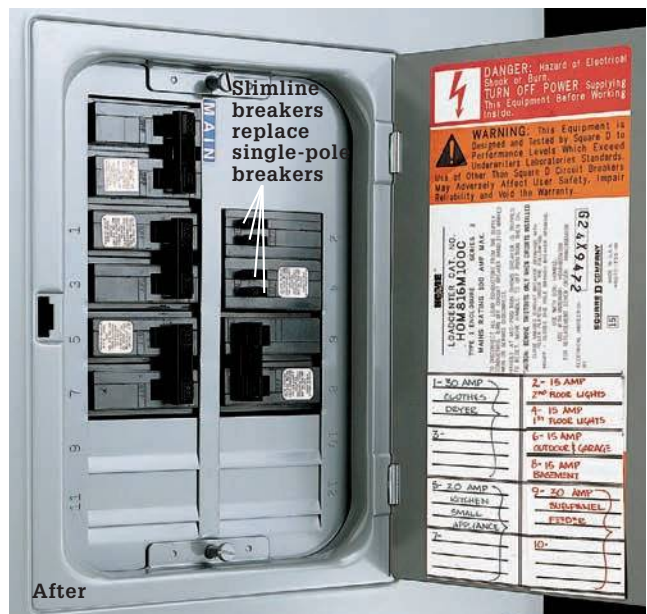

To conserve space in a service panel, you can replace single-pole breakers with slimline breakers. Slimline breakers take up half the space of standard breakers, allowing you to fit two circuits into one single slot on the service panel. In the service panel shown above, four single-pole 120-volt breakers were replaced with slimline breakers to provide the double opening needed for a 30-amp, 240-volt subpanel feeder breaker. Use slimline breakers (if your municipality allows them) with the same amp rating as the standard single-pole breakers you are removing, and make sure they are approved for use in your panel. If your municipality and panel allow slimline breakers, there may be restrictions on the quantity and location where they may be installed on the panel.

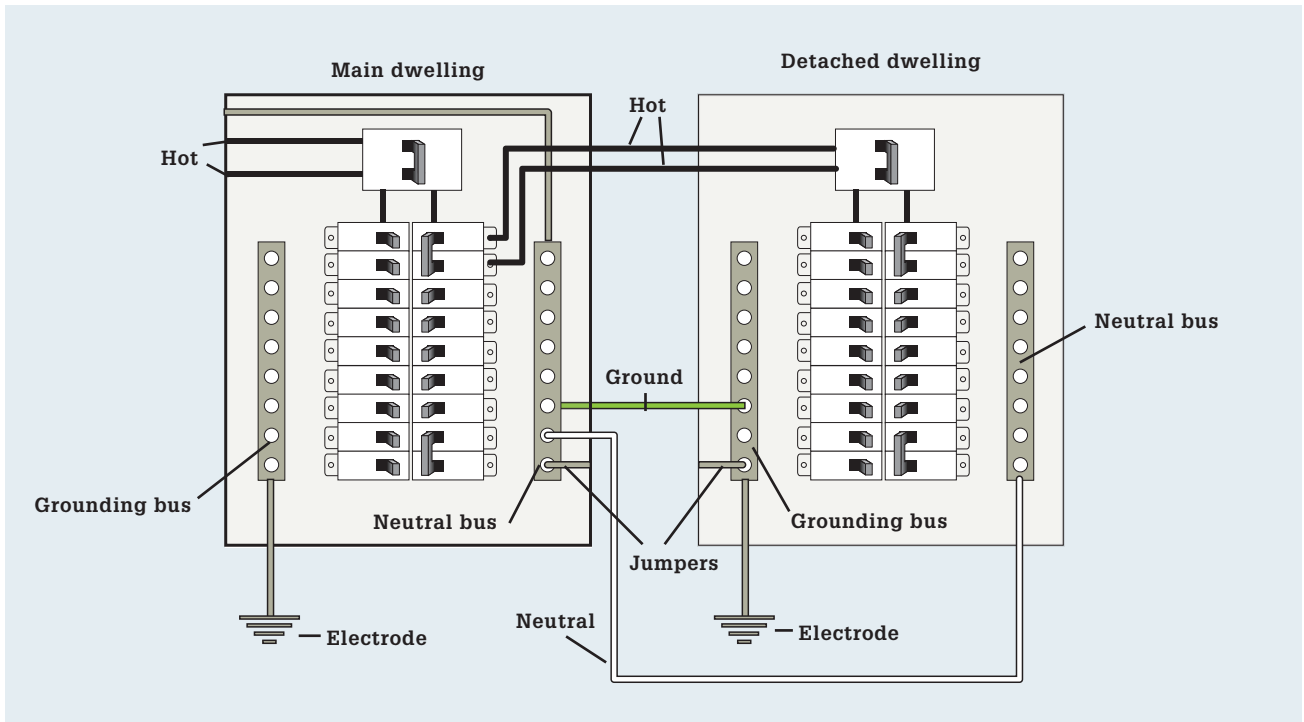

Wiring diagram for wiring a feeder from the main service panel to a subpanel in a separate building.


How to Install a Subpanel



Subpanels are subject to the same installation and clearance rules as service panels. The subpanel can be mounted to the sides of studs or to plywood attached between two studs. The panel shown here extends $\frac{1}{2}$ " past the face of studs so it will be flush with the finished wall surface.




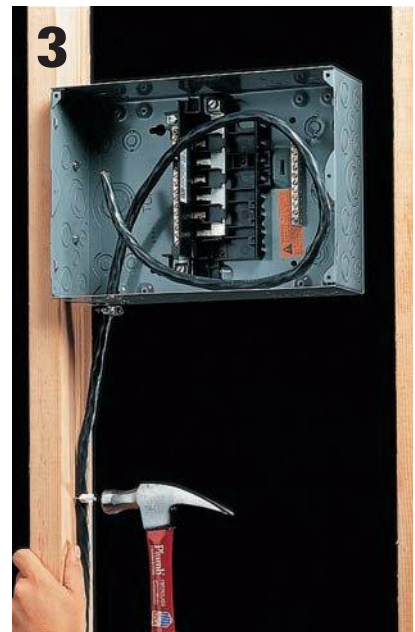Open a knockout in the subpanel using a screwdriver and hammer. Run the feeder cable from the main circuit breaker panel to the subpanel, leaving about 2 ft. of excess cable at each end.




Attach a cable clamp to the knockout in the subpanel. Insert the cable into the subpanel, and then anchor it to framing members within 8" of each panel and every 54" thereafter.


(continued)

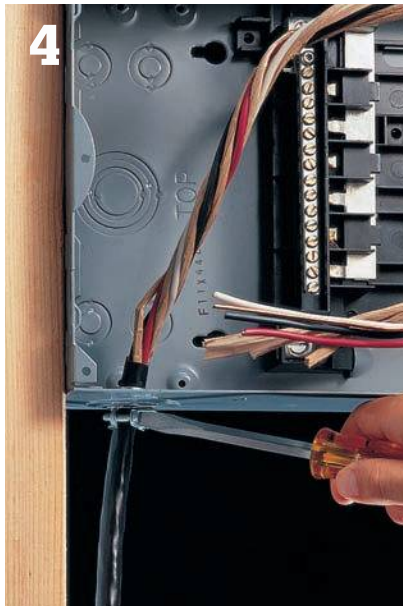

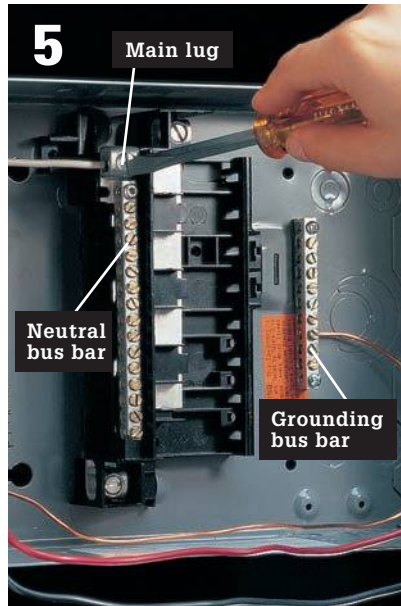
Strip away outer sheathing from the feeder cable using a cable ripper. Leave at least $\frac{1}{4}$ " of sheathing extending into the subpanel. Tighten the cable clamp screws so the cable is held securely, but not so tightly that the wire sheathing is crushed.



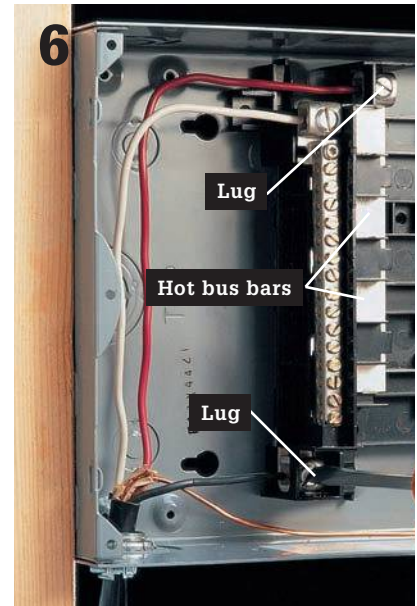Strip $\frac{1}{2}$ " of insulation from the white neutral feeder wire, and attach it to the main lug on the subpanel neutral bus bar. Connect the grounding wire to a setscrew terminal on the grounding bus bar. Fold excess wire around the inside edge of the subpanel.



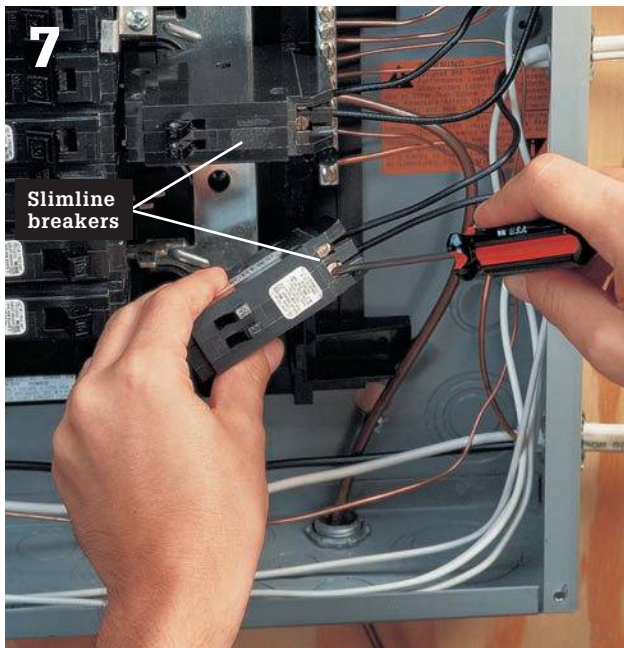
Strip away $\frac{1}{2}$ " of insulation from the red and the black feeder wires. Attach one wire to the main lug on each of the hot bus bars. Fold excess wire around the inside edge of the subpanel.




At the main circuit breaker panel, shut off the main circuit breaker, and then remove the coverplate and test for power. If necessary, make room for the double-pole feeder breaker by removing single-pole breakers and reconnecting the wires to slimline circuit breakers. Open a knockout for the feeder cable using a hammer and screwdriver. Note: some panels do not allow slimline breakers and some restrict where slimline breakers can be installed. Read the instructions on the panel cover.



Strip away the outer sheathing from the feeder cable so that at least $\frac{1}{4}$ " of sheathing will reach into the main service panel. Attach a cable clamp to the cable, and then insert the cable into the knockout, and anchor it by threading a locknut onto the clamp. Tighten the locknut by driving a screwdriver against the lugs. Tighten the clamp screws so the cable is held securely, but not so tightly that the cable sheathing is crushed.

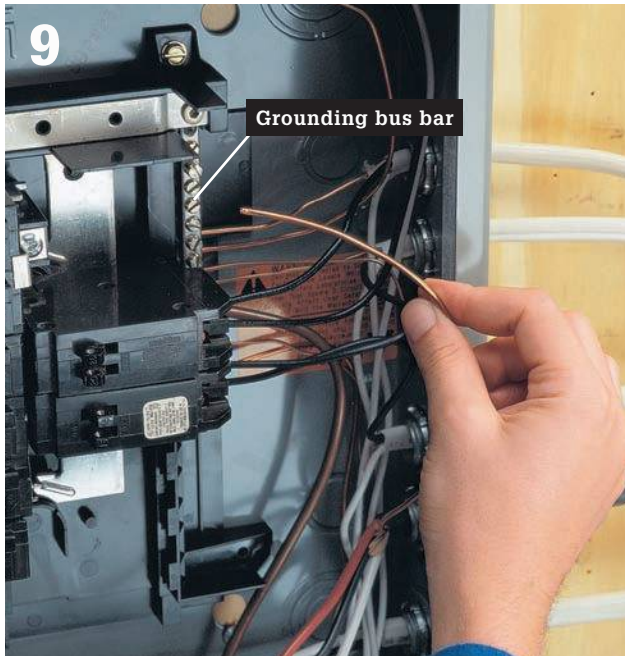

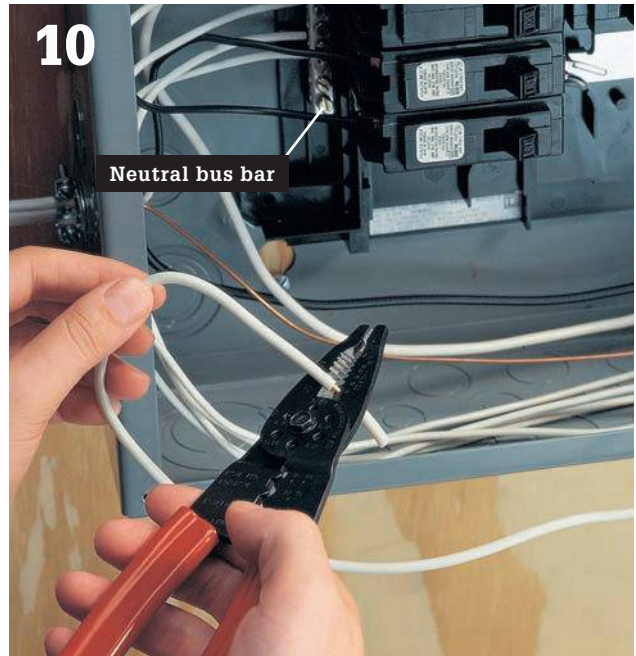Bend the bare copper wire from the feeder cable around the inside edge of the main circuit breaker panel, and connect it to one of the setscrew terminals on the grounding bus bar.



Strip away ½" of insulation from the white feeder wire. Attach the wire to one of the setscrew terminals on the neutral bus bar. Fold excess wire around the inside edge of the service panel.



Strip ½" of insulation from the red and the black feeder wires. Attach one wire to each of the setscrew terminals on the double-pole feeder breaker. *Note: If your subpanel arrived with a preinstalled grounding screw in the panel back, remove and discard it.*



Hook the end of the feeder circuit breaker over the guide hooks on the panel, and then push the other end forward until the breaker snaps onto the hot bus bars (follow manufacturer's directions). Fold excess wire around the inside edge of the circuit breaker panel.



If necessary, open two tabs where the double-pole feeder breaker will fit, and then reattach the cover plate. Label the feeder breaker on the circuit index. Turn the main breaker on, but leave the feeder breaker off until all subpanel circuits have been connected and inspected.

Baseboard Heaters

Baseboard heaters are a popular way to provide additional heating for an existing room or primary heat to a converted attic or basement.

Heaters are generally wired on a dedicated 240-volt circuit controlled by a thermostat. Several heaters can be wired in parallel and controlled by a single thermostat (see circuit map 15, page 39).

Baseboard heaters are generally surface-mounted without boxes, so in a remodeling situation, you only need to run cables before installing wallboard. Be sure to mark cable locations on the floor before installing drywall. Retrofit installations are also not difficult. You can remove existing baseboard and run new cable in the space behind. Baseboard heaters (and other heating equipment) get very hot and can ignite nearby combustible materials. Maintain the manufacturers recommended distance between the heater and materials such as curtains, blinds, and wood.


Tools & Materials ▶

- Drill/driver
- Wire stripper
- Cable ripper
- Wallboard saw
- Baseboard heater or heaters
- 240-thermostat (in-heater or in-wall)
- 12/2 NM cable
- Electrical tape
- Basic wiring supplies



Baseboard heaters can provide primary or supplemental heat for existing rooms or additions. Install heaters with clear space between the heater and the floor.


Baseboard Thermostats

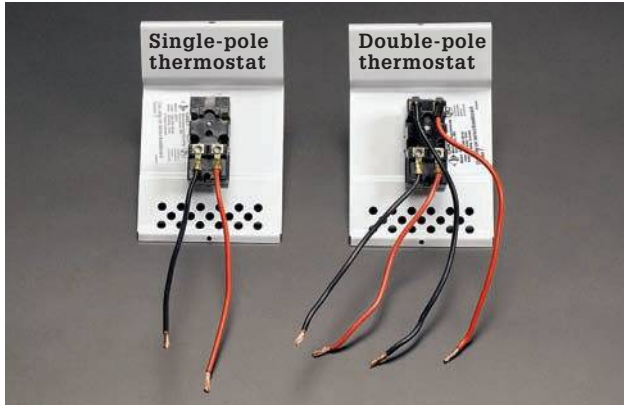

Single-pole and double-pole thermostats work in a similar manner, but double-pole models are safer. The single-pole model will open the circuit (causing shutoff) in only one leg of the power service. Double-pole models have two sets of wires to open both legs, lessening the chance that a person servicing the heater will contact a live wire.



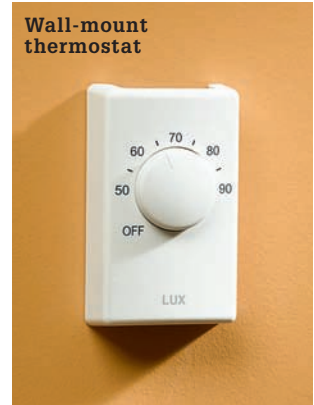In-heater and wall-mount are the two types of baseboard thermostats you can choose from. If you are installing multiple heaters, a single wall-mount thermostat is more convenient. Individual in-heater thermostats give you more zone control, which can result in energy savings.



How Much Heater Do You Need? ▶

If you don't mind doing a little math, determining how many lineal feet of baseboard heater a room requires is not hard.

1. Measure the area of the room in square feet (length × width): _____
2. Multiply the area by 10 to get the baseline minimum wattage: _____
3. Add 5% for each newer window or 10% for each older window: _____
4. Add 10% for each exterior wall in the room: _____
5. Add 10% for each exterior door: _____
6. Add 10% if the space below is not insulated: _____


7. Add 20% if the space above is not well insulated: _____
8. Add 10% if ceiling is more than 8 ft. high: _____
9. Total of the baseline wattage plus all additions: _____
10. Divide this number by 250 (the wattage produced per foot of standard baseboard heater): _____
11. Round up to a whole number. This is the minimum number of feet of heater you need. _____

Note: It is much better to have more feet of heater than is required than fewer. Having more footage of heater does not consume more energy; it does allow the heaters to work more efficiently.


Planning Tips for Baseboard Heaters ▶

- Baseboard heaters require a dedicated circuit. A 20-amp, 240-volt circuit of 12-gauge copper wire will power up to 16 ft. of heater.
- Do not install a heater beneath a wall receptacle. Cords hanging down from the receptacle are a fire hazard.
- Do not mount heaters directly on the floor. You should maintain at least 1" of clear space between the baseboard heater and the floor covering.
- Installing heaters directly beneath windows is a good practice.
- Locate wall thermostats on interior walls only, and do not install directly above a heat source.

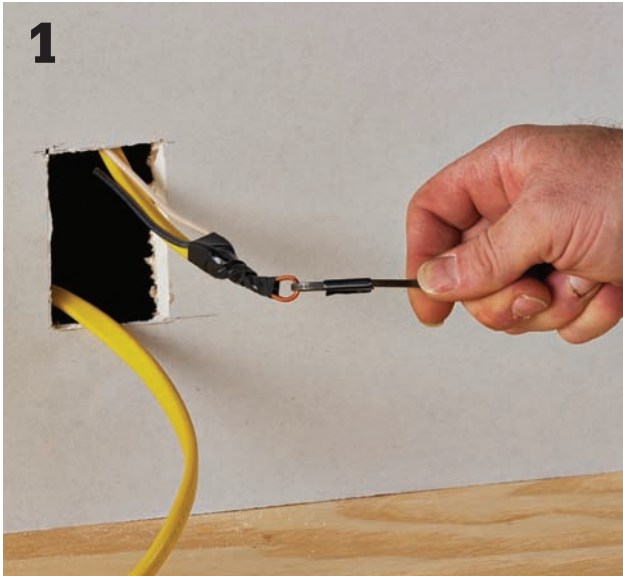How to Install a 240-Volt Baseboard Heater



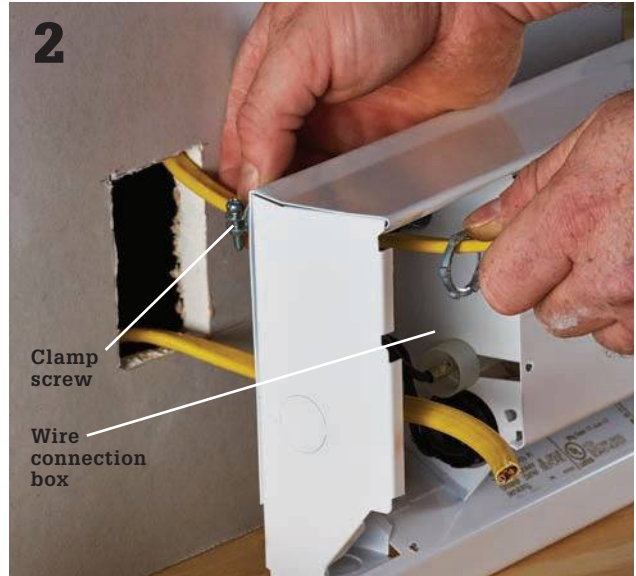
1 **At the heater locations,** cut a small hole in the drywall 3" to 4" above the floor. Pull 12/2 NM cables through the first hole: one from the thermostat, the other to the next heater. Pull all the cables for subsequent heaters. Middle-of-run heaters will have two cables, while end-of-run heaters have only one cable. (See also circuit map 15, page 39.)



2 **Remove the cover on the wire connection box.** Open a knockout for each cable that will enter the box, and then feed the cables through the cable clamps and into the wire connection box. Attach the clamps to the wire connection box, and tighten the clamp screws until the cables are gripped firmly.



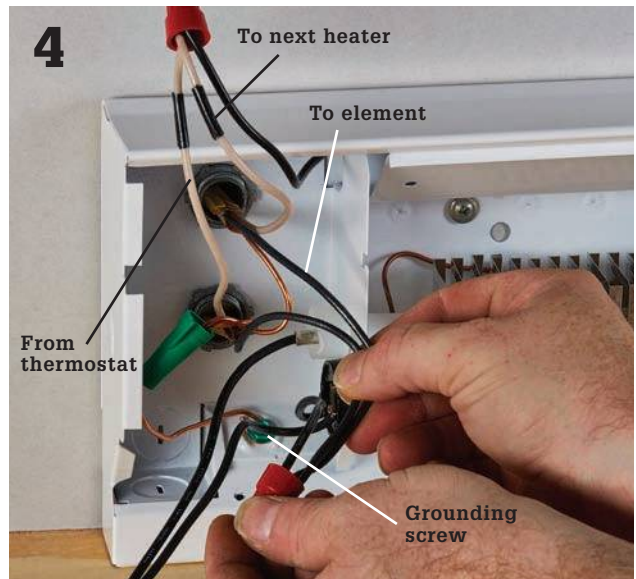3 **Anchor the heater against wall** about 1" off floor by driving flathead screws through the back of the housing and into studs. Strip away cable sheathing so at least 1/2" of sheathing extends into the heater. Strip 3/4" of insulation from each wire using a combination tool.



4 **Make connections to the heating element** if the power wires are coming from a thermostat or another heater controlled by a thermostat. See the next page for other wiring schemes. Connect the white circuit wires to one of the wire leads on the heater. Tag white wires with black tape to indicate they are hot. Connect the black circuit wires to the other wire lead. Connect a grounding pigtail to the green grounding screw in the box, and then join all grounding wires with a wire connector. Reattach the cover.



One heater with end-cap thermostat.

Run both power leads (black plus tagged neutral) into the connection box at either end of the heater. If installing a single-pole thermostat, connect one power lead to one thermostat wire and connect the other thermostat wire, to one of the heater leads. Connect the other hot LINE wire to the other heater lead. If you are installing a double-pole thermostat, make connections with both legs of the power supply.



Multiple heaters.

At the first heater, join both hot wires from the thermostat to the wires leading to the second heater in line. Be sure to tag all white neutrals hot. Twist copper ground wires together and pigtail them to the grounding screw in the baseboard heater junction box. This parallel wiring configuration ensures that power flow will not be interrupted to the downstream heaters if an upstream heater fails.



Wall-mounted thermostat.

If installing a wall-mounted thermostat, the power leads should enter the thermostat first and then be wired to the individual heaters singly or in series. Hookups at the heater are made as shown in step 4. Be sure to tag the white neutral as hot in the thermostat box as well as in the heater box.

Wall Heaters

Installing a wall heater is an easy way to provide supplemental heat to a converted attic or basement without expanding an existing HVAC system.

Wall heaters are easy to install during a remodel (most have a separate can assembly that you attach to the framing before the drywall is installed). They can also be retrofitted.

Most models available at home centers use 120-volt current (shown below), but 240-volt models are also available.


Tools & Materials ▶

| | |
|------------------|--------------------------|
| Drywall saw | Wire connectors |
| Drill | Wall heater |
| Fish tape | Thermostat (optional) |
| Combination tool | Wallboard saw |
| Screwdrivers | |
| 12/2 NM cable | |



Wall heaters are an easy-to-install way to provide supplemental heat. Some models have built-in thermostats, while others can be controlled by a remote thermostat.

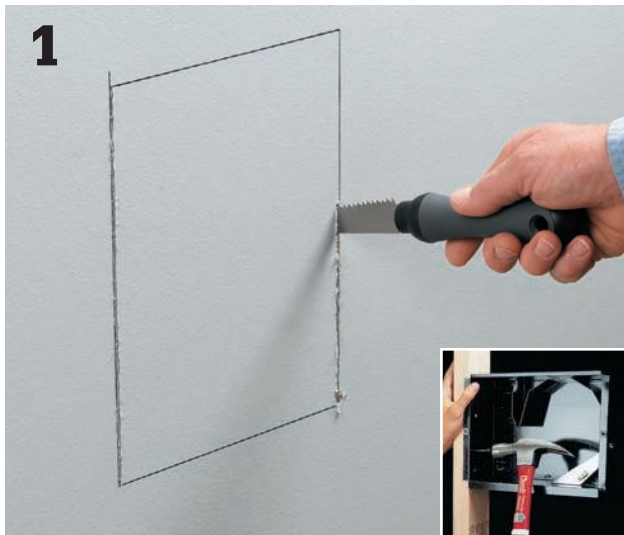How to Install a Wall Heater in a Finished Wall



1 **Make an opening in the wall** for the heater. Use a stud finder to locate a stud in the area where you want to install the heater. Mark the opening for the heater according to the manufacturer's guidelines so that one side of the heater sits flush with a stud. Pay attention to clearance requirements. Cut the opening with a wallboard saw. If the wall is open, install the heater can before hanging drywall (inset).



2 **Turn power off, and test for power.** Pull 12/2 NM cable from the main panel to the wall opening. If the heater is controlled by a separate thermostat, pull cable to the thermostat, and then run another cable from the thermostat to the heater location.



3
Disconnect and remove the motor unit from the heater can. Remove a knockout from the can, and route the cable into the can.




4
Install the can in the opening. Secure the cable with a clamp, leaving 8" to 12" of cable exposed. Attach the can to the framing as directed by the manufacturer.



5
Wire the heater. Connect the black circuit wire to one of the black heater leads. Connect the white circuit wire to the other lead. Connect the grounds.



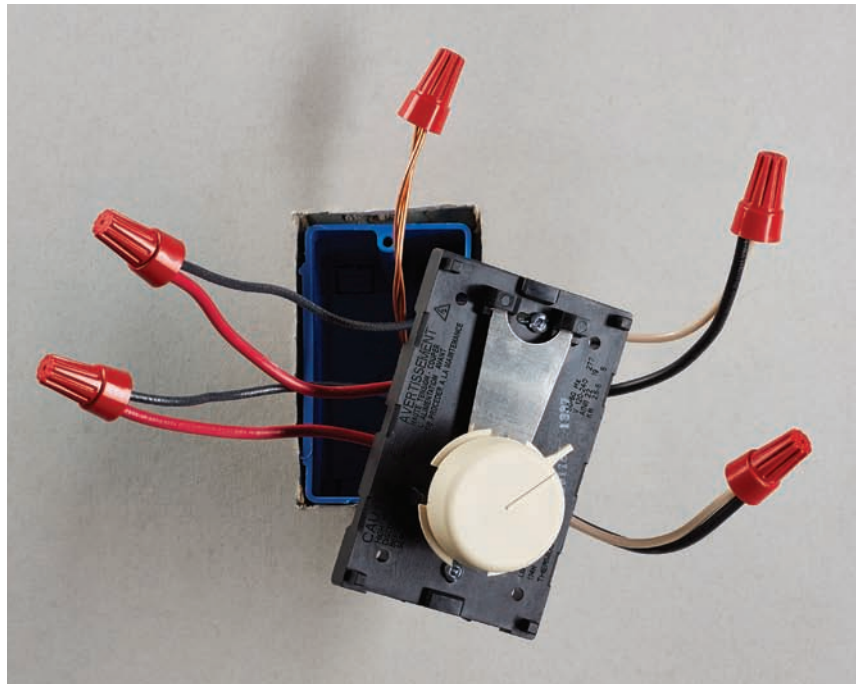6
Secure the heater unit in the can as directed by the manufacturer. Reconnect the motor if necessary. Attach the grill and thermostat knob as directed. Connect the new circuit breaker at the main panel.



Variation: Connect a thermostat to control a wall heater. Some wall heaters do not use built-in thermostats. Install a thermostat in the heater circuit before the wall heater. Connect the black and the white wires coming from the main panel to the red leads on the thermostat. Connect the wires going to the heater to the black leads on the thermostat. Connect the grounds.

Backup Power Supply

Installing a backup generator is an invaluable way to prepare your family for emergencies. The simplest backup power system is a portable gas-powered generator and an extension cord or two. A big benefit of this approach is that you can run a refrigerator and a few worklights during a power outage with a tool that can also be transported to remote job sites or on camping trips when it's not doing emergency backup duty. This is also the least expensive way to provide some backup power for your home. You can purchase a generator at most home centers and be up and running in a matter of hours. If you take this approach, it is critically important that you make certain any loads being run by your generator are disconnected from the utility power source.

The next step up is to incorporate a manual transfer switch for your portable generator. Transfer switches are permanently hardwired to your service panel. They are mounted on either the interior or the exterior of your house between the generator and the service panel. You provide a power feed from the generator into the switch. The switch is wired to selected essential circuits in your house, allowing you to power lights, furnace blowers, and other loads that

can't easily be run with an extension cord. But perhaps the most important job a transfer switch performs is to disconnect the utility power. If the inactive utility power line is attached to the service panel, "backfeed" of power from your generator to the utility line can occur when the generator kicks in. This condition could be fatal to line workers who are trying to restore power. The potential for backfeed is the main reason many municipalities insist that only a licensed electrician hook up a transfer switch. Using a transfer switch not installed by a professional may also void the warranty of the switch and the generator.

Automatic transfer switches turn on the generator and switch off the utility supply when they detect a significant drop in line voltage. They may be installed with portable generators, provided the generator is equipped with an electric starter.

Large standby generators that resemble central air conditioners are the top of the line in backup power supply systems. Often fueled by home natural gas lines or propane tanks that offer a bottomless fuel source, standby generators are made in sizes with as much as 20 to 40 kilowatts of output—enough to supply all of the power needs of a 5,000-sq.-ft. home.



Generators have a range of uses.

Large hard-wired models can provide instant emergency power for a whole house. Smaller models (below) are convenient for occasional short-term backup as well as job sites or camping trips.



Options for Backup Generators



A 2,000- to 5,000-watt gas-powered generator and a few extension cords can power lamps and an appliance or two during shorter-term power outages. Appliances must not be connected to household wiring and the generator simultaneously. Never plug a generator into an outlet. Never operate a generator indoors. Run extension cords through a garage door.




A permanent transfer switch patches electricity from a large portable generator through to selected household circuits via an inlet at your service panel (inset), allowing you to power hardwired fixtures and appliances with the generator.



For full, on-demand backup service, install a large standby generator wired through to an automatic transfer panel. In the event of a power outage, the household system instantly switches to the generator.

A Typical Backup System

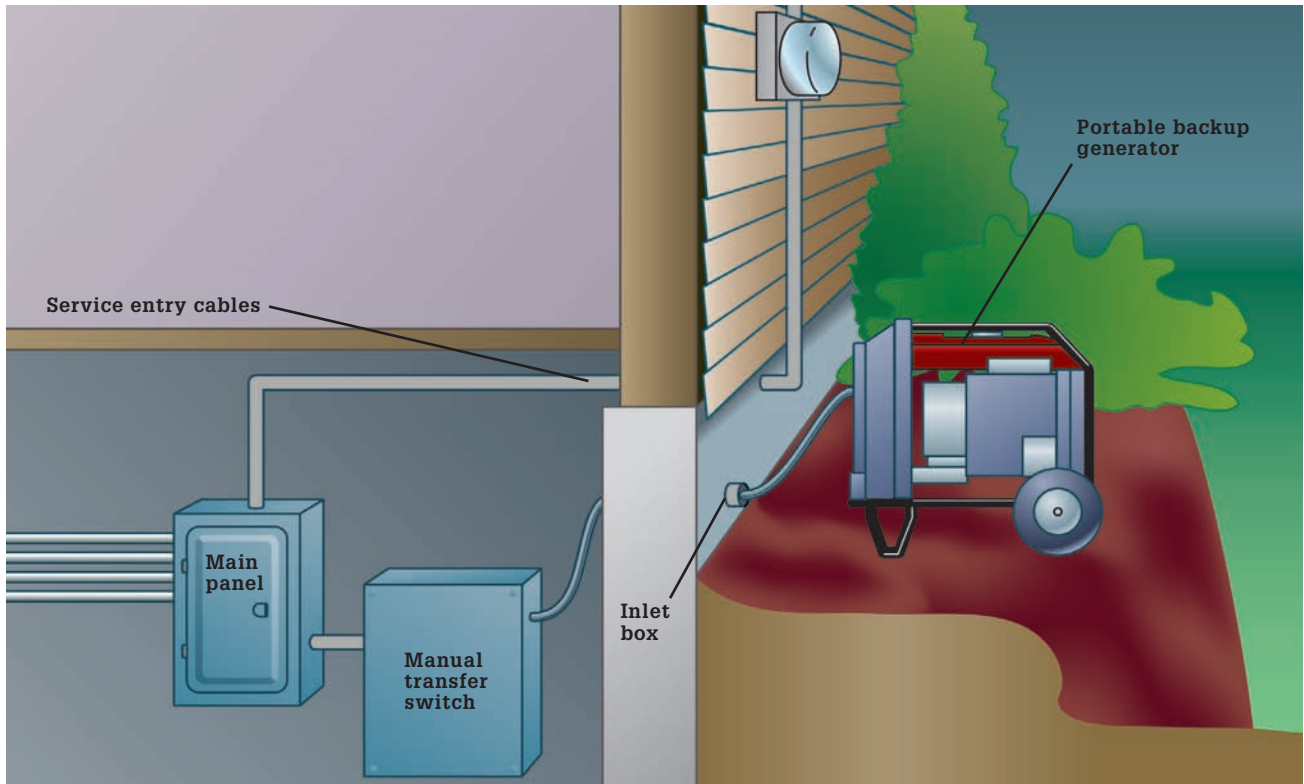

Backup generators supply power to a manual transfer switch, which disconnects the house from the main service wires and routes power from the generator through selected household circuits.

Choosing a Generator

Choosing a generator for your home's needs requires a few calculations. The chart below gives an estimate of the size of generator typically recommended for a house of a certain size. You can get a more accurate number by adding up the power consumption (the watts) of all the circuits or devices to be powered by a generator. It's also important to keep in mind that, for most electrical appliances, the amount of power required at the moment you flip the ON switch is greater than the number of watts required to keep the device running. For instance, though an air conditioner may run on 15,000 watts of power, it will require a surge of 30,000 watts at startup (the power range required to operate an appliance is usually listed somewhere on the device itself). These two numbers are called run watts and surge watts. Generators are typically sold according to run watts (a 5,000-watt generator can sustain 5,000 watts). They are also rated for a certain number of surge watts (a 5,000-watt generator may be able to produce a surge of

10,000 watts). If the surge watts aren't listed, ask, or check the manual. Some generators can't develop many more surge watts than run watts; others can produce twice as much surge as run wattage.

It's not necessary to buy a generator large enough to match the surge potential of all your circuits (you won't be turning everything on simultaneously), but surge watts should factor in your purchasing decision. If you will be operating the generator at or near capacity, it is also a wise practice to stagger startups for appliances.

| SIZE OF HOUSE (IN SQUARE FEET) | RECOMMENDED GENERATOR SIZE (IN KILOWATTS) |
|-----------------------------------|--|
| Up to 2,700 | 5–11 |
| 2,701–3,700 | 14–16 |
| 3,701–4,700 | 20 |
| 4,701–7,000 | 42–47 |

Types of Transfer Switches



Cord-connected transfer switches (shown above) are hard-wired to the service panel (in some cases they're installed after the service panel and operate only selected circuits). These switches contain a male receptacle for a power supply cord connected to the generator. Automatic transfer switches (not shown) detect voltage drop-off in the main power line and switch over to the emergency power source.



When using a cord-connected switch, consider mounting an inlet box to the exterior wall. This will allow you to connect a generator without running a cord into the house.

Generator Tips ▶



If you'll need to run sensitive electronics such as computers or home theater equipment, look for a generator with power inverter technology that dispenses "clean power" with a stable sine wave pattern.



A generator that will output 240-volt service is required to run most central air conditioners. If your generator has variable output (120/240) make sure the switch is set to the correct output voltage.

Running & Maintaining a Backup System

Even with a fully automatic standby generator system fueled by natural gas or propane, you will need to conduct some regular maintenance and testing to make sure all systems are ready in the event of power loss. If you're depending on a portable generator and extension cords or a standby generator with a manual transfer switch, you'll also need to know the correct sequence of steps to follow in a power emergency. Switches and panels also need to be tested on a regular basis, as directed in your owner's manual. And be sure that all switches (both interior and exterior) are housed in an approved enclosure box.



Pull-cord starter

Smaller portable generators often use pull-cords instead of electric starters.

ANATOMY OF A PORTABLE BACKUP GENERATOR



Portable generators use small gasoline engines to generate power. A built-in electronics panel sets current to AC or DC and the correct voltage. Most models will also include a built-in circuit breaker to protect the generator from damage in the event it is connected to too many loads. Better models include features like built-in GFCI protection. Larger portable generators may also feature electric starter motors and batteries for push-button starts.

Operating a Manual System During an Outage



Plug the generator in at the inlet box. Make sure the other end of the generator's outlet cord is plugged into the appropriate outlet on the generator (120-volt or 120/240-volt AC) and the generator is switched to the appropriate voltage setting.



Start the generator with the pull-cord or electric starter (if your generator has one). Let the generator run for several minutes before flipping the transfer switch.



Flip the manual transfer switch. Begin turning on loads one at a time by flipping breakers on, starting with the ones that power essential equipment. Do not overload the generator or the switch, and do not run the generator at or near full capacity for more than 30 minutes at a time.

Maintaining & Operating an Automatic Standby Generator



If you choose to spend the money and install a dedicated standby generator of 10,000 watts or more and operate it through an automatic transfer switch or panel, you won't need to lift a hand when your utility power goes out. The system kicks in by itself. However, you should follow the manufacturer's instructions for testing the system, changing the oil, and running the motor periodically.

Installing a Transfer Switch

A transfer switch is installed next to the main service panel to override the normal electrical service with power from a backup generator during a power outage. Manual transfer switches require an operator to change the power source, while automatic switches detect the loss of power, start the back-up generator, and switch over to the backup power feed. Because the amount of electricity created by a backup generator is not adequate to power all of the electrical circuits in your house, you'll need to designate a few selected circuits to get backup current (see page 81).



A manual transfer switch connects emergency circuits in your main panel to a standby generator.

Tools & Materials ▶

| | |
|----------------|------------------------|
| Circuit tester | Level |
| Drill/driver | Manual transfer switch |
| Screwdrivers | Screws |
| Hammer | Wire connectors |
| Wire cutters | (yellow) |
| Cable ripper | Standby power |
| Wire strippers | generator |



One flip of a switch reassigns the power source for each critical circuit so your backup generator can keep your refrigerator, freezer, and important lights running during an outage of utility power.

Selecting Backup Circuits ▶

Before you purchase a backup generator, determine which loads you will want to power from your generator in the event of a power loss. Generally you will want to power your refrigerator, freezer, and maybe a few lights. Add up the running wattage ratings of the appliances you will power up to determine how large your backup generator needs to be. Because the startup wattage of many appliances is higher than the running wattage, avoid starting all circuits at the same time—it can cause an overload situation with your generator. Here are some approximate running wattage guidelines (see page 132 to 137 for more information on calculating electrical loads):

- Refrigerator: 750 watts
- Forced air furnace: 1,100 to 1,500 watts
- Incandescent lights: 60 watts per bulb (CFL and LED lights use less wattage)
- Sump pump: 800 to 1,000 watts
- Garage door opener: 550 to 1,100 watts
- Television: 300 watts

Add the wattage values of all the loads you want to power, and multiply the sum by 1.25. This will give you the minimum wattage your generator must produce. Portable standby generators typically output 5,000 to 7,500 watts. Most larger, stationary generators can output 10,000 to 20,000 watts (10 to 20 kilowatts).

How to Install a Manual Transfer Switch




1 Turn off the main power breaker in your electrical service panel. CAUTION: The terminals where power enters the main breakers will still be energized.




2 Determine which household circuits are critical for emergency usage during a power outage. Typically this will include the refrigerator, freezer, furnace, and at least one light or small appliance circuit.


(continued)

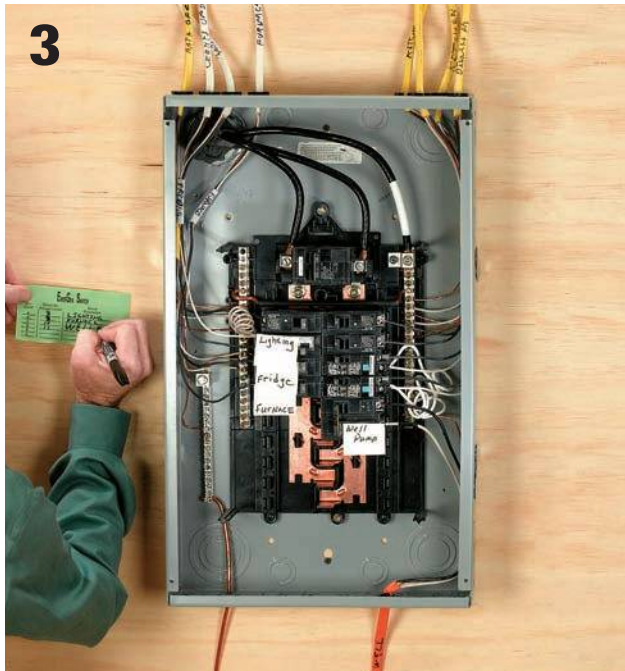


Match your critical circuits with circuit inlet on your pre-wired transfer switch. Try to balance the load as best you can in the transfer switch: For example, if your refrigerator is on the leftmost switch circuit, connect your freezer to the circuit farthest to the right. Double-pole (240-volt) circuits will require two 120-volt circuit connections. Also make sure that 15-amp and 20-amp circuits are not mismatched with one another.

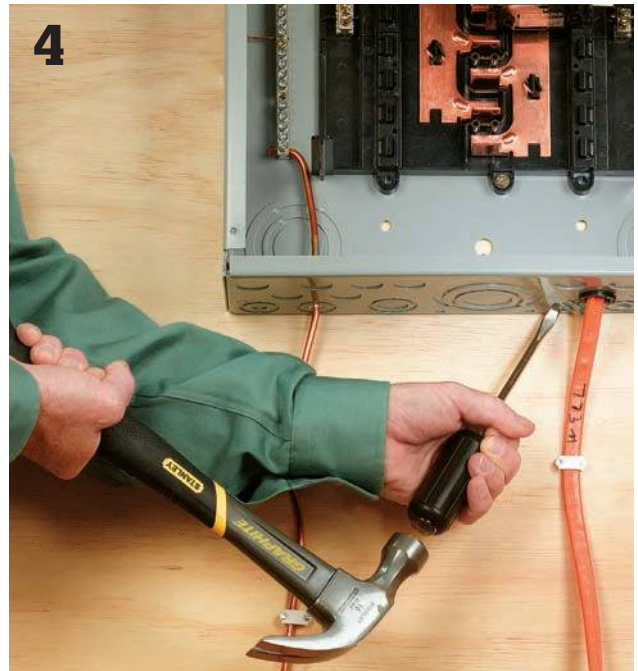

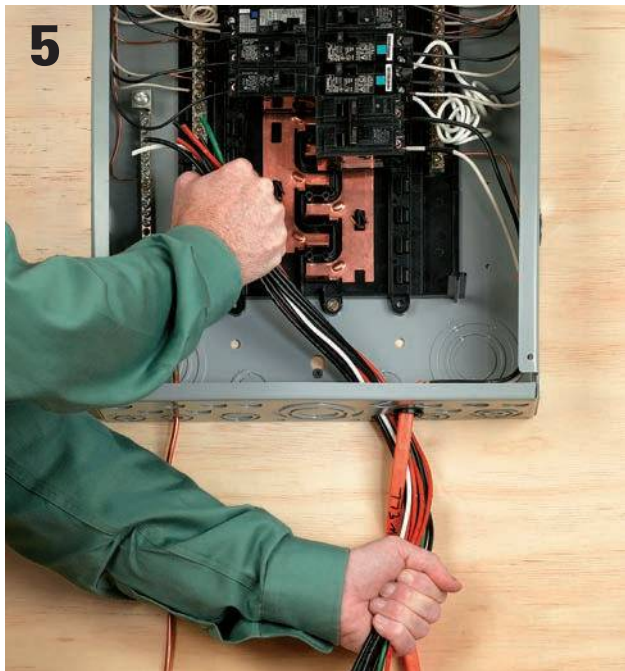Select and remove a knockout at the bottom of the main service panel box. Make sure to choose a knockout that is sized to match the connector on the flexible conduit coming from the transfer switch.



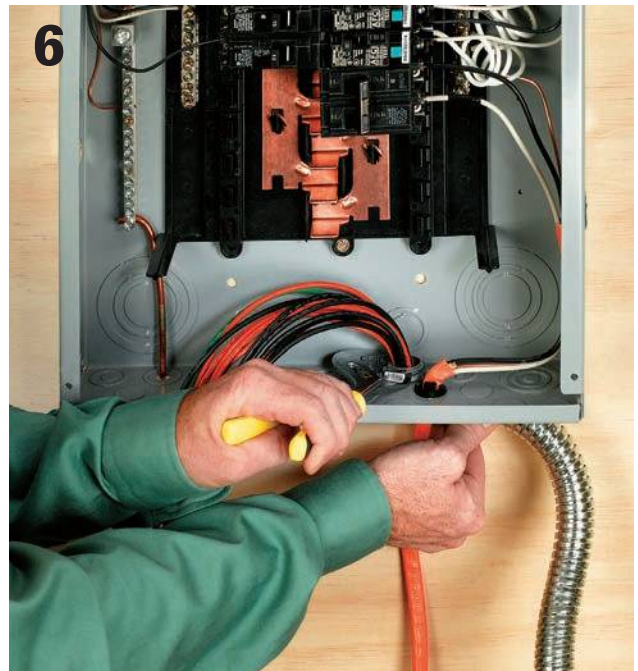
Feed the wires from the transfer switch into the knockout hole, taking care not to damage the insulation. You will note that each wire is labeled according to which circuit in the switch box it feeds.




Secure the flexible conduit from the switch box to the main service panel using a locknut and a bushing where required.



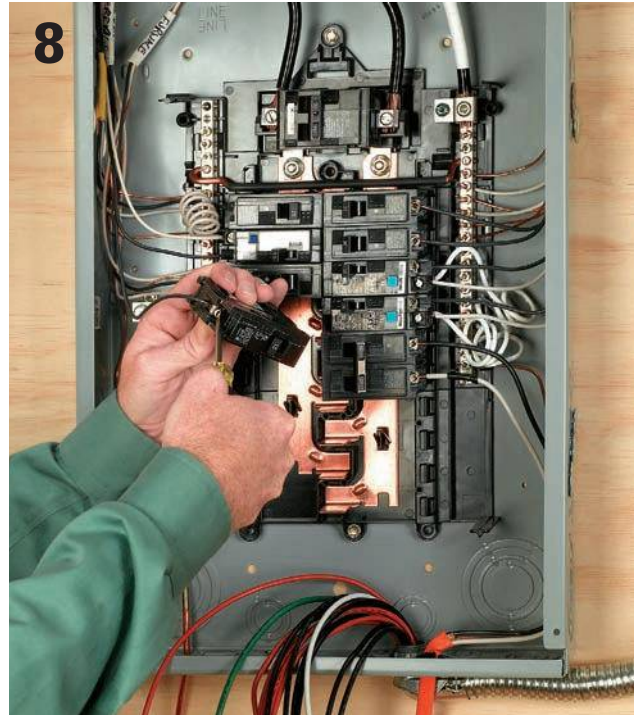
7 Attach the transfer switch box to the wall so the closer edge is about 18" away from the center of the main service panel. Use whichever connectors make sense for your wall type.



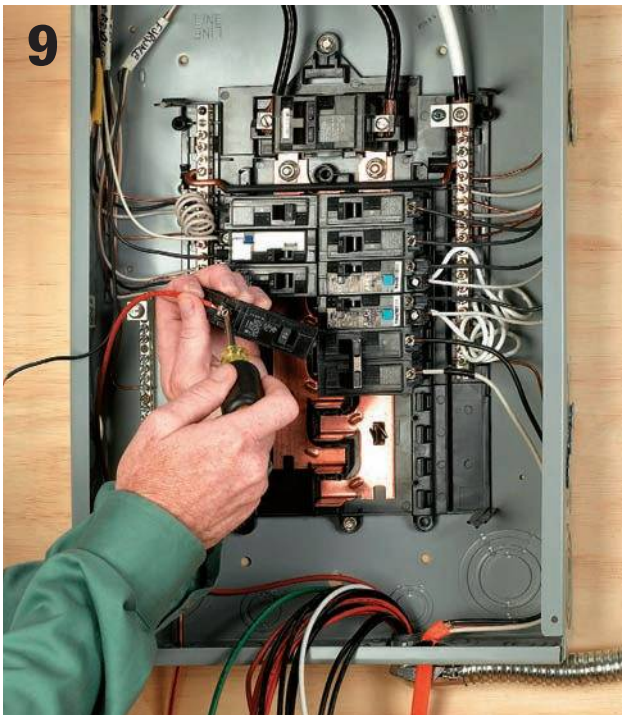8 Remove the breaker for the first critical circuit from the main service panel box, and disconnect the hot wire lead from the lug on the breaker.




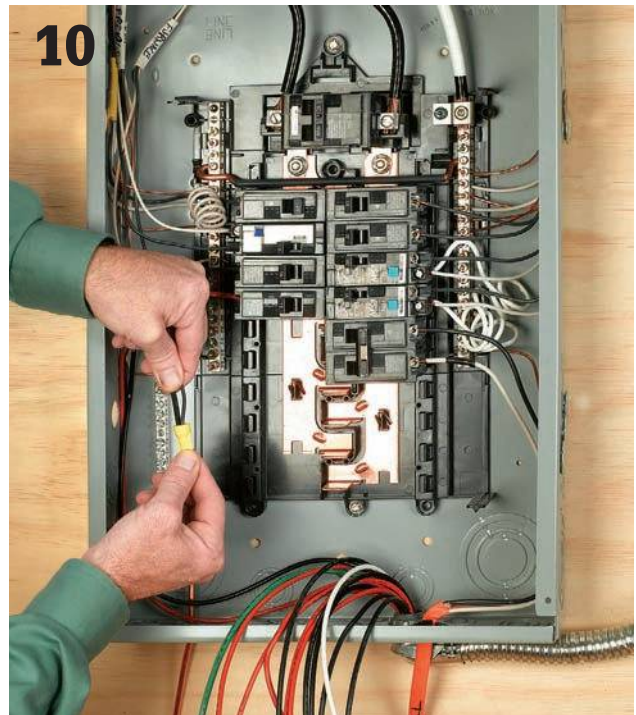9 Locate the red wire for the switch box circuit that corresponds to the circuit you've disconnected. Attach the red wire to the breaker you've just removed, and then reinstall the breaker.




10 Locate the black wire from the same transfer switch circuit, and twist it together with the old feed wire, using a yellow wire connector. Tuck the wires neatly out of the way at the edges of the box. Proceed to the next circuit, and repeat the process.


(continued)

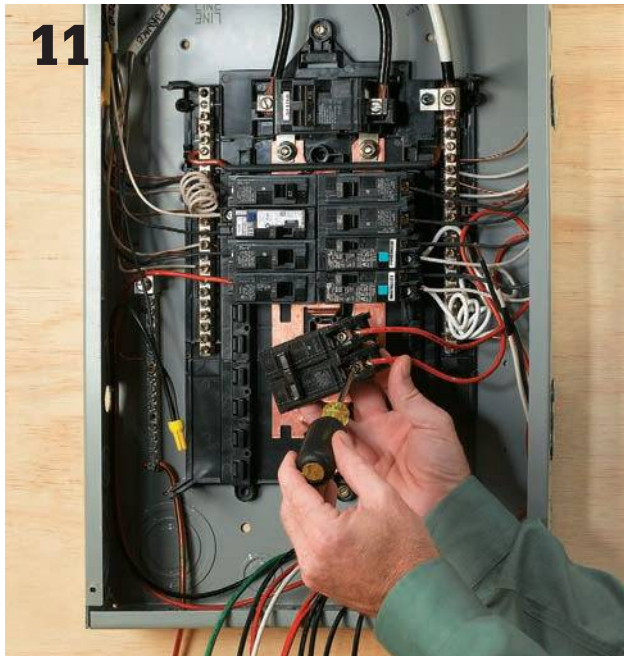

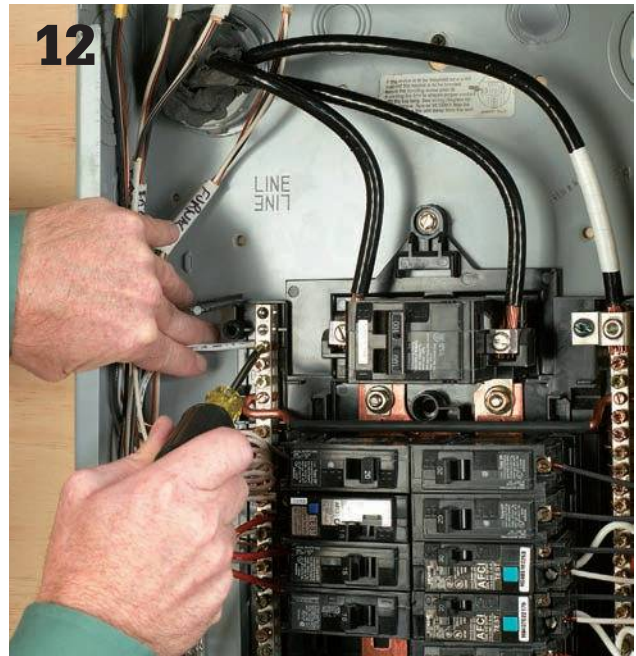11 If any of your critical circuits are 240-volt circuits, attach the red leads from the two transfer switch circuits to the double-pole breaker. The two circuits originating in the transfer switch should be next to one another, and their switches should be connected with a handle tie. If you have no 240-volt circuits you may remove the preattached handle tie and use the circuits individually.



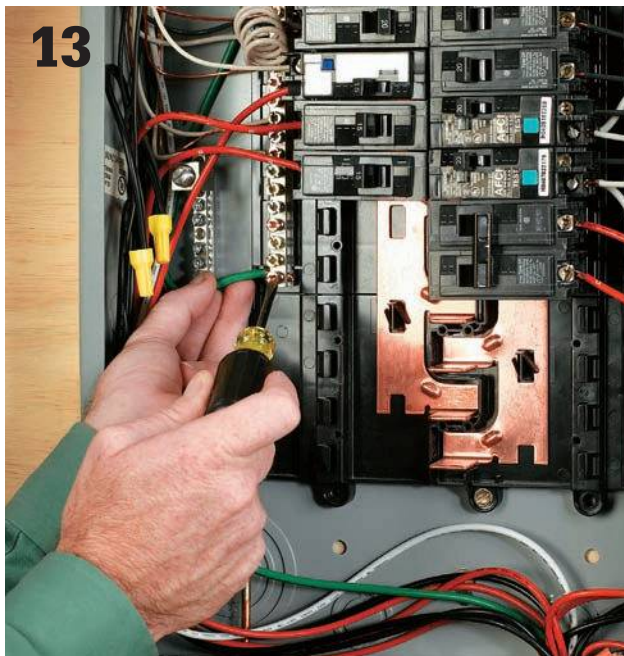12 Once you have made all circuit connections, attach the white neutral wire from the transfer switch to an opening in the neutral bus bar of the main service panel.



13 Attach the green ground wire from the transfer switch to an open port on the grounding bar in your main service panel. This should complete the installation of the transfer switch. Replace the cover on the service panel box, and make sure to fill in the circuit map on your switch box.



14 Begin testing the transfer switch by making sure all of the switches on it are set to the LINE setting. The power should still be OFF at the main panel breakers.

Standby Generators ▶



Make sure your standby generator is operating properly and has been installed professionally. See page 76 for information on choosing a generator that is sized appropriately for your needs.

15



Before turning your generator on, attach the power cord from the generator to the switch box. Never attach or detach a generator cord with the generator running. Turn your standby power generator on, and let it run for a minute or two.

16



Flip each circuit switch on the transfer switch box to GEN, one at a time. Try to maintain balance by moving back and forth from circuits on the left and right side. Do not turn all circuits on at the same time. Observe the onboard wattage meters as you engage each circuit, and try to keep the wattage levels in balance. When you have completed testing the switch, turn the switches back to LINE, and then shut off your generator.

Outbuildings

Nothing improves the convenience and usefulness of an outbuilding more than electrifying it. Running a new underground circuit from your house to an outbuilding lets you add receptacles and light fixtures both inside the outbuilding and on its exterior. If you run power to an outbuilding, you are required to install at least one receptacle.

Adding one or two 120-volt circuits is not complicated, but every aspect of the project is strictly governed by local building codes. Therefore, once you've mapped out the job and have a good idea of what's involved, visit your local building department to discuss your plans and obtain a permit for the work.

This project demonstrates standard techniques for running a circuit cable from the house exterior to a shed, plus the wiring and installation of devices inside the shed. To add a new breaker and make the final circuit connections to your home's main service panel, see page 52. If you run power to an outbuilding, you are required to install at least one receptacle.

First, determine how much current you will need. For basic electrical needs, such as powering a standard

light fixture and small appliances or power tools, a 120-volt, 15-amp circuit should be sufficient. A small workshop may require one or two 120-volt, 20-amp circuits. If you need any 240-volt circuits or more than two 120-volt, 20-amp circuits, you will need to install at least a 60-amp subpanel with appropriate feeder wires. Installing a subpanel in an outbuilding is similar to installing one inside your home, but there are some important differences.

You may use #14 copper wire for one 120-volt, 15-amp circuit or #12 copper wire for one 120-volt, 20-amp circuit. Use #10 copper wire for two 120-volt, 20-amp circuits. Also, if the shed is more than 150 ft. away from the house, you may need heavier-gauge cable to account for voltage drop.


Most importantly, don't forget to call before you dig. Have all utility and service lines on your property marked even before you make serious project plans. This is critical for your safety of course, and it may affect where you can run the circuit cable.



Adding an electrical circuit to an outbuilding such as this shed greatly expands the activities the building will support and is also a great benefit for home security.

Tools & Materials ▶

| | | | |
|---|--|--|---------------------------------------|
| Spray paint | Hacksaw | Single-pole switches (2) | THNN wire (12 gauge) |
| Trenching shovel (4" wide blade) | 90° sweeps for conduit (2) | Interior ceiling light fixture and metal fixture box | 20-amp GFCI-protected circuit breaker |
| 4" metal junction box | Plastic conduit bushings (2) | Exterior motion-detector fixture and plastic fixture box | Wire stripper |
| Metal L-fittings (2) and conduit nipple for conduit | Pipe straps | EMT metal conduit and fittings for inside the shed | Pliers |
| Wood screws | Silicone caulk and caulk gun | Utility knife | Screwdrivers |
| Conduit with watertight threaded and compression fittings | Double-gang boxes, metal (2) | UF two-wire cable (12 gauge) | Wire connectors |
| Wrenches | One exterior receptacle box (with cover) | | Hand tamper |
| | | | Schedule 80 conduit |
| | | | Eye protection |

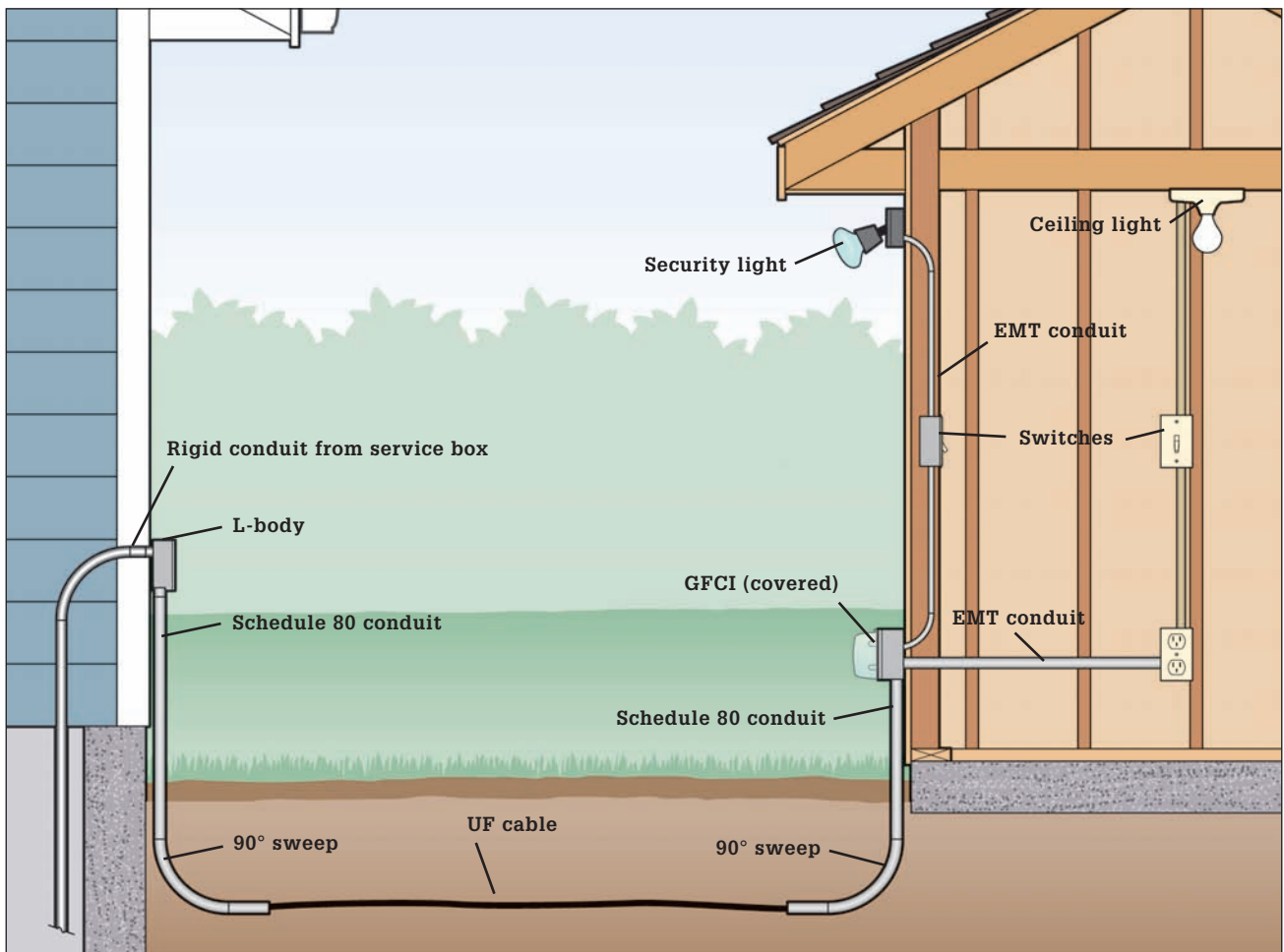

A basic outdoor circuit starts with a waterproof fitting at the house wall connected to a junction box inside. The underground circuit cable—rated UF (underground feeder)—runs in a 24"-deep trench and is protected from exposure at both ends by metal or PVC conduit. Inside the shed, standard NM cable runs through metal conduit to protect it from damage (not necessary if you will be adding interior wallcoverings). All receptacles in the shed must be GFCI protected.

How to Wire an Outbuilding




1 **Identify the circuit's exit point** at the house and entry point at the shed and mark them. Mark the path of the trench between the exit and entry points using spray paint. Make the route as direct as possible. Dig the trench to the depth required by local code (24") using a narrow trenching shovel.



2 **From outside**, drill a hole through the exterior wall and the rim joist at the exit point for the cable (you'll probably need to install a bit extender or an extra-long bit in your drill). Make the hole just large enough to accommodate the L-body conduit fitting and conduit nipple.



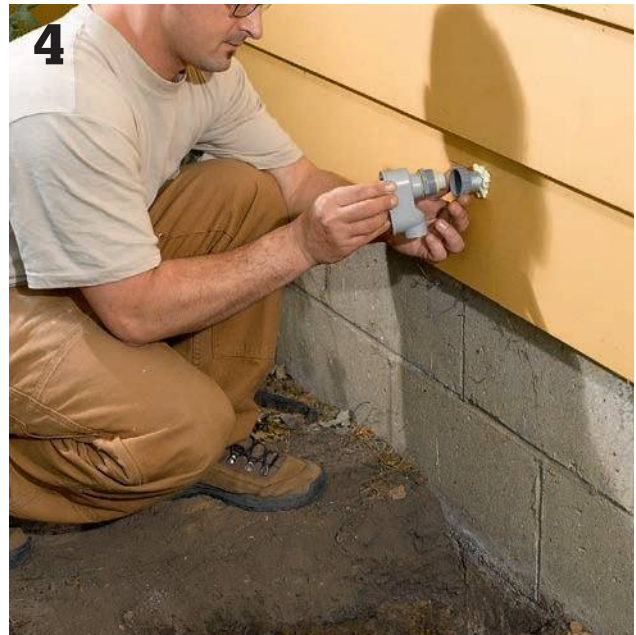3 **Assemble the conduit and junction box fittings** that will penetrate the wall. Here, we attached a 12" piece of $\frac{3}{4}$ " IMC (intermediate metallic conduit) and a sweep to a metal junction box with a compression fitting and then inserted the conduit into the hole drilled in the rim joist. The junction box is attached to the floor joist.



4 **From outside**, seal the hole around the conduit with expandable spray foam or caulk, and then attach the free end of the conduit to the back of a waterproof L-body fitting. Mount the L-body fitting to the house exterior with the open end facing downward.



5

Cut a length of IMC to extend from the L-fitting down into the trench using a hacksaw. Deburr the cut edges of the conduit. Secure the conduit to the L-fitting, and then attach a 90° sweep to the bottom end of the conduit using compression fittings. Add a bushing to the end of the sweep to protect the circuit cable. Anchor the conduit to the wall with a corrosion-resistant pipe strap.



6

Inside the shed, drill a $\frac{3}{4}$ " dia. hole in the shed wall. On the interior of the shed, mount a junction box with a knock-out removed to allow the cable to enter through the hole. On the exterior side directly above the end of the UF trench, mount an exterior-rated receptacle box with cover. The plan (and your plan may differ) is to bring power into the shed through the hole in the wall behind the exterior receptacle.



7

Run conduit from the exterior box down into the trench. Fasten the conduit to the building with a strap. Add a 90° sweep and bushing, as before. Secure the conduit to the box with an offset fitting. Anchor the conduit with pipe straps, and seal the entry hole with caulk.




8

Run UF cable from the house to the outbuilding. Feed one end of the UF circuit cable up through the sweep and conduit and into the L-fitting at the house (the back or side of the fitting is removable to facilitate cabling). Run the cable through the wall and into the junction box, leaving at least 12" of extra cable at the end.

(continued)



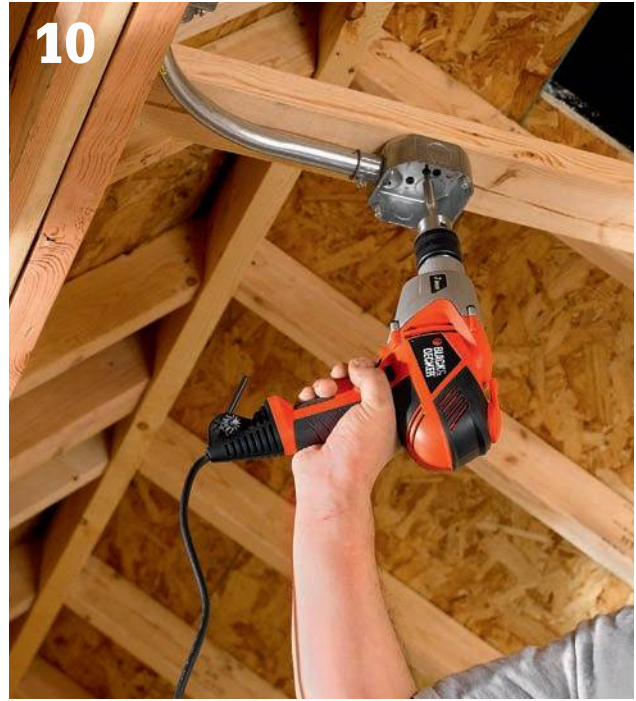9 Lay the UF cable into the trench, making sure it is not twisted and will not contact any sharp objects. Roll out the cable, and then feed the other end of the cable up through the conduit and into the receptacle box in the shed, leaving 12" of slack.



10 Inside the outbuilding, install the remaining boxes for the other switches, receptacles, and lights. With the exception of plastic receptacle boxes for exterior exposure, use metal boxes if you will be connecting the boxes with metal conduit.



11 Connect the electrical boxes with conduit and fittings. Inside the outbuilding, you may use inexpensive EMT to connect receptacle, switch, and fixture boxes. Once you've planned your circuit routes, start by attaching couplings to all of the boxes.



12 Cut a length of conduit to fit between the coupling and the next box or fitting in the run. If necessary, drill holes for the conduit through the centers of the wall studs. Attach the conduit to the fitting that you attached to the first box.



13

If you are surface-mounting the conduit or running it up or down next to wall studs, secure it with straps no more than 3 ft. apart. Use elbow fittings for 90° turns and setscrew couplings for joining straight lengths as needed. Make holes through the wall studs only as large as necessary to feed the conduit through.



14

THNN wire

Measure to find how much wire you'll need for each run, and cut pieces that are a foot or two longer. Before making L-turns with the conduit, feed the wire through the first conduit run.



15

Feed the other ends of the wires into the next box or fitting in line. It is much easier to feed wire into 45° and 90° elbows if they have not been attached to the conduit yet. Continue feeding wire into the conduit and fitting until you have reached the next box in line.



16

Once you've reached the next box in line, coil the ends of the wires and repeat the process with new wire for the next run. Keep working until all of the wire is run and all of the conduit and fittings are installed and secured. If you are running multiple feed wires into a single box, write the origin or destination on a piece of masking tape and stick it to each wire end.


(continued)



17

Note: Your Code may require an in-use rated receptacle box cover.

Make the wiring connections at the receptacles. Strip $\frac{3}{4}$ " of insulation from the circuit wires using a wire stripper. Connect the white (neutral) wire and black (hot) wire of the UF cable to the LINE screw terminals on the receptacle. Connect the white (neutral) and black (hot) wires from the NM cable to the LOAD terminals. Pigtail the bare copper ground wires and connect them to the receptacle ground terminal and the metal box. Install the receptacle and cover plate.

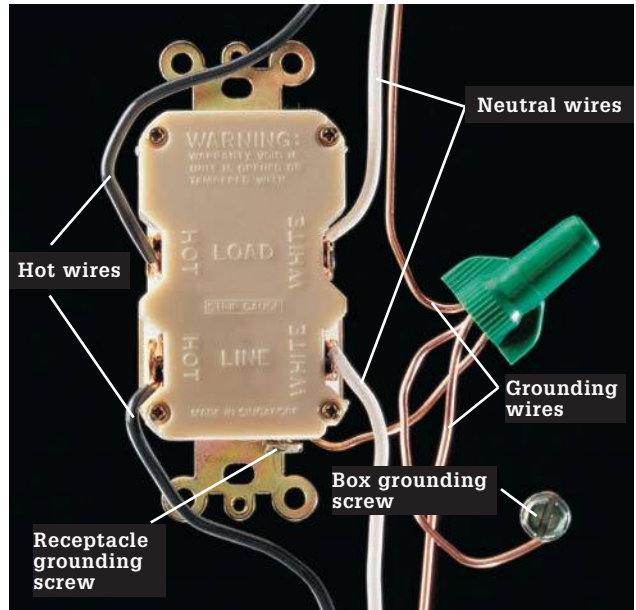

Variation: Installing a GFCI-protected breaker for the new circuit at the main service panel is the best way to protect the circuit and allows you to use regular receptacles in the building, but an alternative that is allowed in many areas is to run the service into a GFCI-protected receptacle and then wire the other devices on the circuit in series. If you use this approach, only the initial receptacle needs to be a GFCI receptacle.




18

Continue installing receptacles in the circuit run, and then run service from the last receptacle to the switch box for the light fixture or fixtures. (If you anticipate a lot of load on the circuit, you should probably run a separate circuit for the lights). Twist the white neutral leads and grounding leads together and cap them. Attach the black wires to the appropriate switches. Install the switches and cover plate.




19

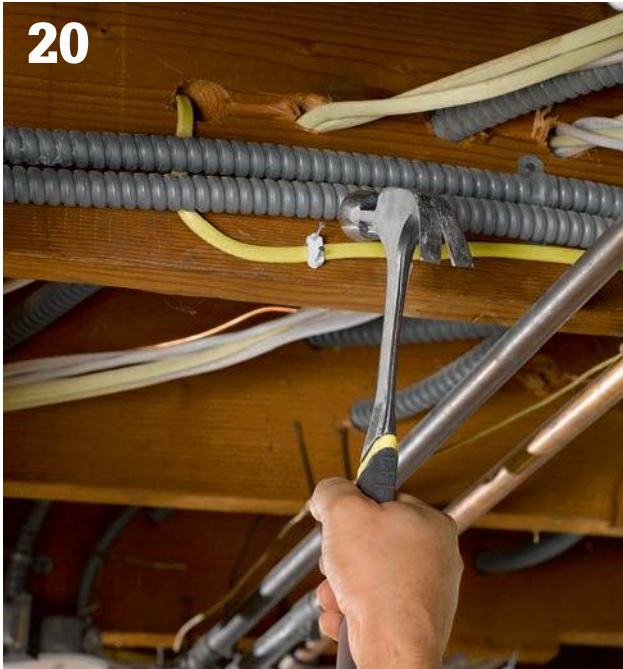Install the light fixtures. For this shed, we installed a caged ceiling light inside the shed and a motion-detector security light on the exterior side.



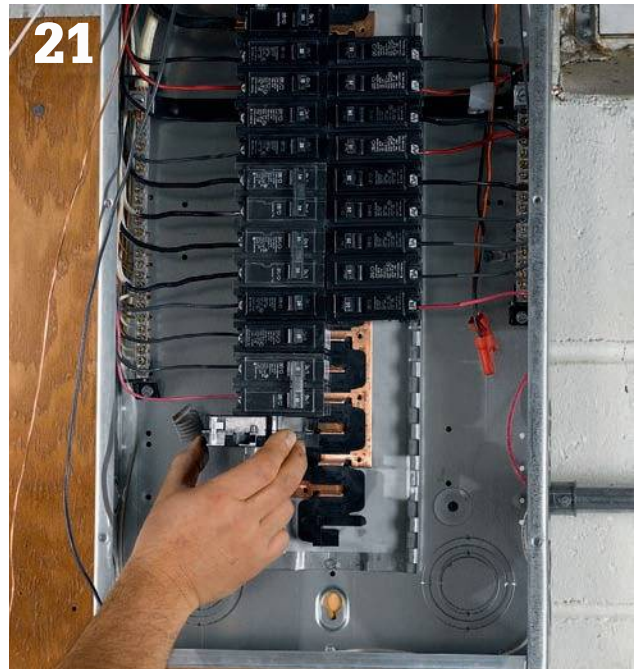Run NM cable from the electrical box in the house at the start of the new circuit to the main service panel. Use cable staples if you are running the cable in floor joist cavities. If the cable is mounted to the bottom of the floor joists or will be exposed, run it through conduit.



At the service panel, feed the NM cable in through a cable clamp. Arrange for your final electrical inspection before you install the breaker. Then attach the wires to a new circuit breaker, and install the breaker in an empty slot. Label the new circuit on the circuit map.



Turn on the new circuit, and test all of the receptacles and fixtures. Depress the Test button and then the Reset button if you installed a GFCI receptacle. If any of the fixtures or receptacles is not getting power, check the connections first, and then test the receptacle or switch for continuity with a multimeter. Backfill the trench.

Standalone Solar Lighting System

A self-contained electrical circuit with dedicated loads, usually 12-volt light fixtures, is one of the most useful solar amenities you can install. A standalone system is not tied into your power grid, which greatly reduces the danger of installing the components yourself. Plus, the fact that your light fixtures are independent of the main power source means that even during a power outage you will have functioning emergency and security lights.

Installing a single solar-powered circuit is relatively simple, but don't take the dangers for granted. Your work will require permits and inspections in most jurisdictions, and you can't expect to pass if the work is not done to the exact specifications required.


Solar panels that convert the sun's energy into electricity are called photovoltaic (PV) panels,

and they produce direct current (DC) power. PV solar panel systems can be small and designed to accomplish a specific task, or they can be large enough to provide power or supplementary power to an entire house. Before you make the leap into a large system, it's a good idea to familiarize yourself with the mechanics of solar power. The small system demonstrated in this project is relatively simple and is a great first step into the world of solar. The fact that the collector, battery, and lights are a standalone system makes this a very easy project to accomplish. By contrast, installing panels that provide direct supplementary power through your main electrical service panel is a difficult wiring job that should be done by professional electricians only.



This 60-watt solar panel is mounted on a garage roof and powers a self-contained home security lighting system. Not only does this save energy costs, it keeps the security lights working even during power outages.

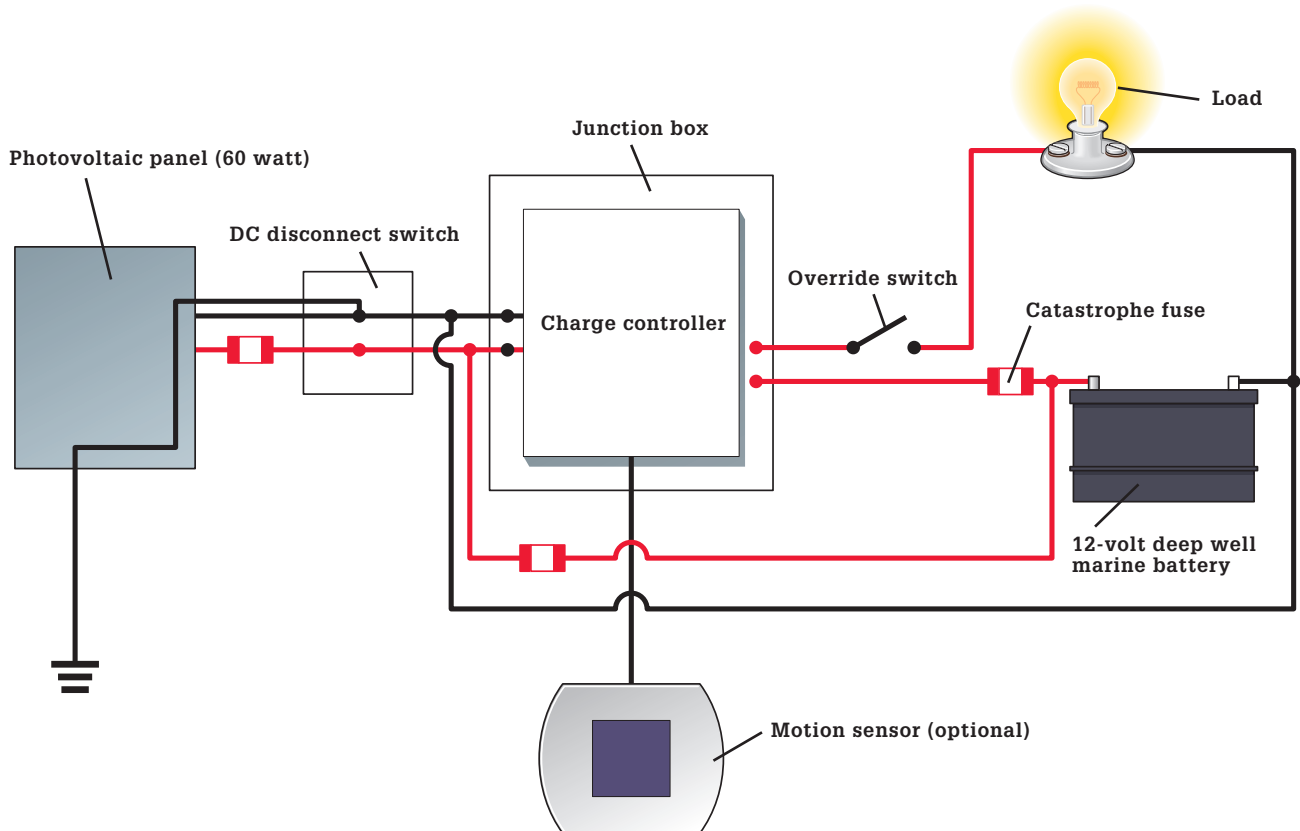Schematic Diagram for an Off-the-Grid Solar Lighting System



Tools & Materials ▶

| | | | |
|------------------------|-------------------------------------|-----------------------------------|--------------------------------------|
| Tape measure | 20 ft. Unistrut 1 $\frac{7}{8}$ " | (2) $\frac{1}{2}$ " liquid | $\frac{1}{2}$ " Greenfield |
| Drill/driver with bits | thick U-channel (See | tight connectors | connectors |
| Caulk gun | Resources, page 125) | (2) Lay-in | (4) $1\frac{1}{16}$ " junction boxes |
| Crimping tool | (4) 45° Unistrut | grounding lugs | with covers |
| Wiring tools | connectors | (2) Insulated terminal | (4) square boxes |
| Metal-cutting saw | (2) 90° Unistrut | bars to accept one | with covers |
| Photovoltaic panel | angle brackets | 2-gauge wire and | PVC 6" × 6" junction |
| (50 to 80 watts) | (4) Unistrut hold | 4 12-gauge wires | box with cover |
| Charge controller | down clamps | (2) Cord cap | 14/2 UF wire |
| Catastrophe fuse | (12) $\frac{3}{8}$ " spring nuts | connectors for | $\frac{1}{4}$ " × 20 nuts and |
| Battery sized for | (12) $\frac{3}{8}$ "-dia. × 1"-long | $\frac{1}{2}$ "-dia. cable | bolts with lock |
| 3 day autonomy | hex-head bolts | $\frac{1}{2}$ " ground rod | washers |
| Battery case | with washers | and clamp | Roof flashing boot |
| Battery cables | DC-rated disconnect | Copper wire | Roof cement |
| 12-volt LED lights | or double throw | (6, 12-gauge) | Silicon caulk |
| including motion- | snap switch | Green ground screws | Eye protection |
| sensor light | 6" length of $\frac{1}{2}$ "-dia. | $\frac{1}{2}$ " Flexible metallic | |
| Additional 12-volt | liquid-tight flexible | conduit or | |
| fixtures as desired | metallic conduit | Greenfield | |

Mounting PV Panels



The mounting stand for the PV panel is constructed from metal U-channel (a product called Unistrut is seen here. See Resources page 125) and pre-bent fasteners. Position the solar panel where it will receive the greatest amount of sunlight for the longest period of time each day—typically the south-facing side of a roof or wall. For a circuit with a battery reserve that powers two to four 12-volt lights, a collection panel rated between 40 and 80 watts of output should suffice. These panels can range from \$200 to \$600 in price, depending on the output and the overall quality.



The stand components are held together with bolts and spring-loaded fasteners. The 45° and 90° connectors are manufactured specifically for use with this Unistrut system.



Connections for the feed wires that carry current from the collector are made inside an electrical box mounted on the back of the collector panel.




An EPDM rubber boot seals off the opening where the PVC conduit carrying the feed wires penetrates the roof.

How to Wire a DC Lighting Circuit



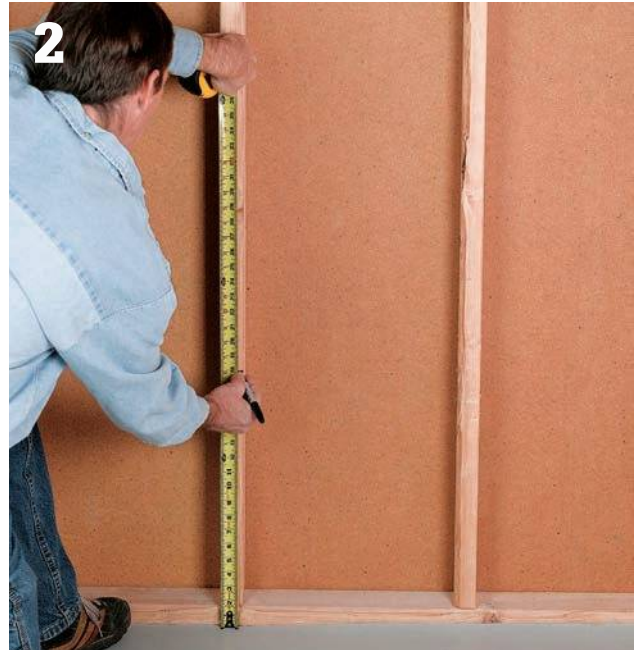
1 **Mount a junction box** inside the building where the conduit and wiring enter from the power source. Secure the box to the conduit with appropriate connectors. Run two #14 awg wires through the conduit and connect them to the positive and negative terminals on the panel (see previous page).



2 **Plan the system layout.** Determine the placement of the battery, and then decide where you will position the charge controller and DC disconnect. The battery should be placed at least 18" off the floor, in a well-ventilated area where it won't be agitated by everyday activity. Mark locations directly on the wall.



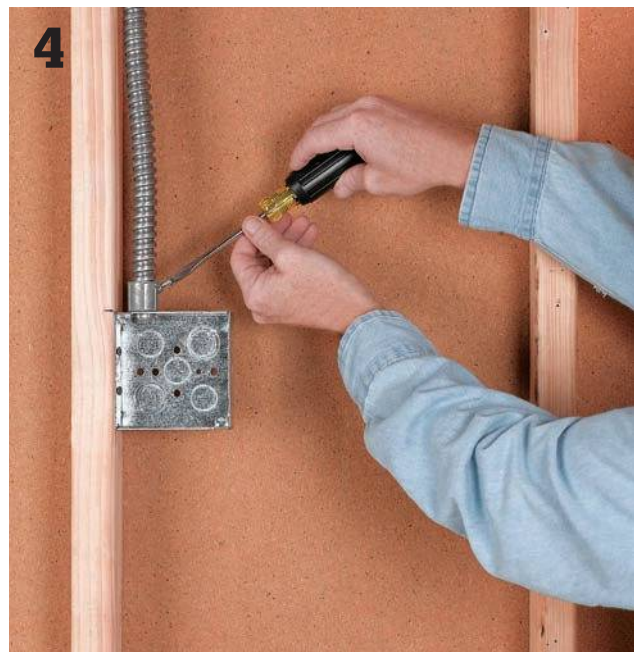3 **Attach a junction box** for enclosing the DC disconnect, which is a heavy-duty switch, to a wall stud near the battery and charge controller location. Use a metal single-gang box with mounting flanges.




4 **Run flexible metal conduit** from the entry point at the power source to the junction box for the DC disconnect box. Use hangers rated for flexible conduit.


(continued)




5 Attach the DC disconnect switch to the wire leads from the power source.

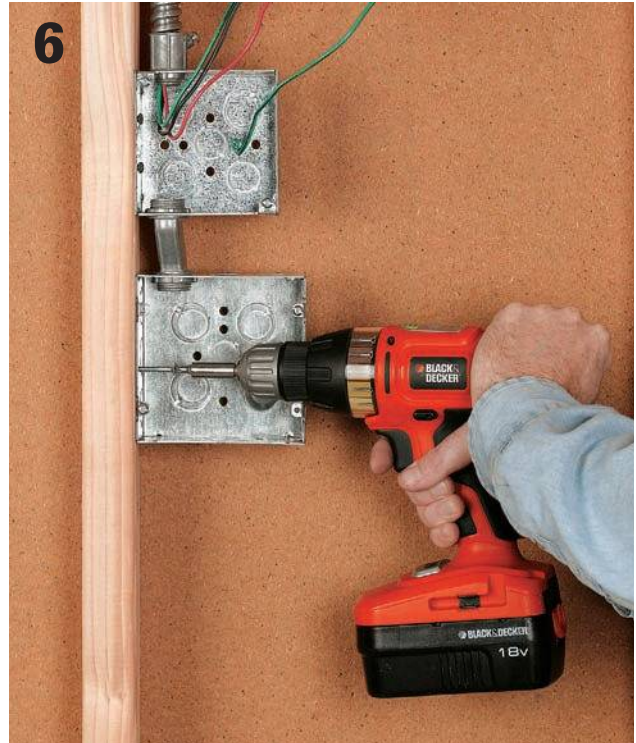

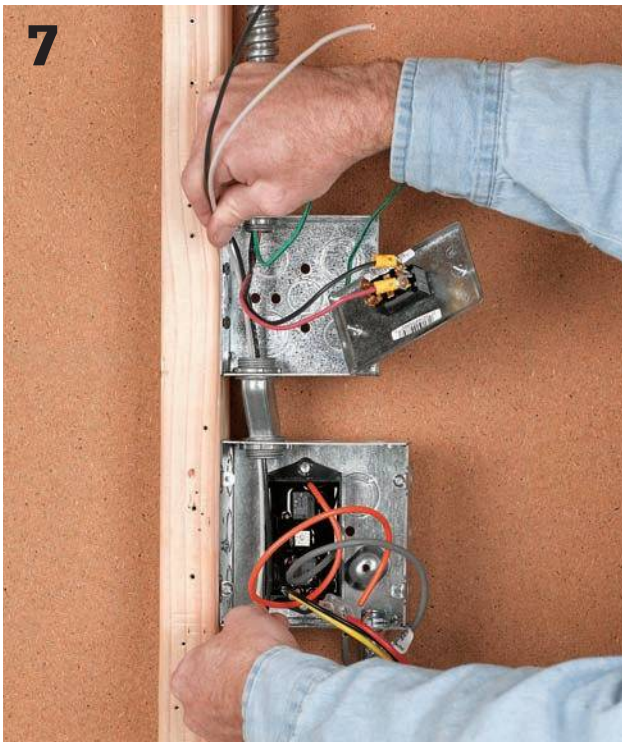6 Attach a double gang metal junction box to the building's frame beneath the DC disconnect box to enclose the charge controller.



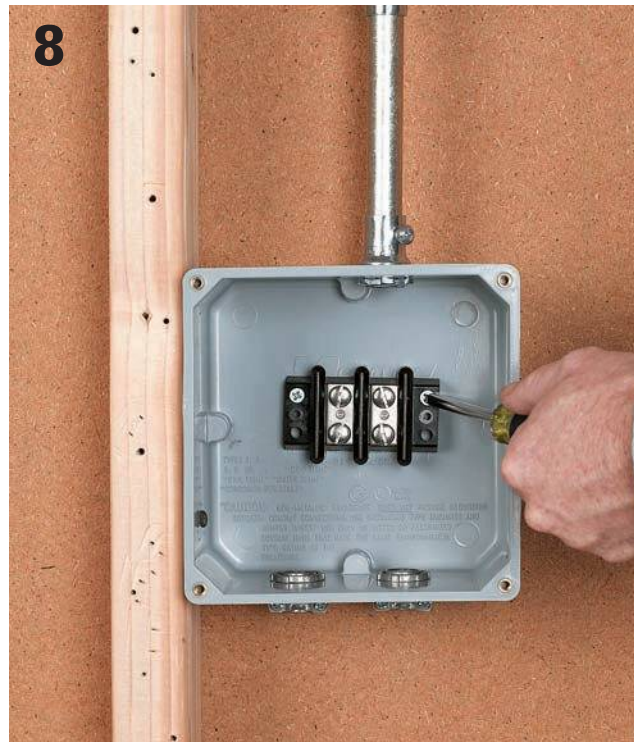7 Install the charge controller inside the box. Run flexible conduit with connectors and conductors from the disconnect box and to the charge controller box.




8 Mount a PVC junction box for the battery controller about 2 ft. above the battery location, and install two insulated terminal bars within the box.




9
Build a support shelf for the battery using 2 × 4s. The shelf should be at least 18" above ground. Set the battery on the shelf in a sturdy plastic case.



10
Set up grounding protection. Pound an 8-ft. long, ½"-dia. ground rod into the ground outside the building, about 1 ft. from the wall on the opposite side of the charge controller. Leave about 2" of the rod sticking out of the ground. Attach a ground rod clamp to the top of the rod. Drill a ⅝" hole through the garage wall (underneath a shake or siding piece) and run the #6-gauge THWN wire to the ground rod. This ground will facilitate lightning protection. See pages 58 to 63 for more information on grounding the system.

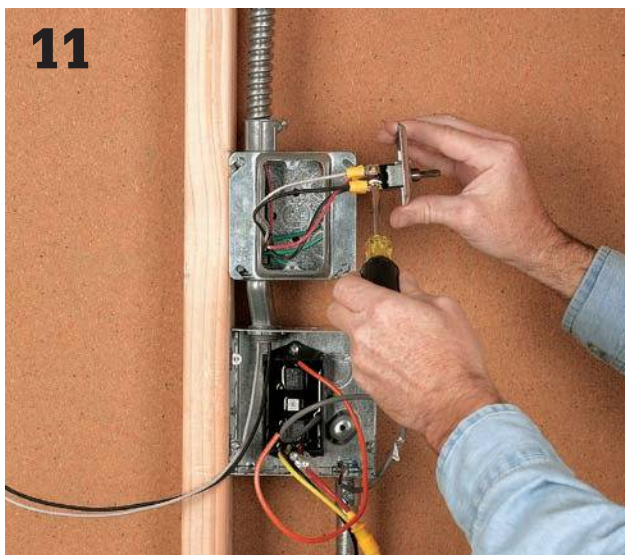

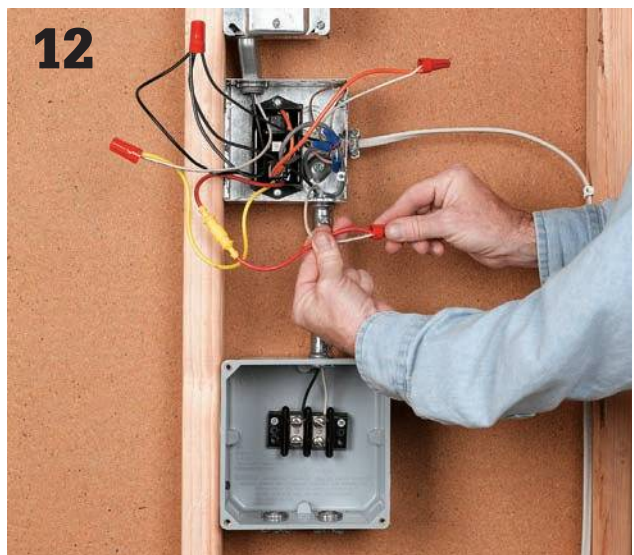11
Wire the DC disconnect. Attach the two #14-gauge wires to the two terminals labeled "line" on the top of the DC disconnect switch.




12
Wire the charge controller. Route two more #14-gauge wires from the bottom of the DC disconnect terminals into the 4" × 1½" junction box and connect to the "Solar Panel In" terminals on the charge controller. The black wire should connect to the negative terminal in the PVC box and the red to the positive lead on the charge controller. Finish wiring of the charge controller according to the line diagram provided with the type of controller purchased. Generally the load wires connect to the orange lead, and the red wire gets tied to the battery through a fuse.

(continued)



OPTION: Attach a motion sensor. Some charge controllers come equipped with a motion sensor to maximize the efficiency of your lighting system—these are especially effective when used with security lighting. The motion sensor is typically mounted to a bell box outside and wired directly to the charge controller with an 18-gauge × 3-conductor insulated cable. A system like this can support up to three motion sensors. Follow the manufacturer’s directions for installing and wiring the motion sensor.

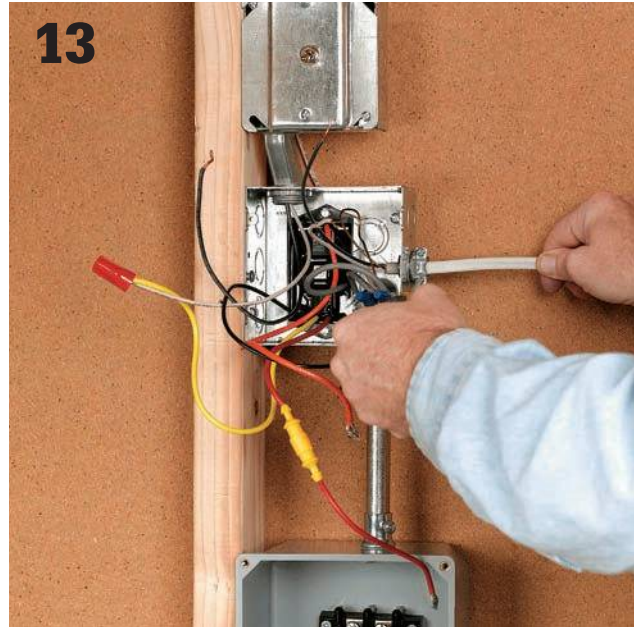


13

Run wiring to the loads (exterior DC lighting fixtures in this case) from the charge controller. DC light fixtures (12-volt) with LED bulbs can be purchased at marine and RV stores if you can’t find them in your home center or electrical supply store.



14

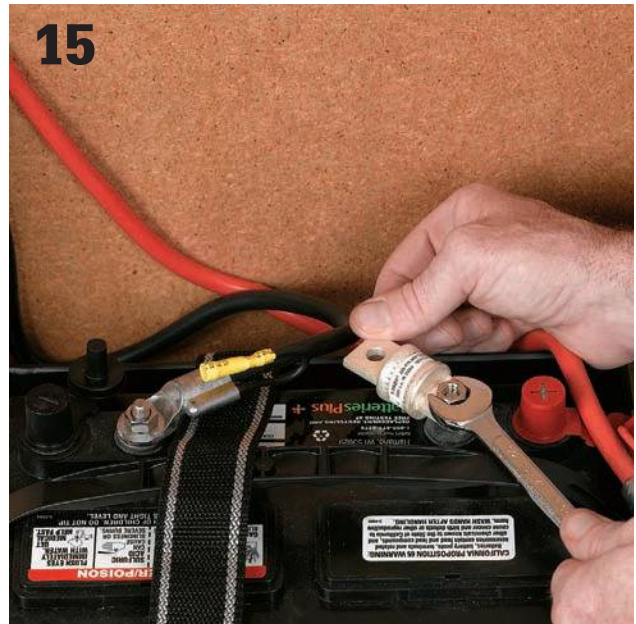Install the battery. Here, a deep-cell 12-volt marine battery is used. First, cut and strip each of the two battery cables at one end and install into the battery control junction box through cord cap connectors. Terminate these wires on two separate, firmly mounted insulated terminal blocks.



15

Install the catastrophe fuse onto the positive terminal using nuts and bolts provided with the battery cables. Connect the battery cables to the battery while paying close attention to the polarity (red to positive and black to negative). Make sure all connections have been made and double checked.

Troubleshooting & Repairs

Running new circuits and hooking up new fixtures are fairly predictable projects when it comes to estimating time and expense. This is less true with repairing problems in your system and fixtures. In some cases, a repair is as simple as opening an electrical box, spotting a loose wire connector and remaking the connection. But there are also times when fixing a dead circuit or device is a highly frustrating proposition. Such cases are almost always caused by tricky diagnostic challenges. Wires are hidden behind walls and there very often are no visual clues to system breakdowns. So essentially, minimizing repair frustration boils down to learning

to deploy logical, systematic diagnostics. Educated troubleshooting, you could say.

In this project you'll learn how to use the most important diagnostic tool in any electrician's toolkit: the multimeter. These handy devices come in a dizzying array of types and qualities, but for diagnostic purposes they are used to take readings for current (amperage), voltage and continuity (whether an electrical path is open or closed). Once you learn the basics of operating a multimeter, you can enlist it in a logical, deductive manner to track down the source of a wiring problem. Once located, correcting the problem is usually very simple.



Diagnostic tools for home wiring use include: Touchless circuit tester (A) to safely check wires for current and confirm that circuits are dead; Plug-in tester (B) to check receptacles for correct polarity, grounding and circuit protection; Multimeter (C) to measure AC/DC voltage, AC/DC current, resistance, capacitance, frequency and duty cycle (model shown is an auto-ranging digital multimeter with clamp-on jaws that measure through sheathing and wire insulation).


Multimeters

Multimeters are nearly indispensable diagnostic tools for doing intermediate to advanced level electrical work (as well as automotive and electronics repair). They are used to measure voltage, current (amperage) and a few other conditions such as continuity, capacitance and frequency. For your home electrical system, by far the most used feature of a multimeter is testing voltage and current, although there are occasions where testing for resistance is needed. Among professional electricians, the most common and widely used multimeters have a clamp-on ammeter that measures current through the wire insulation so you don't have to disconnect the circuit and expose bare wire. Most clamp-on multimeters also are fitted with insertible probes with which you can measure voltage and continuity in the

traditional way. An example of a clamp-on multimeter can be seen on the next page. Among homeowners, however, the most common multimeters these days are digital, auto-ranging tools that use probes or alligator clamps at the ends of wire leads for diagnostic work. Older multimeters that do not have autoranging capability must be pre-set to estimated calibration levels before use. Non-digital multimeters or ammeters usually have a dial gauge that gives readouts. These tools are somewhat more difficult to use and are less precise. Considering that digital, autoranging multimeters can be found for just a few dollars (the top of the line models cost over \$100) there is really no good reason not to replace your old device with one that resembles the tools seen on these pages.

Time to Replace that Neon Tester ▶

Neon circuit testers are inexpensive and easy to use (if the light glows the circuit is hot), but they are less sensitive than multimeters and can be unsafe. In some cases, neon testers won't detect the presence of lower voltage in a circuit. This can lead you to believe that a circuit is shut off when it is not—a dangerous mistake. The small probes on a neon circuit tester also force you to get too close to live terminals and wires. For the most reliable readings, buy and learn to use a multimeter. At the very least, switch to a touchless tester like the one on page 107, Step 1.

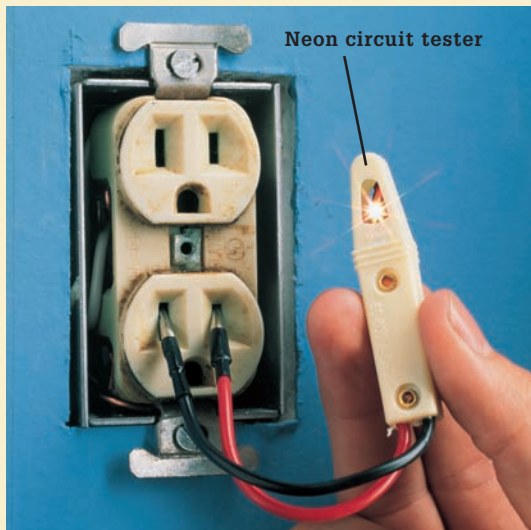

A digital, autoranging multimeter must be adjusted to the proper setting for the reading you want to take. The probe leads also must be inserted into the correct inlet at the bottom of the tool. Inserting the red lead into the incorrect inlet can cause the tool to trip an internal fuse. Study your owner's manual carefully before using any tool.

How to Measure Current



1 **Create access to the wires** you need to test. In most cases this requires that you remove the cover to an electrical service panel or an electrical box (inset).



2 **Set the multimeter to test for amperage** (current is measured in amperes or amps). On some multimeters you need to select between amperage settings that are above or below 40 amps. Use the rated amperage of the circuit as a guide (amperage is printed on the circuit breaker switch).



3 **Clamp the jaws of a clamp-on multimeter** onto the conductor or one of the conductors (if more than one) leading to a circuit breaker. If you are using a non-clamping multimeter, touch one probe to the screw terminal where the hot lead is attached to the breaker and touch the other probe to the metal panel box. The readout on your meter is the amount of current flowing in that circuit.

Taking Measurements at a Receptacle ▶

You may use a multimeter to measure for voltage at a wall receptacle. Regardless of whether the outlet is in service, if it is live you will get a voltage reading in the approximate range of the receptacle rating—here, 120 volts. To detect live current, measured in amps, the receptacle must be in use, with an appliance drawing from it. Taking an amperage reading in such an instance will only yield the amount of current being drawn, which is a factor of the appliance, not the circuit capacity.



How to Measure Voltage



1 To measure voltage using the multimeter, you will have to use the two probes provided with the multimeter and have access to a live terminal or slot as well as a grounded terminal or slot. If your meter has probe holders at the top, snap the probes into them. They are like extra hands.



2 Turn the multimeter to the VAC setting to measure AC voltage that is found in your house. Set the multimeter to VDC if measuring DC voltage, such as in a car or a battery-fed device. On some multimeters, like the one above, you select "V" for voltage then change between AC and DC with the "FUNC" button.



3 To measure the AC voltage, place one probe on a grounded surface, such as the metallic junction box or the bare ground wire. Place the other probe on the hot screw terminal or into the receptacle slot associated with the hot wire. The voltage readout should be in the range of 120 volts, plus or minus 5 volts (usually 120 volts in a residence in the US).



240 VOLTS. You can also measure voltage across the two hot leads to determine if you have 240 volts. This can be done at your range receptacle, dryer receptacle, or any other 240-volt receptacle. Place one probe in one of the small slots and the other probe in the other slot directly across from it. The voltage should read 240 volts, plus or minus 5 volts.



DC Voltage. When testing DC voltage, such as in a car battery, you can measure exactly the same way as for AC as long as the meter is set to the DC function. For more accurate results, test the voltage while the battery is in use.

How to Test for Continuity

Continuity is a condition in a circuit where the conductors form an unbroken pathway through which current may flow. When measuring for continuity, always make sure there is no power

present on the circuit you are testing or damage may occur to the meter. You can also measure the resistance in this mode as well.



1 The setting for continuity is an “audible” or diode symbol display on the dial. Select this setting.



2 Verify that the continuity tester is functional by touching the two probes together. You should hear an alert sound and/or see a reading of zero ohms (Ohms is a value of the resistance to current flow).



3 To test a circuit, touch one probe to one of the wires on a given circuit and the other to the second wire of the circuit. If you hear an audible sound or read a value of resistance other than zero, you have a complete or unbroken path for current to flow.

How to Test a 3-way Switch ▶

Remove the switch from the circuit and place one of the probes onto the common terminal and the other probe onto one of the other two terminals used for the traveler wires. If the meter indicates infinity ohms or there is no sound, flip the switch and if it is in working order the meter should read zero ohms or emit an audible sound. It should only work in one direction or the other, not both.



Troubleshooting an Open Neutral

An open neutral is an electrical problem where the circuit is broken on the return path wire or neutral (white wire). When this situation occurs anything plugged into or connected to this circuit can experience

low or high voltage, which could damage voltage sensitive electronics such as a computer or flat screen TV. The lights will be dim or not work at all, depending upon where the problem lies within the circuit.

Possible Symptoms of an Open Neutral ▶

1. When a whole circuit does not work and the breaker associated with that circuit is operating normally.
2. When the neutral or white wire registers as a hot wire by using a non contact voltage tester when the circuit breaker is on. This most likely indicates a problem between the main service panel and the utility transformer. The condition should be readable on other receptacles as well.
3. If you register a voltage lower than 110 volts between the hot and neutral.
4. When the incandescent lights work, but are very dim.
5. When the fluorescent lights are barely lit and are flickering.
6. Discoloration of the wires or exposed copper turning green under the wrenut holding the neutral wires together.



How to Troubleshoot an Open Neutral



1 Verify which lights and receptacles are on the circuit by turning the breaker off and by checking for power with a non-contact voltage tester. It is helpful to either draw a map of the house or place some tape on every affected opening.



2 Start at the outlet nearest to the panel. With the breaker off and using a multimeter, check for continuity between the neutral (white wire) and the ground (bare or green wire). These two wires land at the same point electrically in your electrical panel. If there is an indication of continuity between these two wires, the neutral and ground connections are sound and you should proceed to the next outlet as you move away from the panel.



3 When you encounter a point at which you read infinity ohms or there is no continuity between the neutral and ground wires, the problem lies within the connections in that box or the box just upstream (toward) the panel from the one you are checking. Sometimes you will see evidence of arcing on the wire cap containing the connection which may include discoloration, or a blackish char near the copper.



4 When you have found the problem connection, remove the wire cap and, if it is possible, cut the damaged portions of the wires off and restrip the wires to expose new copper. Line the wire ends up and twist on a new wire cap.



5 Turn the circuit breaker back on and verify the proper voltage is present at your receptacles by measuring with a multimeter.

Troubleshooting a Short Circuit

Short circuits are a direct connection between the hot or power wire (black or red) and to either the neutral (white) or ground (bare) wire. This connection between the two will cause your circuit breaker or fuse to blow, which should interrupt power to the affected circuit.


Short circuits are a common problem and can usually be solved by taking the following steps. The

idea behind electrical troubleshooting is to simplify the circuit by checking it at certain points, in order to narrow down the problem point by process of elimination. Generally, the problem is that there is a bare ground wire touching a hot terminal within a switch or an outlet box. There will usually be a black scorched mark or some sign of an electrical arc where the problem lies.

How to Troubleshoot a Short Circuit



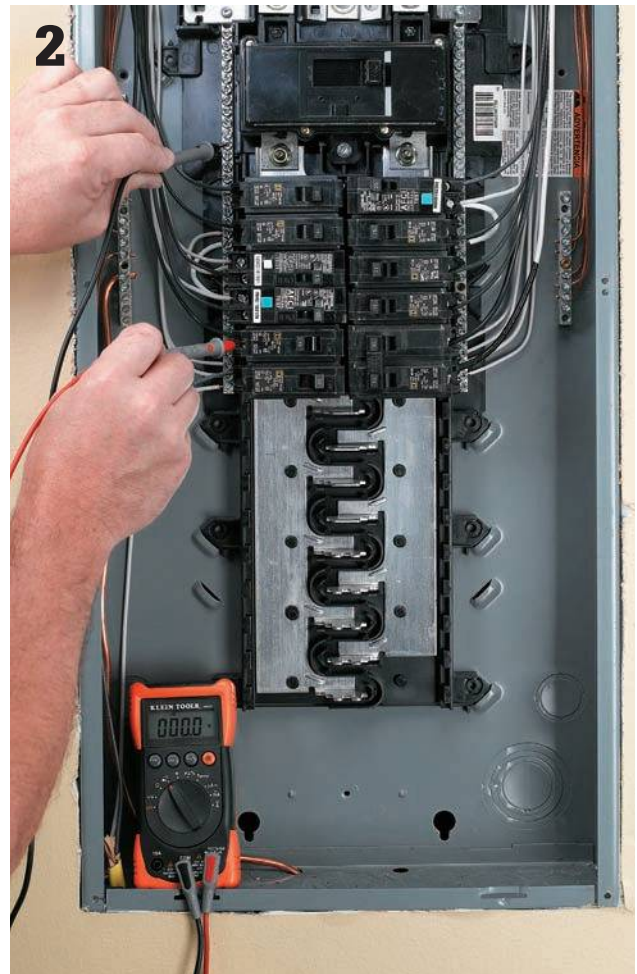1 Turn the power off at the affected breaker and verify with a non-contact voltage tester that there is no power present. Unplug everything from the receptacles and turn the lights off on the circuit that is affected.



2 Using a multimeter set to the ohms or continuity setting, check the wires at the panel. Touch one of the probes to the hot or black wire and the other probe to the ground or bare wire. If the meter rings or indicates a low resistance value, you have a direct short to ground. If the meter does not ring or indicates a high resistance value the circuit is clear. If the meter does not ring, start by turning the switches on one-by-one and re-testing to verify the resistance value. If the meter indicates a low resistance value or a short circuit, the problem is downstream from the switch or within the light fixture itself.



3 If the meter consistently rings or indicates a low resistive value, you will need to find the electrical box that contains the affected circuit. Choose a box that is convenient to open and preferably in the middle of the run, such as a receptacle. Verify there is no power present by touching all of the wires within the box with a non-contact voltage tester.



4 If the box you have chosen is in fact in the middle of the run, it will contain at least two cables. Remove the receptacle from the two cables and separate all of the wires.



5 Check the resistance between the black and the ground on both sets of cables. One of the cables should cause the continuity alert to ring and the other should not. Mark the affected one with a piece of black tape and place wire caps over the exposed ends of the black wires.



6 Check the wires at the panel to see if the short has cleared. If the short is clear, the problem lies down stream from the opened box and it is now safe to turn the breaker back on to help eliminate further problem points. If the short is still present, the problem lies between the opened electrical box and the panel.



7 Choose another box in the middle of the affected circuit, there by narrowing down the possible problem areas until the short circuit can be positively identified and corrected. When you have discovered the short circuit, verify the wires are still in good shape and repair the connection.

Types of Wall Switches

Wall switches are available in three general types. To re-connect or replace a switch, it is important to identify its type.


Single-pole switches are used to control a set of lights from one location. Three-way switches are used to control a set of lights from two different locations and are always installed in pairs. Four-way switches are used in combination with a pair of three-way switches to control a set of lights from three or more locations.

Identify switch types by counting the screw terminals. Single-pole switches have two screw terminals, three-way switches have three screw

terminals, and four-way switches have four. Most switches include a grounding screw terminal, which is identified by its green color.

When replacing a switch, choose a new switch that has the same number of screw terminals as the old one. The location of the screws on the switch body varies depending on the manufacturer, but these differences will not affect the switch operation.

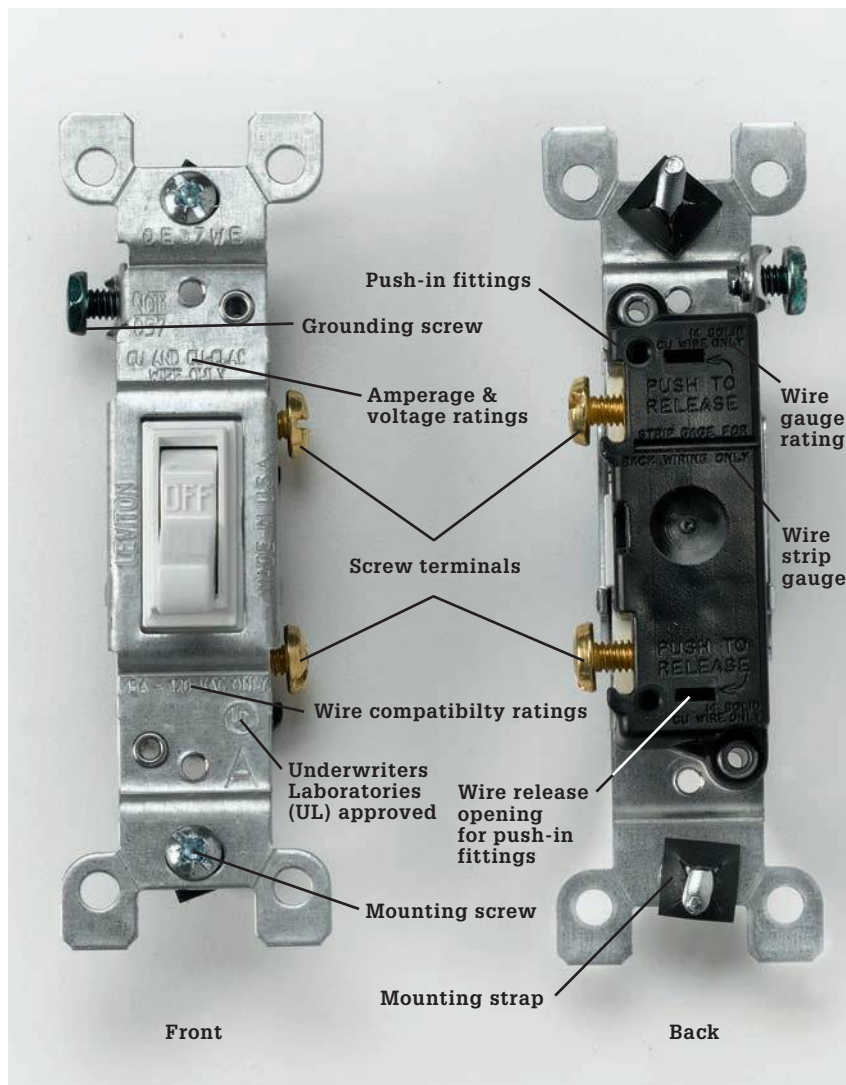Whenever possible, connect switches using the screw terminals rather than push-in fittings. Some specialty switches (pages 118 to 119) have wire leads instead of screw terminals. They are connected to circuit wires with wire connectors.



A wall switch is connected to circuit wires with screw terminals or with push-in fittings on the back of the switch. A switch may have a stamped strip gauge that indicates how much insulation must be stripped from the circuit wires to make the connections.

The switch body is attached to a metal mounting strap that allows it to be mounted in an electrical box. Several rating stamps are found on the strap and on the back of the switch. The abbreviation UL or UND. LAB. INC. LIST means that the switch meets the safety standards of the Underwriters Laboratories. Switches also are stamped with maximum voltage and amperage ratings. Standard wall switches are rated 15A or 125V. Voltage ratings of 110, 120, and 125 are considered to be identical for purposes of identification.

For standard wall switch installations, choose a switch that has a wire gauge rating of #12 or #14. For wire systems with solid-core copper wiring, use only switches marked COPPER, CU, or CO/ALR. For aluminum wiring, use only switches marked CO/ALR. Note that while CO/ALR switches and receptacles are approved by the National Electrical Code for use with aluminum wiring, the Consumer Products Safety Commission does not recommend using these. Switches and receptacles marked AL/CU can no longer be used with aluminum wiring, according to the National Electrical Code.


Single-Pole Wall Switches

A single-pole switch is the most common type of wall switch. It has ON-OFF markings on the switch lever and is used to control a set of lights, an appliance, or a receptacle from a single location. A single-pole switch has two screw terminals and a grounding screw. When installing a single-pole switch, check to make sure the ON marking shows when the switch lever is in the up position.

In a correctly wired single-pole switch, a hot circuit wire is attached to each screw terminal. However, the color and number of wires inside the switch box will vary, depending on the location of the switch along the electrical circuit.


If two cables enter the box, then the switch lies in the middle of the circuit. In this installation, both of the hot wires attached to the switch are black.

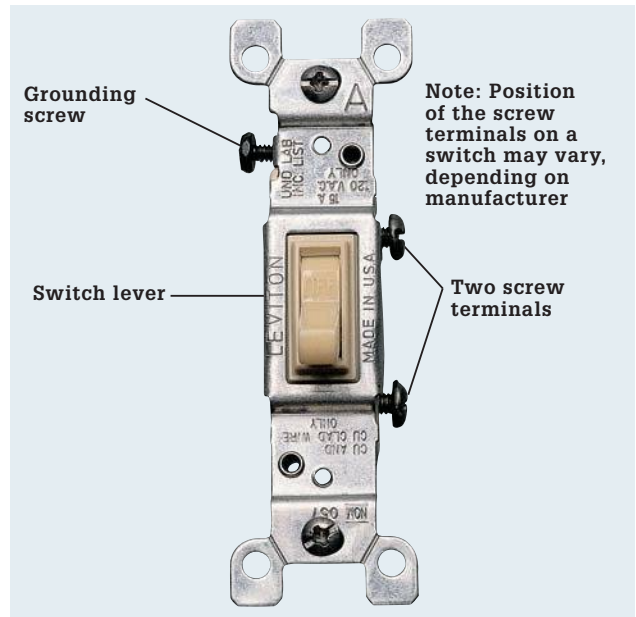If only one cable enters the box, then the switch lies at the end of the circuit. In this installation (sometimes called a switch loop), one of the hot wires is black, but the other hot wire usually is white. A white hot wire should be coded with black tape or paint.




A single-pole switch is essentially an interruption in the black power supply wire that is opened or closed with the toggle. Single-pole switches are the simplest of all home wiring switches.


Typical Single-Pole Switch Installations

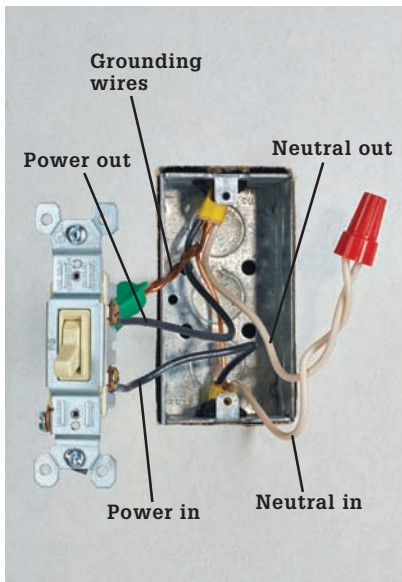

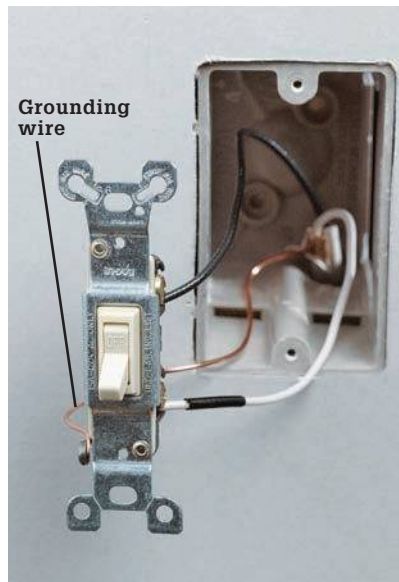Two cables enter the box when a switch is located in the middle of a circuit. Each cable has a white and a black insulated wire, plus a bare copper grounding wire. The black wires are hot and are connected to the screw terminals on the switch. The white wires are neutral and are joined together with a wire connector. Grounding wires are pigtailed to the switch.



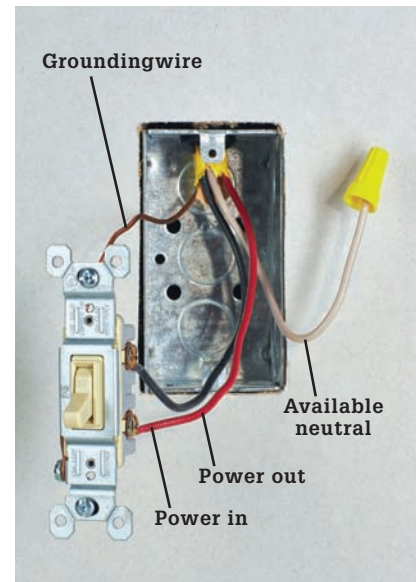Old method: One cable enters the box when a switch is located at the end of a circuit. In this installation, both of the insulated wires are hot. The white wire should be labeled with black tape or paint to identify it as a hot wire. The grounding wire is connected to the switch grounding screw.



Code change: In new switch wiring, the white wire should not supply current to the switched device and a separate neutral wire should be available in the switch box.


Three-Way Wall Switches

Three-way switches have three screw terminals and do not have ON-OFF markings. Three-way switches are always installed in pairs and are used to control a set of lights from two locations.


One of the screw terminals on a three-way switch is darker than the others. This screw is the common screw terminal. The position of the common screw terminal on the switch body may vary, depending on the manufacturer. Before disconnecting a three-way switch, always label the wire that is connected to the common screw terminal. It must be reconnected to the common screw terminal on the new switch.

The two lighter-colored screw terminals on a three-way switch are called the traveler screw terminals. The traveler terminals are interchangeable, so there is no need to label the wires attached to them.

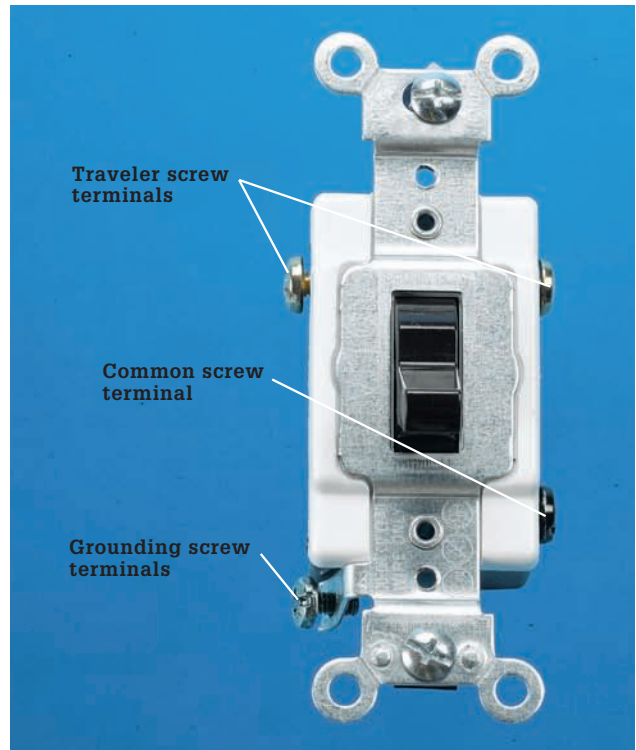Because three-way switches are installed in pairs, it sometimes is difficult to determine which of the switches is causing a problem. The switch that receives greater use is more likely to fail, but you may need to inspect both switches to find the source of the problem.




Typical Three-Way Switch Installation

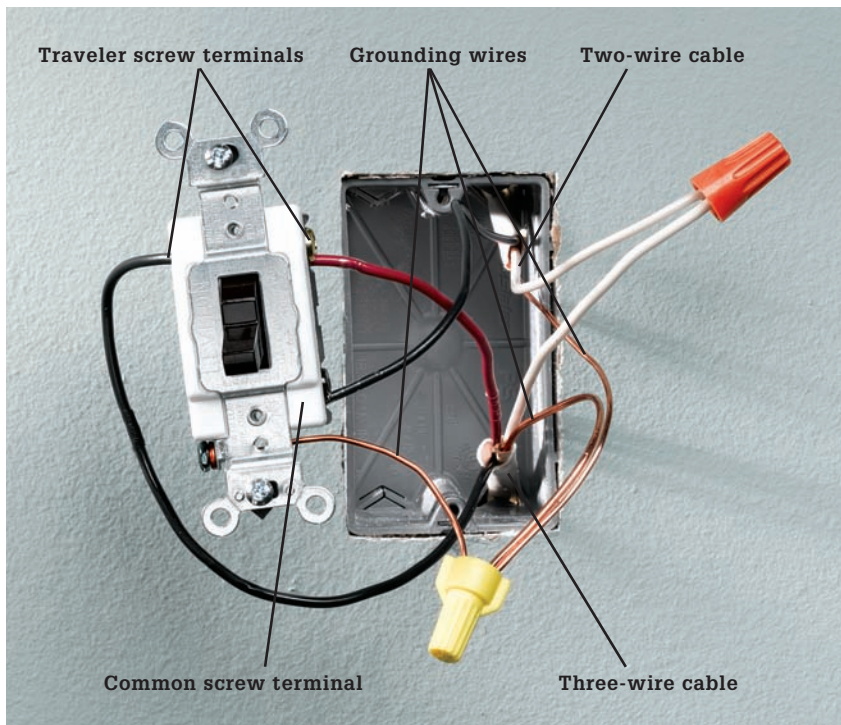


Two cables enter the box: one cable has two wires, plus a bare copper grounding wire; the other cable has three wires, plus a ground. The black wire from the two-wire cable is connected to the dark common screw terminal. The red and black wires from the three-wire cable are connected to the traveler screw terminals. The white neutral wires are joined together with a wire connector, and the grounding wires are pigtailed to the grounded metal box.

How to Replace a Three-Way Wall Switch

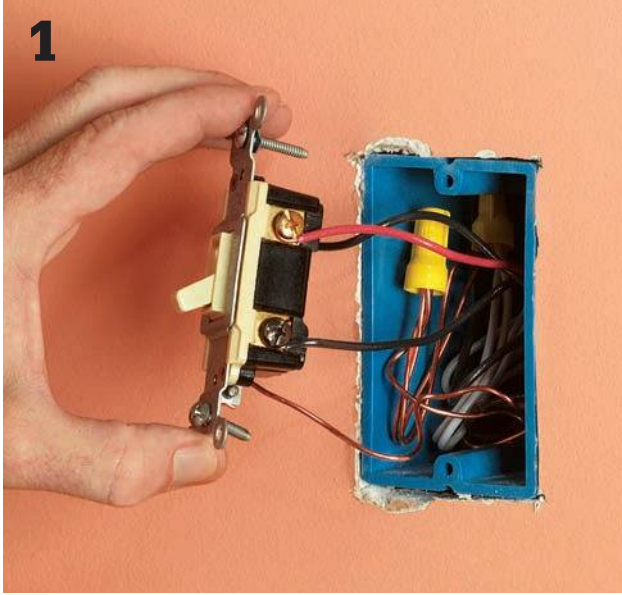

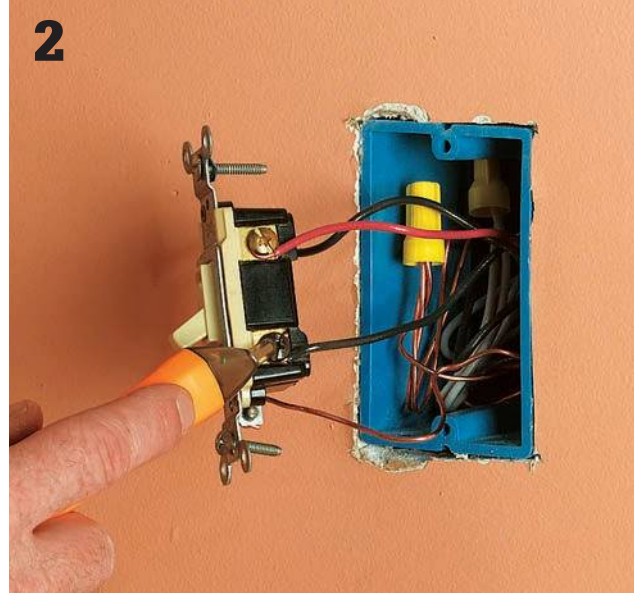1 Turn off the power to the switch at the panel, and then remove the switch cover plate and mounting screws. Holding the mounting strap carefully, pull the switch from the box. Be careful not to touch the bare wires or screw terminals until they have been tested for power. *Note: If you are installing a new switch circuit, you must provide a neutral conductor at the switch.*



2 Test for power by touching one probe of the circuit tester to the grounded metal box or to the bare copper grounding wire and touching the other probe to each screw terminal. Tester should not glow. If it does, there is still power entering the box. Return to the panel, and turn off the correct circuit.



3 Locate the dark common screw terminal, and use masking tape to label the “common” wire attached to it. Disconnect wires and remove switch. Test the switch for continuity. If it tests faulty, buy a replacement. Inspect wires for nicks and scratches. If necessary, clip damaged wires and strip them.



4 Connect the common wire to the dark common screw terminal on the switch. On most three-way switches, the common screw terminal is black. Or it may be labeled with the word COMMON stamped on the back of the switch. Reconnect the grounding screw, and connect it to the circuit grounding wires with a pigtail.




5 Connect the remaining two circuit wires to the screw terminals. These wires are interchangeable and can be connected to either screw terminal. Carefully tuck the wires into the box. Remount the switch, and attach the cover plate. Turn on the power at the panel.


Four-Way Wall Switches

Four-way switches have four screw terminals and do not have ON-OFF markings. Four-way switches are always installed between a pair of three-way switches. This switch combination makes it possible to control a set of lights from three or more locations. Four-way switches are common in homes where large rooms contain multiple living areas, such as a kitchen opening into a dining room. Switch problems in a four-way installation can be caused by loose connections or worn parts in a four-way switch or in one of the three-way switches (facing page).


In a typical installation, there will be a pair of three-wire cables that enter the box for the four-way switch. With most switches, the white and red wires from one cable should be attached to the bottom or top pair of screw terminals, and the white and red wires from the other cable should be attached to the remaining pair of screw terminals. However, not all switches are configured the same way, and wiring configurations in the box may vary, so always study the wiring diagram that comes with the switch.

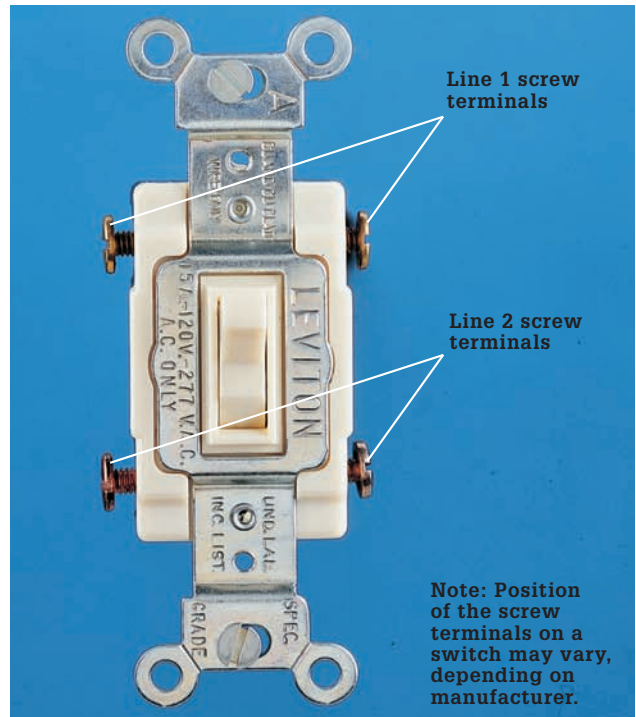

Typical Four-Way Switch Installation

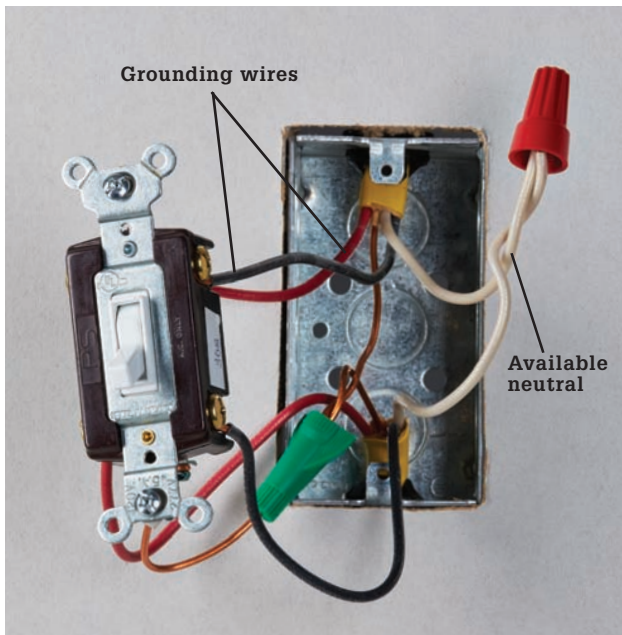


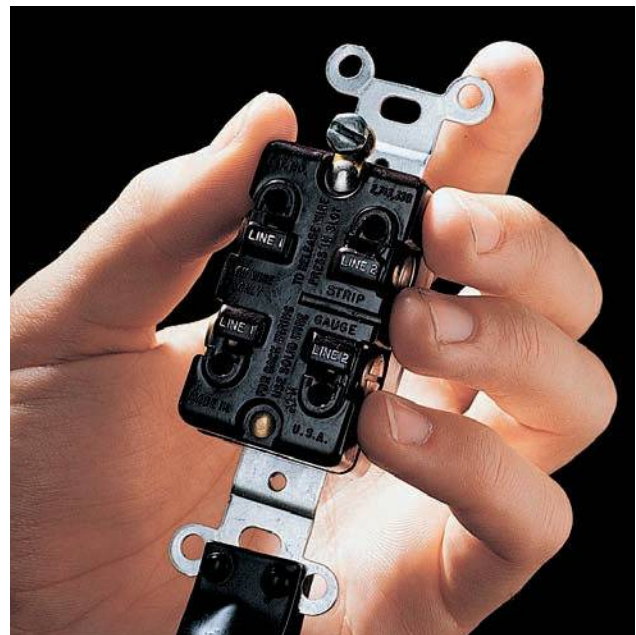Four wires are connected to a four-way switch. The red and white wires from one cable are attached to the top pair of screw terminals, while the red and white wires from the other cable are attached to the bottom screw terminals. In new switch wiring, the white wire should not supply current to the switched device, and a separate neutral wire should be available in the switch box.




Switch variation: Some four-way switches have a wiring guide stamped on the back to help simplify installation. For the switch shown above, one pair of color-matched circuit wires will be connected to the screw terminals marked LINE 1, while the other pair of wires will be attached to the screw terminals marked LINE 2.


How to Replace a Four-Way Wall Switch

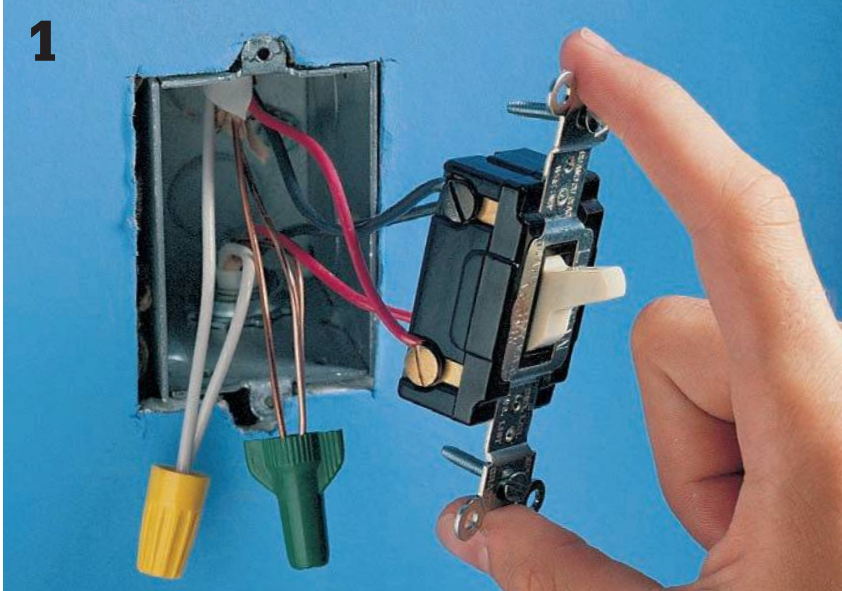


1 Turn off the power to the switch at the panel, and then remove the switch cover plate and mounting screws. Holding the mounting strap carefully, pull the switch from the box. Be careful not to touch any bare wires or screw terminals until they have been tested for power. Test for power by touching one probe of the neon circuit tester to the grounded metal box or bare copper grounding wire and touching the other probe to each of the screw terminals. The tester should not glow. If it does, there is still power entering the box. Return to the panel, and turn off the correct circuit.

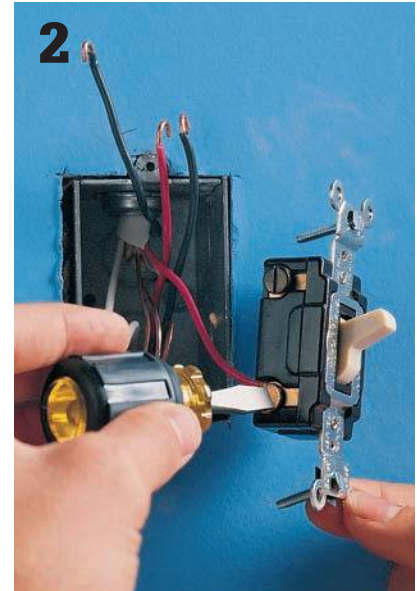

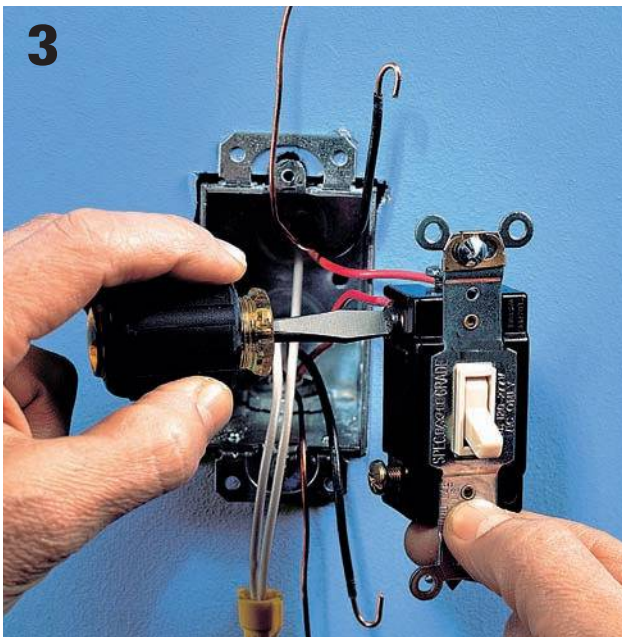2 Disconnect the wires and inspect them for nicks and scratches. If necessary, clip damaged wires and strip them. Test the switch for continuity. Buy a replacement if the switch tests faulty.



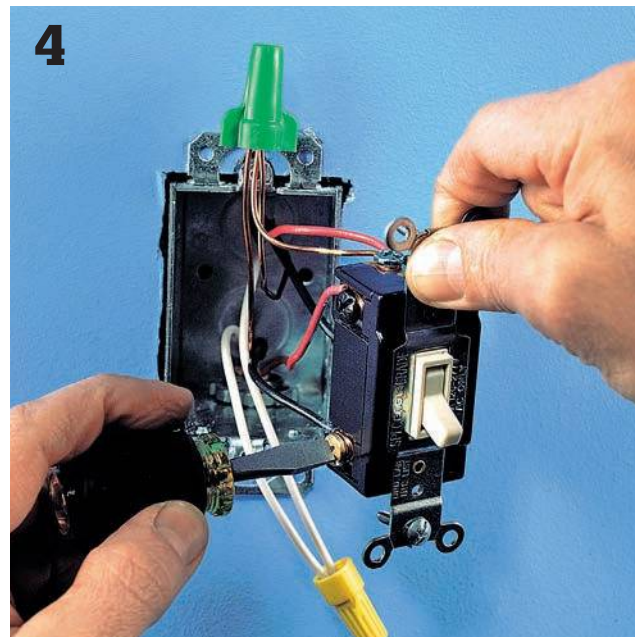3 Connect two wires from one incoming cable to the top set of screw terminals.




4 Attach remaining wires to the other set of screw terminals. Pigtail the grounding wires to the grounding screw. Carefully tuck the wires inside the switch box, and then remount the switch and cover plate. Turn on power at the panel.

Double Switches


A double switch has two switch levers in a single housing. It is used to control two light fixtures or appliances from the same switch box.

In most installations, both halves of the switch are powered by the same circuit. In these single-circuit installations, three wires are connected to the double switch. One wire, called the feed wire (which is hot), supplies power to both halves of the switch. The other wires, called the switch leg, carry power out to the individual light fixtures or appliances.

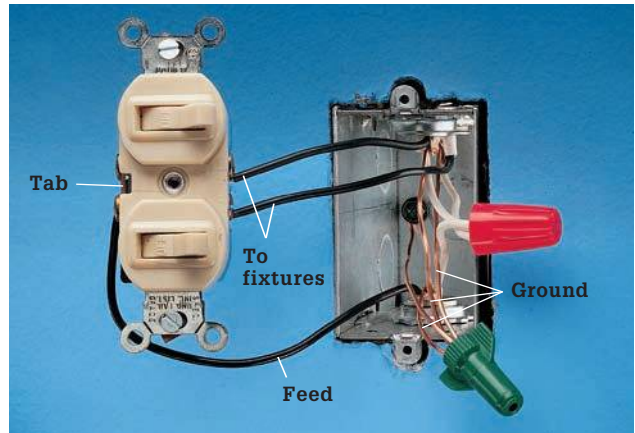
In rare installations, each half of the switch is powered by a separate circuit. In these separate-circuit installations, four wires are connected to the switch, and the metal connecting tab joining two of the screw terminals is removed (see photo below).



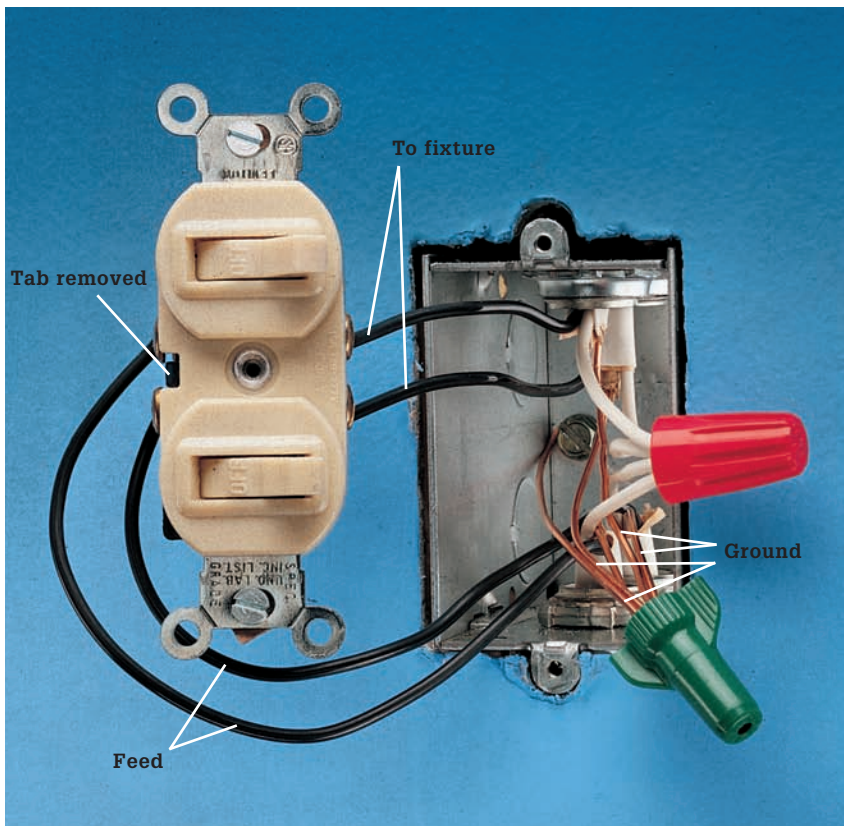Single-circuit wiring: Three black wires are attached to the switch. The black feed wire bringing power into the box is connected to the side of the switch that has a connecting tab. The wires carrying power out to the light fixtures or appliances are connected to the side of the switch that does not have a connecting tab. The white neutral wires are connected together with a wire connector.



Separate-circuit wiring: Four black wires are attached to the switch. Feed wires from the power source are attached to the side of the switch that has a connecting tab, and the connecting tab is removed (photo, right). Wires carrying power from the switch to light fixtures or appliances are connected to the side of the switch that does not have a connecting tab. White neutral wires are connected together with a wire connector.

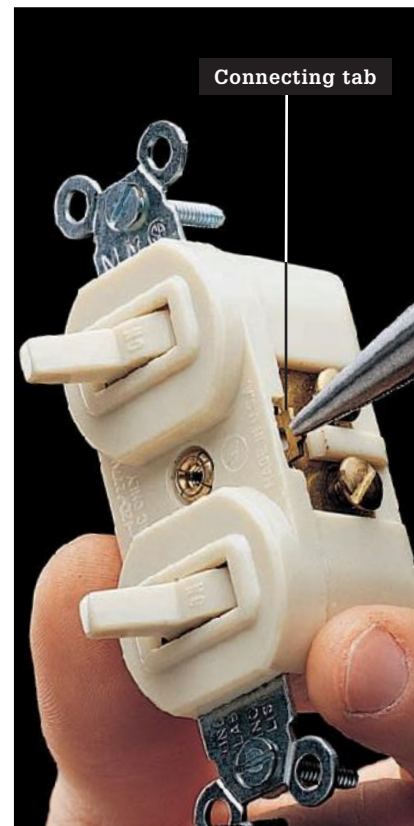


Remove the connecting tab on a double switch when wired in a separate-circuit installation. The tab can be removed with needle-nose pliers or a screwdriver.

Pilot-Light Switches

A pilot-light switch has a built-in bulb that glows when power flows through the switch to a light fixture or appliance. Pilot-light switches often are installed for convenience if a light fixture or appliance cannot be seen from the switch location. Basement lights, garage lights, and attic exhaust fans frequently are controlled by pilot-light switches.

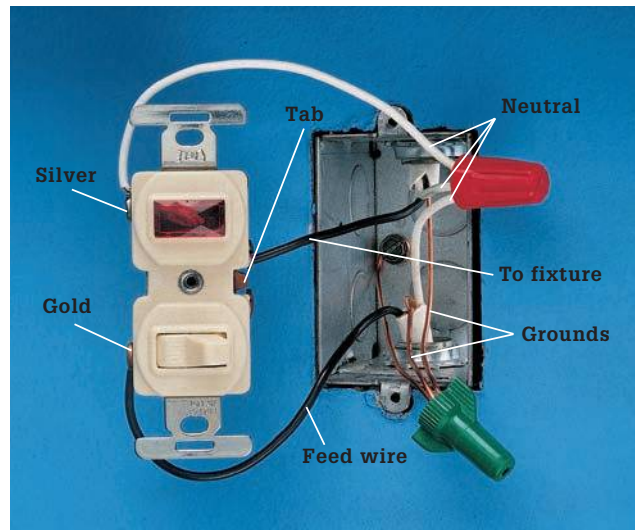A pilot-light switch requires a neutral wire connection. A switch box that contains a single two-wire cable has only hot wires and cannot be fitted with a pilot-light switch.



Pilot-light switch wiring: Three wires are connected to the switch. One black wire is the feed wire that brings power into the box. It is connected to the brass (gold) screw terminal on the side of the switch that does not have a connecting tab. The white neutral wires are pigtailed to the silver screw terminal. The black wire carrying power out to a light fixture or appliance is connected to the screw terminal on the side of the switch that has a connecting tab.


Switch/Receptacles

A switch/receptacle combines a grounded receptacle with a single-pole wall switch. In a room that does not have enough wall receptacles, electrical service can be improved by replacing a single-pole switch with a switch/receptacle.

A switch/receptacle requires a neutral wire connection. A switch box that contains a single two-wire cable has only hot wires and cannot be fitted with a switch/receptacle.

A switch/receptacle can be installed in one of two ways. In the most common installations, the receptacle is hot even when the switch is off (photo, right).

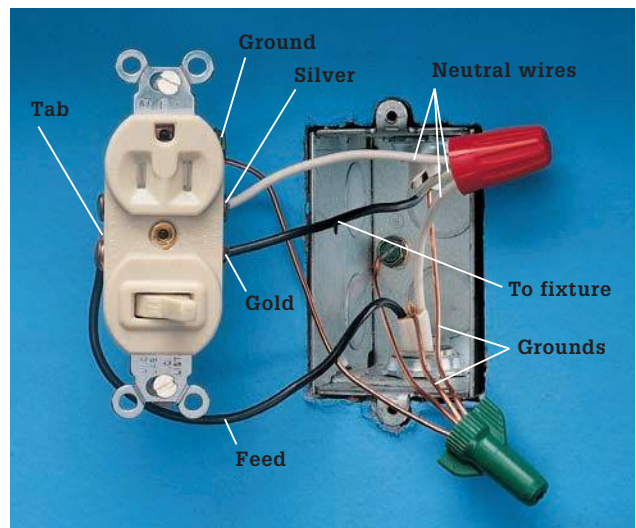In rare installations, a switch/receptacle is wired so the receptacle is hot only when the switch is on. In this installation, the hot wires are reversed, so that the feed wire is attached to the brass screw terminal on the side of the switch that does not have a connecting tab.



Switch/receptacle wiring: Three wires are connected to the switch/receptacle. One of the hot wires is the feed wire that brings power into the box. It is connected to the side of the switch that has a connecting tab. The other hot wire carries power out to the light fixture or appliance. It is connected to the brass screw terminal on the side that does not have a connecting tab. The white neutral wire is pigtailed to the silver screw terminal. The grounding wires must be pigtailed to the green grounding screw on the switch/receptacle and to the grounded metal box.

Specialty Switches

Your house may have several types of specialty switches. Dimmer switches (pages 96 to 97) are used frequently to control light intensity in dining and recreation areas. Timer switches and time-delay switches (below) are used to control light fixtures and exhaust fans automatically. Electronic switches provide added convenience and home security, and they are easy to install. Electronic switches are durable, and they rarely need replacement.

Most specialty switches have preattached wire leads instead of screw terminals and are connected to circuit wires with wire connectors. Some motor-driven timer switches require a neutral wire connection and

cannot be installed in switch boxes that have only one cable with two hot wires. It is precisely due to the rise in popularity of “smart” switches that the NEC Code was changed in 2014 to require an available neutral wire in newly-installed switch boxes.

If a specialty switch is not operating correctly, you may be able to test it with a continuity tester. Timer switches and time-delay switches can be tested for continuity, but dimmer switches cannot be tested. With electronic switches, the manual switch can be tested for continuity, but the automatic features cannot be tested.

Timer Switches

Countdown timer switches can be set to turn lights or fans on and off automatically once each day. They are commonly used to control outdoor light fixtures.


Timer switches have three preattached wire leads. The black wire lead is connected to the hot feed wire that brings power into the box, and the red lead is connected to the wire carrying power out

to the light fixture. The remaining wire lead is the neutral lead. It must be connected to any neutral circuit wires. A switch box that contains only one cable has no neutral wires, so it cannot be fitted with a timer switch.


After a power failure, the dial on a timer switch must be reset to the proper time.



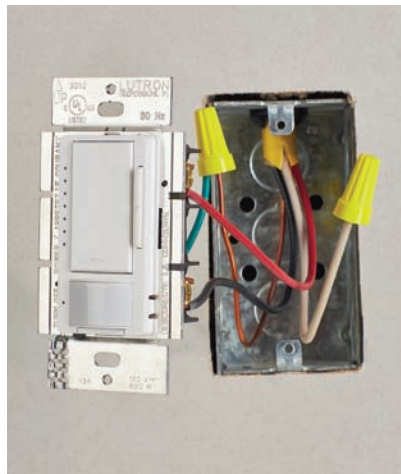
Countdown timer switch. This rocker-type switch gives you the option to easily program the switch to shut off after a specified time: from 5 to 60 minutes. Garage lights or basement lights are good applications: anywhere you want the light to stay on long enough to allow you to exit, but not to stay on indefinitely. These switches often are used to control vent fans.



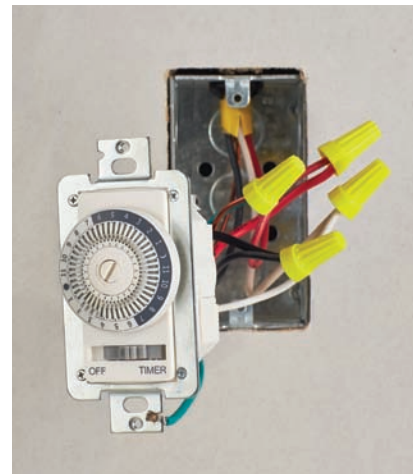
Occupancy sensor. Many smart switches incorporate a motion detector that will switch the lights on if they sense movement in the room and will also shut them off when no movement is detected for a period of time. The model shown above also has a dimmer function for further energy savings.



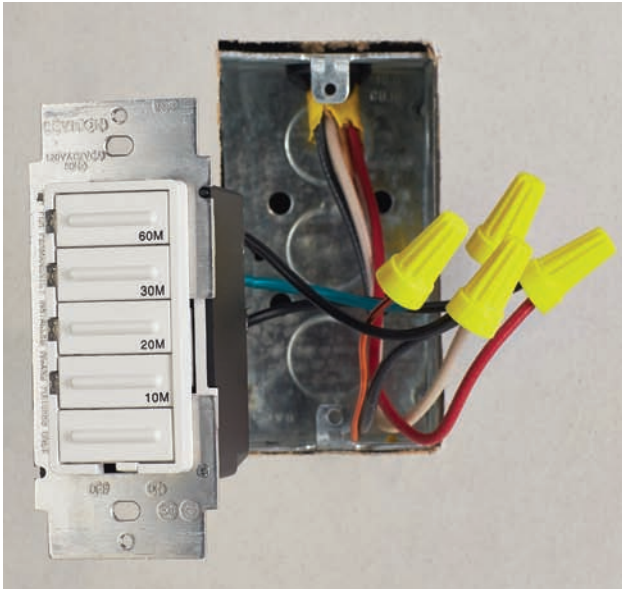
Programmable timer switch. A dial-type timer allows you to program the switch to turn on for specific time periods at designated times of day within a 24-hour cycle. Security lights, space heaters, towel warmers, and radiant floors are typical applications.



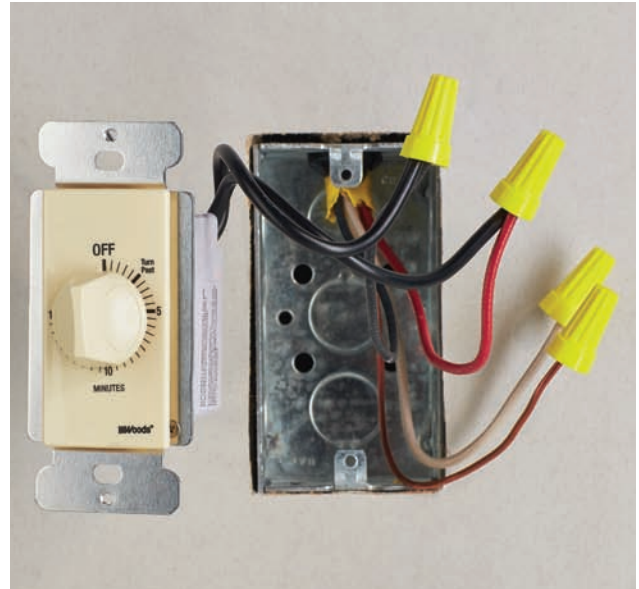
Preset timer switch. This lets you turn on lights, heat lamps, and other loads for a designated amount of time (10 to 60 minutes) with one easy push of a button. The green LED at the bottom of this unit provides a readout of how much time is left before the switch shuts off. The model shown is not compatible with fluorescent ballasts.



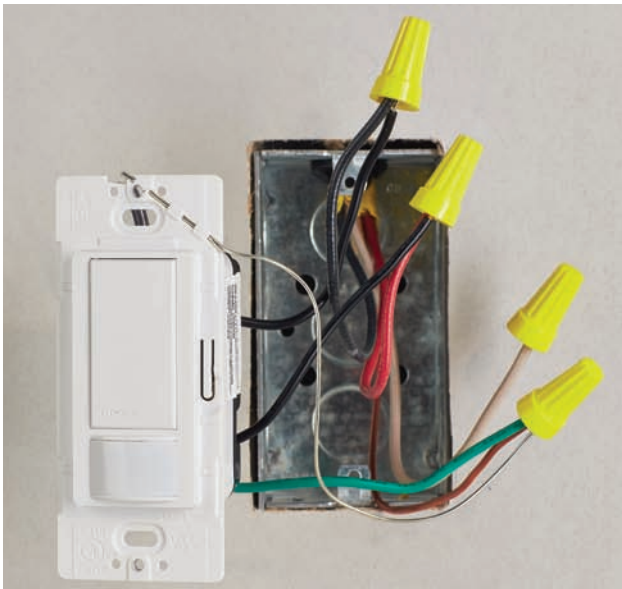Spring-wound timer switch. A relatively simple device, this timer switch functions exactly like a kitchen timer, employing a hand-turned dial to and spring mechanism to shut the switch off in increments up to 15 minutes.



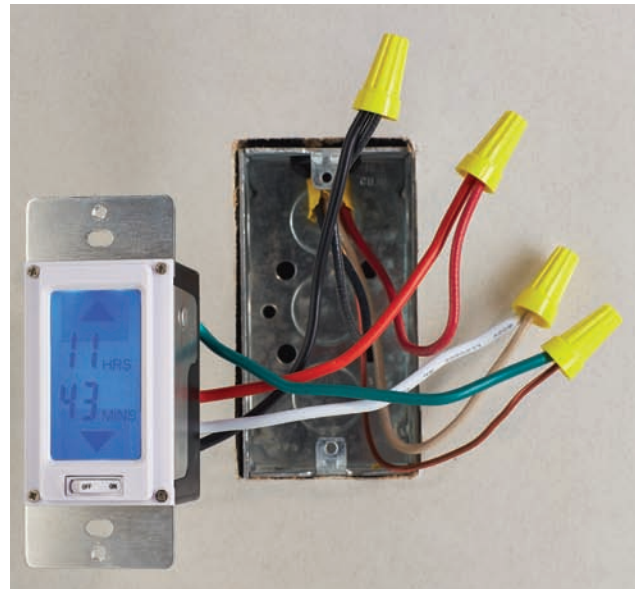Daylight sensor switch. This switch automatically turns on when light levels drop below a proscribed level. It can also be programmed as an occupancy sensor to shut off when the room is vacant and turn on when the room is entered.



Backlit countdown timer. This digital switch lets you program lights or other devices to stay on for up to 24 hours and then shut off automatically. The backlit, LED readout gives a countdown, in minutes, of the amount of time left in the "on" cycle. Up and down buttons let you raise or lower the remaining time easily, and a manual override button will shut off the switch until it is turned back on.

Ground-fault (GFCI) & Arc-fault (AFCI) Protection

GROUND-FAULT LOCATION REQUIREMENTS

1. Kitchen receptacles. Install ground-fault circuit interrupt (GFCI) protection on all 120-volt receptacles that serve kitchen countertops. This does not include receptacles under the kitchen sink receptacles located on kitchen walls that do not serve the countertop and receptacles that are not within six feet of a sink.
2. Kitchen. Install ground-fault circuit interrupt (GFCI) protection on the outlets that supply dishwashing machines.
3. Bathroom receptacles. Install ground-fault circuit interrupt (GFCI) protection on all 120-volt receptacles located in bathrooms. This applies to all receptacles regardless of where they are located in the bathroom and includes receptacles located at countertops, inside cabinets, and along bathroom walls. This also applies to bathtubs and shower stalls that are not located in a bathroom. Install ground-fault circuit interrupt (GFCI) protection on all circuits serving electrically heated floors in bathrooms, kitchens, and around whirlpool tubs, spas, and hot tubs.
4. Garage and Accessory Building receptacles. Install ground-fault circuit interrupt (GFCI) protection on all 120-volt receptacles located in garages and grade-level areas of unfinished accessory buildings.
5. Exterior receptacles. Install ground-fault circuit interrupt (GFCI) protection on all 120-volt receptacles located outdoors. This does not apply to receptacles that are dedicated for deicing equipment and are located under the eaves. This applies to holiday lighting receptacles located under the eaves.
6. Basement receptacles. Install ground-fault circuit interrupt (GFCI) protection on all 120-volt receptacles located in unfinished basements. An unfinished basement is not intended as habitable space and is limited to storage and work space.
7. Crawl space receptacles. Install ground-fault circuit interrupt (GFCI) protection on all 120-volt receptacles located in crawl spaces. Receptacles in crawl spaces are not required unless equipment requiring service is located there.
8. Sink receptacles. Install ground-fault circuit interrupt (GFCI) protection on all 120-volt receptacles that are located within six feet of the outside edge of a sink. This includes wall, floor, and countertop receptacles.
9. Boathouse receptacles. Install ground-fault circuit interrupt (GFCI) protection on all 120-volt receptacles located in boathouses.



Ground-fault receptacles and circuit breakers detect unwanted current running between an energized wire and a grounded wire.



A combination ARC-fault circuit breaker detects sparking (arcing) faults along damaged energized wires and detects these faults between wires. A branch ARC-fault circuit breaker only detects arcing faults between wires.

10. Spas, tubs, and other circuits requiring ground-fault protection. Install ground-fault circuit interrupt (GFCI) protection on all circuits serving spa tubs, whirlpool tubs, hot tubs, and similar equipment. Refer to the general codes for more information about receptacles serving these components.
11. Install GFCI circuit breakers and receptacles so that they are readily accessible.

ARC-FAULT LOCATION REQUIREMENTS

1. Install a combination type or an outlet (receptacle) type arc-fault circuit interrupter (AFCI) on all 15- and 20-amp, 120-volt branch circuits serving sleeping, family, dining, living, sun, and recreation rooms, kitchens, laundry areas, and parlors, libraries, dens, hallways, closets, and similar rooms and areas. This means that 15- and 20-amp, 120-volt branch circuits serving most interior spaces in a home are required to have AFCI protection. Note that garages, basements, utility and mechanical rooms, and exterior branch circuits are not included in
2. You may provide AFCI protection for the entire branch circuit by installing a combination-type AFCI circuit breaker in the electrical panel where the branch circuit originates.
3. You may provide AFCI protection to a branch circuit using several different combinations of branch-circuit type AFCI circuit breakers and branch-circuit type AFCI receptacles. Refer to general codes or your local building inspector for details about these alternate methods.
4. Provide AFCI for branch circuits that are modified, replaced, or extended. You may use either of the following methods: (a) install a combination-type AFCI circuit breaker in the electrical panel where the branch circuit originates, or (b) install a branch-circuit type AFCI receptacle at the first receptacle in the existing branch circuit.
5. Install AFCI circuit breakers and receptacles so that they are readily accessible.



Receptacles for whirlpool tubs must be GFCI protected.

Junction Boxes, Device Boxes & Enclosures


All electrical boxes are available in different depths. A box must be deep enough so a switch or receptacle can be removed or installed easily without crimping and damaging the circuit wires. Replace an undersized box with a larger box using the Electrical Box Fill Chart (see page 124) as a guide. **The NEC also says that all electrical boxes must remain accessible. Never cover an electrical box with drywall, paneling, or wall coverings.**

NONMETALLIC BOX INSTALLATION

1. Use nonmetallic boxes only with NM type cable or with nonmetallic conduit or tubing. You may use nonmetallic boxes with metallic conduit or tubing if you maintain the electrical continuity of the metallic conduit or tubing by installing a bonding jumper through the box. In many situations it is easier to use a metallic box with metallic conduit or tubing.
2. Extend NM cable sheathing at least $\frac{1}{4}$ inch into a nonmetallic box knockout opening.
3. Secure NM cable, conduit, and tubing to each box. You may secure NM cable with cable clamps inside the box or with compression tabs provided where the cable enters the box. You do not need to secure NM cable to a standard single-gang box ($2\frac{1}{4}$ by 4 inches) mounted in a wall or ceiling if you fasten the cable not more than eight inches from the box and if the sheathing enters the box at least $\frac{1}{4}$ inch. Measure the eight inches along the length of the sheathing, not from the outside of the box.

LIGHT FIXTURE BOX INSTALLATION

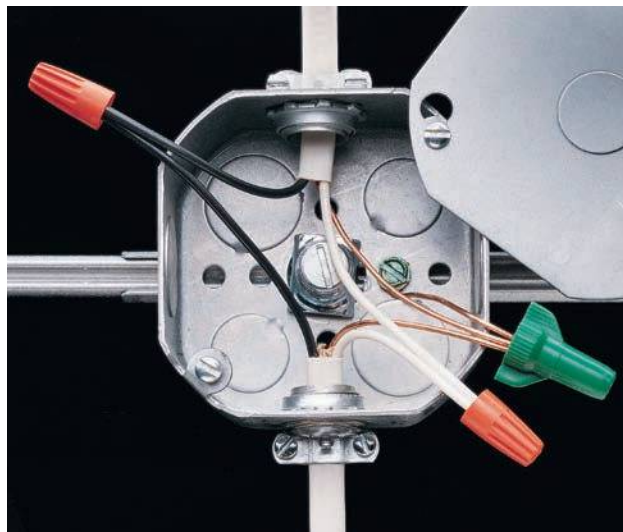1. Use boxes designed for mounting light fixtures if a light fixture is to be mounted to the box. These boxes are usually four-inch round or octagonal.
2. You may use other boxes to mount light fixtures on walls if the fixture weighs less than 6 pounds and if the fixture is secured to the box using at least #6 screws.
3. Support light fixtures weighing at least 50 pounds independently from the light fixture box. You may use the light fixture box to support light fixtures weighing less than 50 pounds. Note that ceiling fans are not light fixtures.



Box shape is directly related to function, as electrical fixtures are created to fit on boxes of a particular shape. Octagonal and round boxes generally are designed for ceiling mounting, while square and rectangular boxes are sized for single-pole, duplex, and other standard switch and receptacle sizes.



Do not support heavy light fixtures using only the light fixture electrical box. The eye hook supporting this chandelier is driven into the same ceiling joist to which the electrical box is mounted.

BOX CONTENTS LIMITATIONS

1. Limit the number of wires, devices (such as switches and receptacles), and fittings in a box. This limitation is primarily based on the heat generated by the wires and devices in the box. The actual size of the box relative to its contents is a secondary consideration.
2. Use the cubic inch volume printed on the box or provided in the box manufacturer's instructions to determine box volume. Do not attempt to measure the box volume. Do not estimate box volume from the volume of similar size boxes. You will probably not get the same volume as provided by the manufacturer.
3. Use table "Wire Volume Unit" to determine the volume units required by wires, devices, and fittings in a box.

BOX INSTALLATION TOLERANCES

1. Install boxes in non-combustible material, such as masonry, so that the front edge is not more than $\frac{1}{4}$ inch from the finished surface.
2. Install boxes in walls and ceilings made of wood or other combustible material so that the front edge is flush with the finished surface or projects from the finished surface.
3. Cut openings for boxes in drywall and plaster so that the opening is not more than $\frac{1}{8}$ inch from the perimeter of the box.



Boxes must be installed so the front edges are flush with the finished wall surface, and the gap between the box and the wall covering is not more than $\frac{1}{8}$ ".

Wire Volume Unit ▶

| WIRE SIZE (AWG) | WIRE VOLUME |
|-----------------|-----------------------|
| 14 | 2.00 in. ³ |
| 12 | 2.25 in. ³ |
| 10 | 2.50 in. ³ |
| 8 | 3.00 in. ³ |
| 6 | 5.00 in. ³ |

Volume Units ▶

Calculate the volume units required by wires, devices, and fittings based on the following definitions:

Volume units for current-carrying wires. Allow one volume unit for each individual hot (ungrounded) and neutral (grounded) wire in the box. Use Table 47 to determine the volume units of common wire sizes. Example: two pieces of #14/2 NM are in a box. Each piece of this cable contains one hot (ungrounded) and one neutral (grounded) wire and one grounding wire. From table "Wire Volume Unit", each #14 wire uses 2.00 cubic inches in the box. The total volume units required by the hot (ungrounded) and neutral (grounded) wires is eight cubic inches.

Volume units for devices. Allow two volume units for each device (switch or receptacle) in the box. Base the volume units on the largest hot (ungrounded) or neutral (grounded) wire in the box. Example: NM cable size #14 and #12 are in a

box. From Table 47, #14 wire uses 2.00 cubic inches and #12 wire uses 2.25 cubic inches. Allow 4.5 cubic inches volume units (2×2.25 cubic inches) for each switch or receptacle in the box based on the volume of the larger #12 NM cable.

Volume units for grounding wires. Allow one volume unit for all grounding wires in the box. Base the volume unit on the largest hot (ungrounded) or neutral (grounded) wire in the box.

Volume units for clamps. Allow one volume unit for all internal cable clamps in the box, if any. Base the volume unit on the largest hot (ungrounded) or neutral (grounded) wire in the box.

Volume units for fittings. Allow one volume unit for all fittings in the box, if any. Base the volume unit on the largest hot (ungrounded) or neutral (grounded) wire in the box.

Resources

Applied Energy Innovations

Solar, wind, geothermal installations
612 532 0384
www.appliedenergyinnovations.org

Black & Decker

Portable power tools and more
www.blackanddecker.com

Broan-NuTone, LLC

Vent fans
800 558 1711
www.broan.com

Generac Power Systems

Standby generators and switches
888 436 3722
www.generac.com

Honda Power Equipment/ American Honda Motor Company, Inc.

Standby generators
770 497 6400
www.hondapowerequipment.com

Kohler

Standby generators
800 544 2444
www.kohlergenerators.com

Pass & Seymour Legrand

Home automation products
877 295 3472

www.passandseymour.com

Unistrut Metal Framing

Solar panel mounts
www.unistrut.com

Westinghouse

Ceiling fans, decorative lighting, solar outdoor lighting, & other lighting fixtures and bulbs
866 442 7873
Purchase here: www.budgetlighting.com
www.westinghouse.com

Photo Credits

p. 53 photo © Mike Clarke / www.istock.com

p. 74 photo © Jeff Chevrier / www.istock.com

p. 75 photos (top right & lower) courtesy of Generac Power Systems, Inc.

p. 86 photo courtesy of Cabin Fever, featuring McMaster Carr vapor-tight light fixtures

Index

- A**
AFCI (arc fault circuit interruption) breakers
 installation, 49
 location requirements, 121
 NEC requirements, 48
 vs. GFCI, 48
air conditioners, central, wattage of, 19
air conditioners, window
 circuits for, 40
 wattage of, 19
amperage
 evaluating loads and, 16
 measuring with multimeter, 103
appliances
 circuits for high-wattage, 39–40
 circuits from small, 38
 NEC requirements, 11
arc fault circuit interruption (AFCI) breakers.
 See AFCI (arc fault circuit interruption)
 breakers
arc-fault location requirements, 121
- B**
backup power supply
 transfer switch types, 77
 types of, 74–75
 typical system layout, 76
 See also generators
baseboard heaters
 calculating heating needs, 69
 circuits for, 39, 68–69
 installation, 240-volt, 70–71
 thermostats for, 69
basements, 120, 121
bathrooms
 circuits for, 32, 41
 ground-fault protection requirements,
 120–121
 NEC requirements, 11, 13
batteries
 for DC lighting circuits, 100
 measuring voltage with multimeter, 104
bedrooms, NEC requirements, 13
boathouses, 120
bonding wiring systems, 58–63
boxes. *See* electrical boxes
branch circuits, 121
breakers. *See* circuit breakers
- C**
cables
 NEC requirements, 12
 nonmetallic electrical boxes and, 122
 in outbuildings, 90–91, 93
 volume of in electrical boxes, 123
 volume unit chart for electrical boxes, 123
catastrophe fuses, 100
ceiling fans
 circuits for, 47
 supporting, 122
 See also light fixtures
ceilings
 electrical boxes in, 122–123, 124
 light fixtures in circuit maps, 47
 shutting off power for work in, 7
 See also ceiling fans; light fixtures
central air conditioners, wattage of, 19
circuit breaker panels
 NEC requirements, 12
 See also service panels
circuit breakers
 AFCI
 installation, 49
 NEC requirements, 48, 120
 vs. GFCI, 48
 compatibility, 7
 exercising, 61
 GFCI
 installation, 49
 vs. AFCI, 48
 measuring current at, 103
 short circuit troubleshooting, 108–109
 slimline breakers, 64
circuit indexes, 6, 55
circuit maps, 32–47
circuits
 arc-fault protection requirements, 121
 diagnostic tools for testing, 101, 102
 evaluating loads on, 9, 16–19
 generators and backup, 81
 maps for, 32–47
 NEC requirements for, 11
 open neutral troubleshooting, 106–107
 sample kitchen project, 26–29
 sample room addition, 22–25
 troubleshooting short circuits, 108–109
clamp-on multimeters, 103
clothes dryers, wattage of, 19
computers, 40
conduit, nonmetallic electrical boxes and, 122
continuity, testing for, 105
crawl spaces, 120
current, measuring, 103.
 See also amperage
- D**
device boxes. *See* electrical boxes
diagnostic tools, 101
dining rooms, 13
dishwashers, 18, 120
dryers. *See* clothes dryers
duplex receptacles. *See* receptacles
- E**
electrical boxes
 about nonmetallic, 122
 accessibility and, 122
 content limits of, 123
 damp/wet locations and, 124
 depth of, 122
 fill chart for, 124
 inspections and, 14–15
 installation tolerances, 123
 labeling, 15
 light fixtures, 122
 NEC requirements, 12, 122
 in outbuilding, 90–92
 shape of, 122
 volume unit chart, 123
electrical loads
 evaluating, 9, 16–19
 locating wattage information, 18–19
electrical symbols, 21
electric meters, service panel upgrades/
 replacements and, 56–57
electric ranges
 in circuit maps, 39
 wattage of, 18
extension cords, 7
- F**
fixtures
 NEC requirements, 12
 See also light fixtures
food disposers, 18
forced-air furnaces, wattage of, 19
freezers, 19
fuse panels. *See* service panels
fuses
 catastrophe, 100
 compatibility, 7
- G**
garages, 120, 121
garbage disposals, 18
gas pipes, metal, 59–60
generators
 automatic standby, 79, 85
 choosing, 76, 77
 manual transfer switch installation, 80–84
 outage operation of portable, 79
 selecting backup circuits, 81
 types of, 74–75
 typical system layout, 76
 See also backup power supply
GFCI (ground-fault circuit interrupter) breakers
 installation, 49
 location requirements, 120–121
 vs. AFCI, 48
GFCI (ground-fault circuit interrupter)
 receptacles, 120–121
ground fault circuit interrupter (GFCI) breakers.
 See GFCI (ground-fault circuit interrupter)
 breakers
ground fault circuit interrupter (GFCI)
 receptacles. *See* GFCI (ground-fault circuit
 interrupter) receptacles
ground-fault protection location requirements,
 120–121
grounding
 service panel upgrades/replacements, 56
 wiring systems, 58–63
grounding electrode systems, 61–63
grounding rods, installing, 58, 61–63
- H**
hallways, 13
heating and air conditioning
 baseboard heater installation, 70–71
 evaluation of electrical loads and, 17
 thermostats for baseboard heaters, 69
 wall heater installation, 72–73
- I**
inspections
 planning projects and, 9
 preparing for, 14–15
 service panel upgrades and, 57
inspectors, 11
- J**
junction boxes. *See* electrical boxes
- K**
kitchens
 arc-fault protection requirements, 121
 circuits for, 32
 GFCI requirements, 120
 NEC requirements, 11, 13
 receptacle spacing in, 15
 sample project circuits, 26–27
- L**
laundry rooms
 arc-fault protection requirements, 121
 NEC requirements, 13
light bulbs, wattage of, 18
light fixtures
 ceiling fans, 47, 122

- in circuit maps, 33–35, 41–47
- DC circuits for, 97–100
- electrical boxes for, 122
- evaluation of electrical loads and, 17
- NEC requirements, 11, 12
- in outbuildings, 92
- supporting, 122

- living areas
 - arc-fault protection requirements, 121
 - NEC requirements, 11, 13
 - sample room addition
 - circuits for, 22–23
 - wiring diagrams for, 24–25

- local codes, 11
 - See also National Electrical Code

M

- main service panels. See service panels
- meters, service panel upgrades/replacements and, 56–57

- microwave ovens, wattage of, 18
- multimeters
 - about, 101, 102
 - measuring current with, 103
 - measuring voltage with, 104
 - testing for continuity, 105
 - types of, 102

N

- National Electrical Code
 - by area, 13
 - bathrooms, 11
 - electrical boxes, 12, 122
 - fixtures, 12
 - grounding, 12
 - grounding and, 58
 - kitchens, 11
 - living areas, 11
 - permanent appliances, 11
 - planning projects and, 8, 11
 - receptacles, 11, 12
 - service panels, 12
 - switch requirements, 12
 - wires/cables, 12
- neon circuit testers, 102

O

- open neutrals
 - about, 106
 - symptoms of, 106
 - troubleshooting, 106–107
- outbuildings
 - about, 86
 - ground-fault protection requirements, 120–121
 - installing wiring in, 88–93
 - materials for wiring, 87
 - wiring plan for connecting to main panel, 65
- outdoors
 - circuits for, 33
 - ground-fault protection requirements, 120–121
 - NEC requirements, 13
 - See also outbuildings
- outlets. See receptacles

P

- permits, 9, 50
- pilot-light switches, 117
- planning
 - evaluating loads, 9, 16–17
 - examining service panels, 8, 9, 10
 - locating wattage information, 18–19
 - National Electrical Code and, 8
 - permits and, 9
 - sample kitchen project wiring diagrams, 28–29
 - sample room addition
 - circuits for, 22–23
 - wiring diagrams for, 24–25

- wiring diagrams, 9
 - drawing, 20–21
 - electrical symbol key, 21
- plug-in testers, 101
- power
 - shutting off, 6
 - testing receptacles for, 6
- PV (photovoltaic) panels, 94–96

R

- receptacles
 - circuit maps containing, 32–33, 35–40, 43
 - GFCI
 - AFCI breakers and, 48
 - location requirements, 120–121
 - inspections and, 14–15
 - measuring current at, 103
 - NEC requirements, 11, 12
 - safety and, 6
 - short circuit troubleshooting, 108–109
 - spacing of, 15
 - switch-controlled split receptacles, 36–37
 - switch/receptacles, 117
 - testing for power, 6, 104
- repairs, 101
- resistance, measuring, 105
- room heaters, 19

S

- safety
 - baseboard heaters and, 68
 - basics of, 6–7
- screw terminals, wall switches, 110
- service drops, 50, 51, 57
- service laterals, 50–51
- service masts
 - safety and, 7
 - short roofs and, 57
- service panels
 - circuit indexes, 6, 55
 - expandability of, 10
 - finding service size of, 10
 - grounding main, 60
 - location of, 52
 - measuring current at, 103
 - NEC requirements, 12
 - outbuildings and, 93
 - planning projects and, 8, 9, 10
 - replacing main, 53–57
 - short circuit troubleshooting, 108–109
 - splicing in box, 177
 - upgrading
 - equipment for, 52
 - new panel location, 52
 - permits for, 50
 - replacing main, 53–57
- short circuits
 - about, 108
 - troubleshooting, 108–109
- sinks, 120
- solar lighting. See standalone solar lighting systems
- speed-control switches, 47
- stairways, 13
- standalone solar lighting systems
 - about, 94–95
 - DC lighting circuit wiring, 97–100
 - PV (photovoltaic) panel installation, 286
- subpanels
 - about, 64
 - connecting to main service panels, 64
 - installation, 65–67
 - outbuildings and, 65, 93
 - wiring diagrams for, 65
- switch-controlled split receptacles, 36–37
- switches
 - in circuit maps, 33–37, 41–47
 - dimmer switches, 47
 - measuring current at, 103
 - NEC requirements, 12

- pilot-light switches, 117
- speed-control, 47
- switch-controlled split receptacles, 36–37
- switch/receptacles, 117
- timer switches, 118–119

T

- thermostats, for baseboard heaters, 69
- timer switches, 118–119
- touchless circuit testers, 101
- troubleshooting
 - about, 101
 - multimeters, 102–105
 - open neutrals, 106–107
 - short circuits, 108–109

U

- ufers, 63
- UL (Underwriters Laboratories), 6
- Underwriters Laboratories (UL), 6
- utility companies, 50, 53
- utility rooms, 13, 121

V

- vent fans, 40
- voltage, measuring, 104
- volume unit chart, for electrical boxes, 123

W

- walls
 - electrical boxes in, 123, 124
 - NEC requirements, 11
 - shutting off power for work in, 7
- wall switches
 - in circuit maps, 33–37, 41–47
 - double switches, 116
 - four-way
 - about, 110, 114
 - in circuit maps, 45–46
 - typical installation, 114
 - four-way replacing, 115
 - installing, 110
 - NEC requirements, 11
 - pilot-light switches, 117
 - screw terminals and, 110
 - single-pole
 - about, 110–111
 - in circuit maps, 33–35, 41
 - typical installation, 111
 - three-way
 - about, 110, 111
 - in circuit maps, 42–44
 - replacing, 112
 - testing, 105
 - typical installation, 111
- water heaters
 - bonding/grounding wiring systems and, 58, 59
 - wattage of, 19
- water pipes, metal bonding, 58–60
- window air conditioners
 - circuits for, 40
 - wattage of, 19
- wires
 - NEC requirements, 12
 - nonmetallic electrical boxes and, 122
 - volume of in electrical boxes, 123
 - volume unit chart for electrical boxes, 123
- wiring diagrams, 9
- wiring plans
 - connecting outbuildings to main panel, 65
 - drawing, 20–21
 - electrical symbol key, 21
 - for sample kitchen project, 28–29
 - for sample room addition, 24–25

WHOLE HOME NEWS

A BLOG ABOUT...
Sustainable Living • Farming
DIY • Gardening • Home Improvement

For even more information on improving your own home or homestead, visit www.wholehomenews.com today! From raising vegetables to raising roofs, it's the one-stop spot for sharing questions and getting answers about the challenges of self-sufficient living.

Brought to you by two publishing imprints of Quarto Publishing Group USA Inc., Voyageur Press and Cool Springs Press, *Whole Home News* is a blog for people interested in the same things we are: self-sufficiency, gardening, home improvement, country living, and sustainability. Our mission is to provide you with information on the latest techniques and trends from industry experts and everyday enthusiasts.

In addition to regular posts written by our volunteer in-house advisory committee, you'll also meet others from the larger enthusiast community dedicated to "doing it for ourselves." Some of these contributors include published authors of bestselling books, magazine and newspaper journalists, freelance writers, media personalities, and industry experts. And you'll also find features from ordinary folks who are equally passionate about these topics.

Join us at www.wholehomenews.com to keep the conversation going. You can also shoot us an email at wholehomenews@quartous.com. We look forward to seeing you online, and thanks for reading!




@wholehomenews

ADVANCED HOME WIRING

Current with 2014-2017 Codes

Ready to Tackle a Demanding Wiring Project?

Professional electricians don't simply jump in and work on large, complicated projects the moment they are certified: there is a progression involved, from apprentice to journeyman to master. For amateur home wiring enthusiasts, the process is similar. You begin with replacing a switch or installing a new overhead light; next, you might add a small circuit or run power to a shed or outbuilding. As your experience and confidence advances, you'll naturally take on new and more complex jobs. Eventually, you'll consider adding a subpanel or even upgrading your main service panel. Or perhaps you'll decide to try something very new and different, such as installing solar panels and direct-current circuitry. By the time you reach this point, your need for information will have changed. You'll still want to keep all of your old wiring manuals around for reference and refreshing, but you'll want a book that deals with higher-level projects. This is why we've published this new edition of *BLACK+DECKER Advanced Home Wiring* and updated it to be current with the 2014 National Electrical Code.

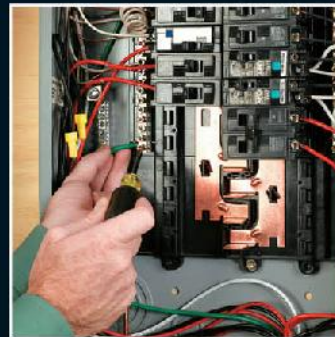

Installing PV Panels



The growing need for less-polluting energy has led to a new wave of solar power. This book provides the information you need to know about solar power, from the basics of how it works to the details of how to install a solar panel on your roof. The book covers everything you need to know to get started, from choosing a solar panel to the details of how to install it. It also includes information on how to get the most out of your solar panel system.



There is a growing need for less-polluting energy. This book provides the information you need to know about solar power, from the basics of how it works to the details of how to install a solar panel on your roof. The book covers everything you need to know to get started, from choosing a solar panel to the details of how to install it. It also includes information on how to get the most out of your solar panel system.

How to Wire a DC Lighting Circuit



How to wire a DC lighting circuit. This book provides the information you need to know about DC lighting, from the basics of how it works to the details of how to install a DC lighting circuit. The book covers everything you need to know to get started, from choosing a DC lighting fixture to the details of how to install it. It also includes information on how to get the most out of your DC lighting system.



How to wire a DC lighting circuit. This book provides the information you need to know about DC lighting, from the basics of how it works to the details of how to install a DC lighting circuit. The book covers everything you need to know to get started, from choosing a DC lighting fixture to the details of how to install it. It also includes information on how to get the most out of your DC lighting system.

Over 300 Photos and Illustrations Navigate each step of the project quickly and easily

Detailed Step-by-Step Instructions Never have to guess about what to do next

Visit wholehomenews.com

Follow us on     

Scan this code to visit our **WHOLE HOME NEWS** blog!



CATEGORY: HOME IMPROVEMENT

ISBN: 978-1-59186-635-0

UPC  \$18.99 US
£20.99 UK
\$11.99 CAN

 **COOL SPRINGS PRESS**
Home and Garden Experts™
www.coolspringspress.com

EAN  5 1899